

**COE 405**

**VHDL**

By Dr.  
**Aiman El-Maleh**

**Rayan Jamal Mufti**  
**985023**  
**Burhan Ali**  
**987528**

**Assignment 1**

## Q.1.

(i)

The entity description of the four bit carry look ahead adder is as follow:

```
-----  
-- ENTITY DESCRIPTION OF CLA  
-----  
--  
ENTITY CLA is  
PORT (      A,B: in      Bit_Vector (3 DOWNT0 0);      -- A & B ==> four bit inputs each.  
          C0:   in      Bit;                          -- C0 ==> Carry in (C zero).  
          S:    out     Bit_Vector (3 DOWNT0 0);      -- S ==> four bit output.  
          C4:   out     Bit);                          -- C4 ==> Carry out.  
END CLA;  
--
```

## Q.1.


(ii)

```
-----  
-- ARCHITECTURE DESCRIPTION OF CLA  
-----  
--  
ARCHITECTURE Arch1 of CLA4 is  
SIGNAL C1,C2,C3: Bit;  
SIGNAL P,G: Bit_Vector (3 DOWNT0 0);  
BEGIN  
    P(0) <= A(0)XOR B(0);      -- The propagate function of A & B.  
    G(0) <= A(0)AND B(0);      -- The generate function of A & B.  
    S(0) <= P(0)XOR C0 after 5 ns;  -- The sum of A & B.  
    C1  <= G(0)OR  
          (P(0)AND C0) after 3 ns;  -- The carry is generated after 2 gates only.  
-----  
    P(1) <= A(1)XOR B(1);      -- The propagate function of A & B.  
    G(1) <= A(1)AND B(1);      -- The generate function of A & B.  
    S(1) <= P(1)XOR C1 after 5 ns;  -- The sum of A & B.  
    C2  <= G(1)OR(P(1)AND G(0))OR  -- The carry is generated after 2 gates only.  
          (P(1)AND P(0)AND C0) after 3 ns;  
-----  
    P(2) <= A(2)XOR B(2);      -- The propagate function of A & B.  
    G(2) <= A(2)AND B(2);      -- The generate function of A & B.  
    S(2) <= P(2)XOR C2 after 5 ns;  -- The sum of A & B.  
    C3  <= G(2)OR (P(2)AND G(1))OR  -- The carry is generated after 2 gates only.  
          (P(2)AND P(1)AND G(0))OR  
          (P(2)AND P(1)AND P(0)AND C0) after 4 ns;  
-----  
    P(3) <= A(3)XOR B(3);      -- The propagate function of A & B.  
    G(3) <= A(3)AND B(3);      -- The generate function of A & B.  
    S(3) <= P(3)XOR C3 after 5 ns;  -- The sum of A & B.  
    C4  <= G(3)OR (P(3)AND G(2))OR  -- The carry is generated after 2 gates only.  
          (P(3)AND P(2)AND G(1))OR  
          (P(3)AND P(2)AND P(1)AND G(0))OR  
          (P(3)AND P(2)AND P(1)AND P(0)AND C0) after 5 ns;  
END Arch1;
```

**Q.1.**  
**(iii)**


*The simulation is working properly.*

 Example:     A: 1111  
              B: 1111 +  
              C0: 1 +  
              -----  
              S: 1111  
              C4: 1




```
>force A 1111 2ns
>force B 1111 2ns
>force C0 1 2ns
>run 15
```

 Example:     A: 0101  
              B: 1010 +  
              C0: 1 +  
              -----  
              S: 0000  
              C4: 1



```
>force A 0101 2ns
>force B 1010 2ns
>force C0 1 2ns
>run 15
```

 
Example:     A: 1001  
              B: 1011 +  
              C0: 0 +  
              -----  
              S: 0100  
              C4: 1



```
>force A 1001 2ns
>force B 1011 2ns
>force C0 0
>run 15
```

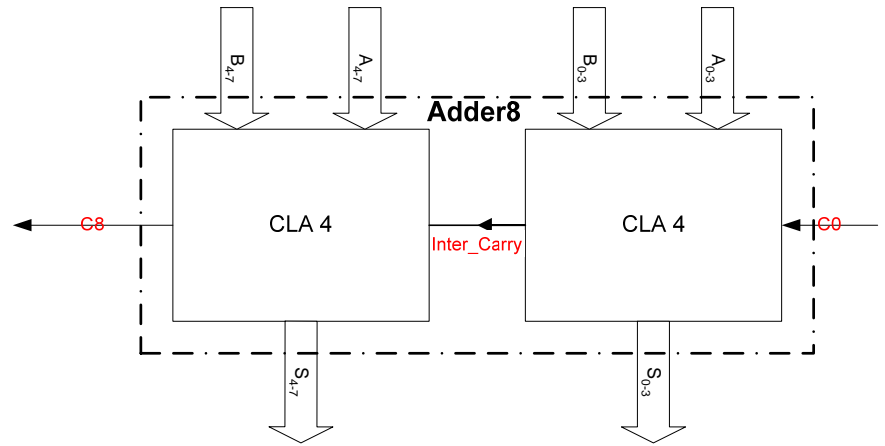**Q.2.**  
**(i)**

The Adder8 uses 2 instants of the four bits CLA. The carry goes out from CLA1 as C4 and connects to CLA2 C4 via an internal signal called "Inter\_Carry".



```

-----
--  ENTITY DESCRIPTION OF Adder8
-----
--
ENTITY Adder8 IS
PORT (
    SIGNAL X,Y : IN bit_vector (7 DOWNT0 0);           -- X & Y ==> eight bit inputs each.
    SIGNAL Z0   : IN bit ;                               -- Carry in
    SIGNAL P    : OUT bit_vector (7 DOWNT0 0) ;         -- P ==> eight bit outputs each.
    SIGNAL R8   : OUT bit ) ;                           -- Carry out
END Adder8 ;
--

```

**Q.2.**  
**(ii)**

```

-----
--  ARCHITECTURE DESCRIPTION OF Adder8
-----
--
ARCHITECTURE Struct OF Adder8 IS
    SIGNAL Inter_Carry : bit;
    COMPONENT CLA4
    PORT (
        A,B: in    Bit_Vector (3 downto 0);
        C0:  in    Bit;
        S:   out   Bit_Vector (3 downto 0);
        C4:  out   Bit
    );
    END COMPONENT;
BEGIN
    -- Instantiation:

    CLA1: CLA4 PORT MAP (    X(3 DOWNT0 0)             --X(3),X(2),X(1),X(0)
                            Y(3 DOWNT0 0),             --Y(3),Y(2),Y(1),Y(0)
                            Z0,
                            P(3 DOWNT0 0),             --P(3),(2),P(1),P(0)
                            Inter_Carry
    );


    CLA2: CLA4 PORT MAP (    X(7 DOWNT0 4),             --X(7),X(6),X(5),X(4)
                            Y(7 DOWNT0 4),             --Y(7),Y(6),Y(5),Y(4)
                            Inter_Carry,
                            P(7 DOWNT0 4),             --P(7),P(6),P(5),P(4)
                            C8
    );
END Struct;

```

**Q.2.**  
**(iii)**


*The simulation is working properly.*

 Example: X: 1111 1111  
Y: 1111 1111 +  
Z0: 1 +  
-----  
P: 1111 1111  
C8 1




```
>force X 11111111 2ns
>force Y 11111111 2ns
>force Z0 1 2ns
>run 20
```

 Example: X: 1010 1010  
Y: 0101 0101 +  
Z0: 1 +  
-----  
P: 0000 0000  
C8 1



```
>force X 10101010 2ns
>force Y 01010101 2ns
>force Z0 1 2ns
>run 20
```

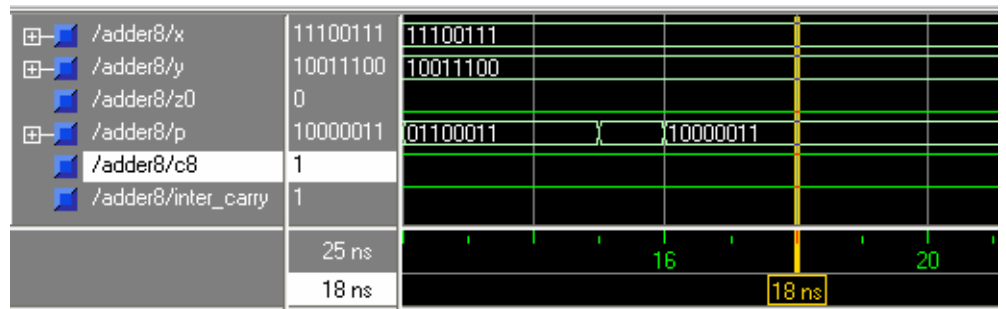Example: X: 1110 0111  
Y: 1001 1100 +  
Z0: 0 +  
-----  
P: 1000 0011  
C8 1



```
>force X 11100111 2ns
>force Y 10011100 2ns
>force Z0 1 2ns
>run 20
```