

HW#1 Solution**Q1-i**

Entity CLA4 is

```
port ( a , b : IN Bit_Vector(3 downto 0) ; s : OUT Bit_Vector(3 downTo 0) ;
      Cin : in Bit; C3 : out Bit) ;
End;
```

Q1-ii

Architecture Arch1 of CLA4 is

```
SIGNAL P , G : Bit_Vector(3 downto 0);
SIGNAL c0 , c1 , c2 : bit;
```

Begin

```
-- Pi = Ai Xor Bi
-- Gi = Ai And Bi
-- Si = Pi Xor Ci
-- C(i+1) = Gi Or (Pi And Ci)
P(0) <= a(0) Xor b(0);
G(0) <= a(0) And b(0);
```

```
P(1) <= a(1) Xor b(1);
G(1) <= a(1) And b(1);
```

```
P(2) <= a(2) Xor b(2);
G(2) <= a(2) And b(2);
```

```
P(3) <= a(3) Xor b(3);
G(3) <= a(3) And b(3);
```

```
s(0) <= P(0) Xor Cin ;
c0 <= G(0) OR (p(0) AND Cin);
```

```
s(1) <= P(1) XOR c0;
c1 <= G(1) OR (P(1) And G(0))
OR (P(1) And P(0) And Cin);
```


```
s(2) <= P(2) XOR c1;
c2 <= G(2) OR (P(2) AND G(1))
OR (P(2) AND P(1) AND G(0))
OR (P(2) And P(1) And P(0) And Cin);
```

```

s(3) <= P(3) XOR c2;
c3 <= G(3) OR (P(3) And G(2))
    OR (P(3) And P(2) And G(1))
    OR (P(3) AND P(2) And P(1) And G(0))
    OR (P(3) AND P(2) And P(1) AND P(0) And Cin);
End Arch1 ;

```

Q1-iii

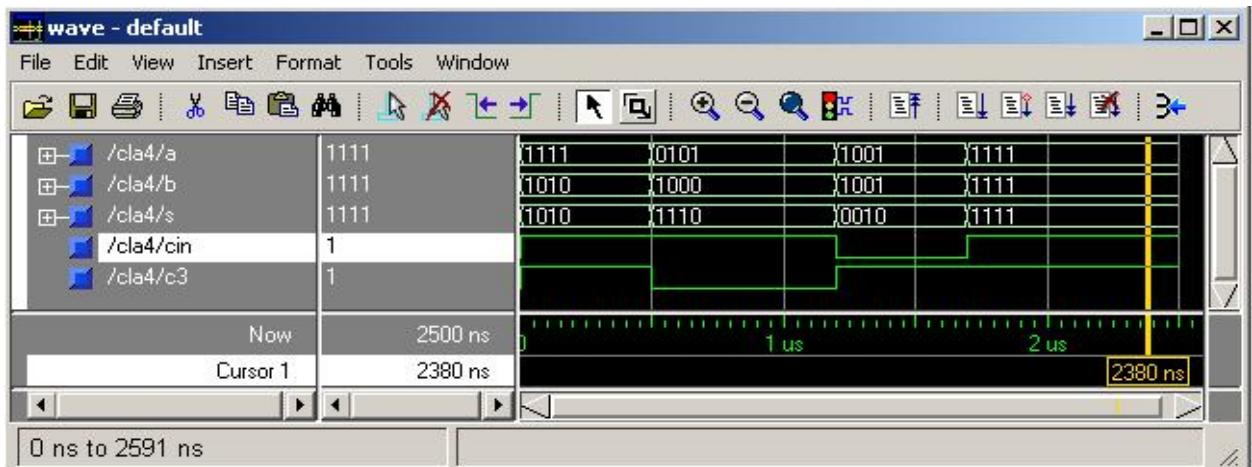

Q1-iv

-- Define the entities needed in gate level architecture

Entity AND2 is
PORT(a , b : IN bit ; c : OUT bit);
End ;

Architecture and2Arch of AND2 is
Begin
c <= a AND b after 2 ns;
End and2Arch;

Entity OR2 is
PORT(a , b : IN bit ; c : OUT bit);
End ;

Architecture OR2Arch of OR2 is
Begin
c <= a OR b after 2 ns;
End OR2Arch;

```
-----  
Entity XOR2 is  
PORT(a , b : IN bit ; c : OUT bit);  
End ;
```

```
Architecture XOR2Arch of XOR2 is  
Begin  
c <= a XOR b after 2 ns;  
End XOR2Arch;
```

```
Entity C0Eval is  
PORT(a , b , c : IN bit ; d : OUT bit);  
End ;  
---- c0 <= G(0) OR (p(0) AND Cin);  
Architecture C0Arch of C0Eval is  
Begin  
d <= a OR (b And c) after 3 ns; -- since we have 3 inputs  
End C0Arch;
```

```
Entity C1Eval is  
PORT(a , b , c , d , e : IN bit ; f : OUT bit);  
End ;  
---- c1 <= G(1) OR (P(1) And G(0))  
---- OR (P(1) And P(0) And Cin);  
Architecture C1Arch of C1Eval is  
Begin  
f <= a OR (b And c) OR (b AND d And e) after 5 ns;  
End C1Arch;
```

```
Entity C2Eval is  
PORT(a, b , c ,d, e, f , g : IN bit ; h : OUT bit);  
End ;  
---- c2 <= G(2) OR (P(2) AND G(1))  
---- OR (P(2) AND P(1) AND G(0))  
---- OR (P(2) And P(1) And P(0) And Cin);
```

```
Architecture C2Arch of C2Eval is  
Begin
```

```
h <= a OR (b AND c)
```

```
    OR (b AND d AND e)
    OR (b AND d AND f And g) after 7 ns; -- since we have 7 inputs
End C2Arch;
```

```
Entity C3Eval is
PORT(a, b , c ,d, e, f , g , h , i : IN bit ; j : OUT bit);
End ;
```

```
---- c3  <= G(3) OR (P(3) And G(2))
----      OR (P(3) And P(2) And G(1))
----      OR (P(3) AND P(2) And P(1) And G(0))
----      OR (P(3) AND P(2) And P(1) AND P(0) And Cin);
```

```
Architecture C3Arch of C3Eval is
Begin
```

```
j  <=  a OR (b And c)
      OR (b And d And e)
      OR (b AND d And f And g)
      OR (b AND d And f AND h And i) after 9 ns;
End C3Arch;
```

```
Architecture Arch2 of CLA4 is
SIGNAL P , G : Bit_Vector(3 downto 0);
SIGNAL c0 , c1 , c2 : bit;
```

```
component AND2
port(a,b:in bit; c:out bit);
end component ;
```

```
component OR2
port(a,b:in bit; c:out bit);
end component ;
```

```
component XOR2
port(a,b:in bit; c:out bit);
end component ;
```

```
component c0Eval
port(a,b,c:in bit; d:out bit);
end component ;
```

```
component c1Eval
port(a,b,c,d,e:in bit; f:out bit);
end component ;
```

```

component c2Eval
port(a,b,c,d,e,f,g:in bit; h:out bit);
end component ;

component c3Eval
port(a,b,c,d,e,f,g,h,i:in bit; j:out bit);
end component ;

Begin
g0 : AND2 PORT MAP (a(0), b(0), G(0) );
g1 : AND2 PORT MAP (a(1), b(1), G(1) );
g2 : AND2 PORT MAP (a(2), b(2), G(2) );
g3 : AND2 PORT MAP (a(3), b(3), G(3) );

p0 : XOR2 PORT MAP (a(0), b(0), P(0) );
p1 : XOR2 PORT MAP (a(1), b(1), P(1) );
p2 : XOR2 PORT MAP (a(2), b(2), P(2) );
p3 : XOR2 PORT MAP (a(3), b(3), P(3) );

sum0 : XOR2 PORT MAP (P(0) , Cin , s(0));
car0 : C0Eval PORT MAP (G(0) , P(0) , Cin , c0 );

sum1 : XOR2 PORT MAP (P(1) , c0 , s(1));
car1 : c1Eval PORT MAP (a => G(1) ,b=> P(1) ,c=> G(0) ,d=> P(0) ,e=> Cin , f=> c1);

sum2 : XOR2 PORT MAP (P(2) , c1 , s(2));
car2 : c2Eval PORT MAP (G(2) , P(2) ,G(1),P(1),G(0),P(0),Cin, c2);


sum3 : XOR2 PORT MAP (P(3) , c2 , s(3));
car3 : c3Eval PORT MAP (G(3), P(3) , G(2) ,P(2), G(1), P(1) , G(0) , P(0) , Cin , c3);

End Arch2;

```

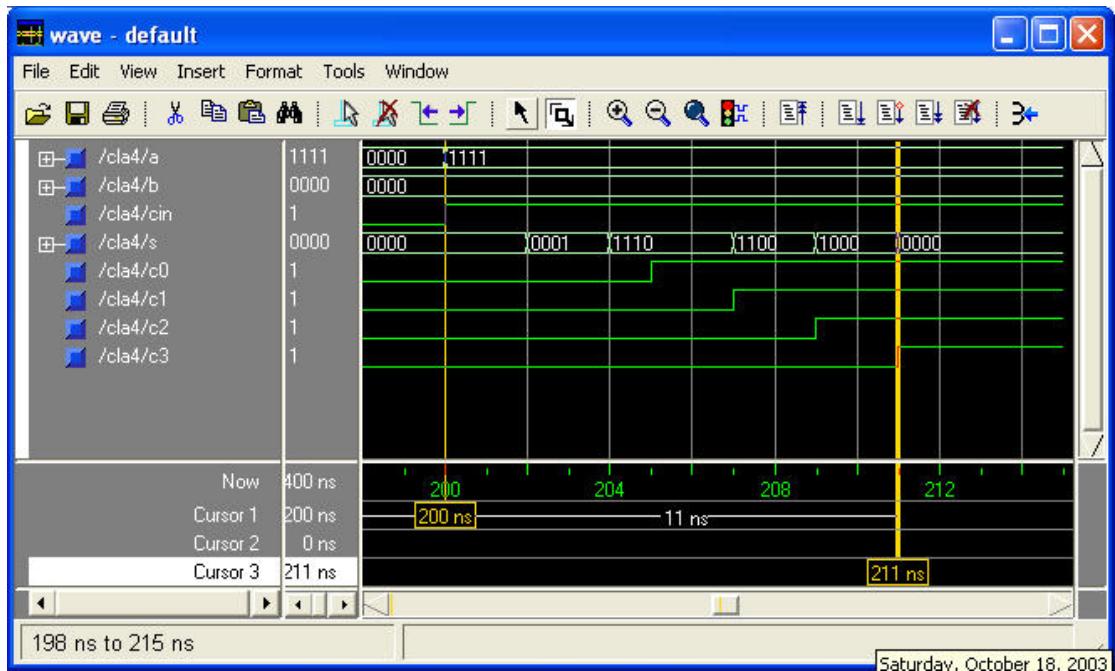Q1-v

Critical path highlighted when carry-in is propagated through all stages to C3. The critical path delay is 11ns.



Q2-i

Entity FAR is
 port (d,clk,reset : in BIT ; q : out BIT);
 End FAR;


Q2-ii

Architecture Arch1 of FAR is
 Begin

```
process (clk , reset)
Begin
  if reset = '0' then
    q <= '0';
  else
    if (clk= '1' and clk'Event) then
      q <= d ;
    end if;
  end if ;
End process;
End Arch1;
```

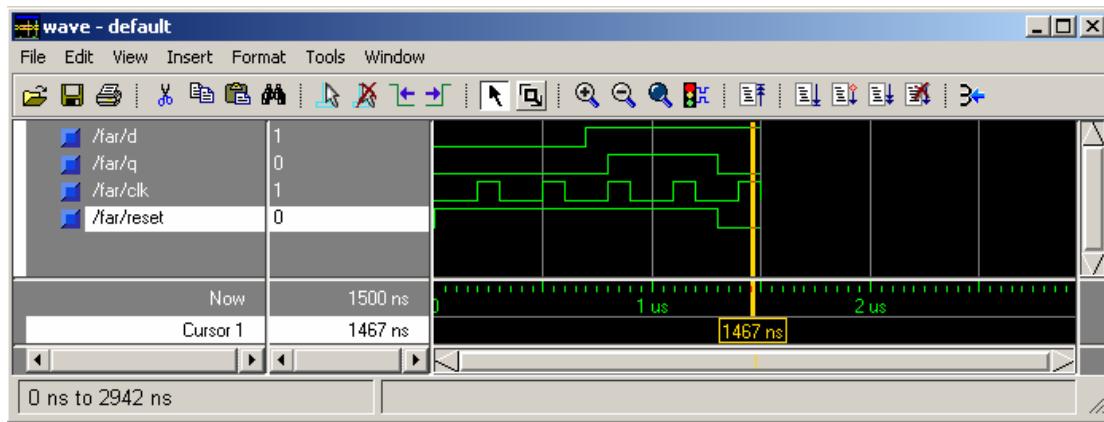Q2-iii

The following figure shows the operation of D-flip flop with a synchronous rising edge clock and asynchronous reset .



Q2-iv

Entity Reg4 is

```
Port(i:In Bit_Vector(3 downto 0);clock,res:IN BIT;o:OUT bit_Vector(3 downto 0));
End Reg4;
```

Q2-v

Architecture ArchReg1 of Reg4 is


```
component FAR
port (d,clk,reset : in bit ; q : OUT bit);
End component;

begin
bit0 : FAR PORT MAP (i(0),clock,res,o(0));
bit1 : FAR PORT MAP (i(1),clock,res,o(1));
bit2 : FAR PORT MAP (i(2),clock,res,o(2));
bit3 : FAR PORT MAP (i(3),clock,res,o(3));

End ArchReg1;
```

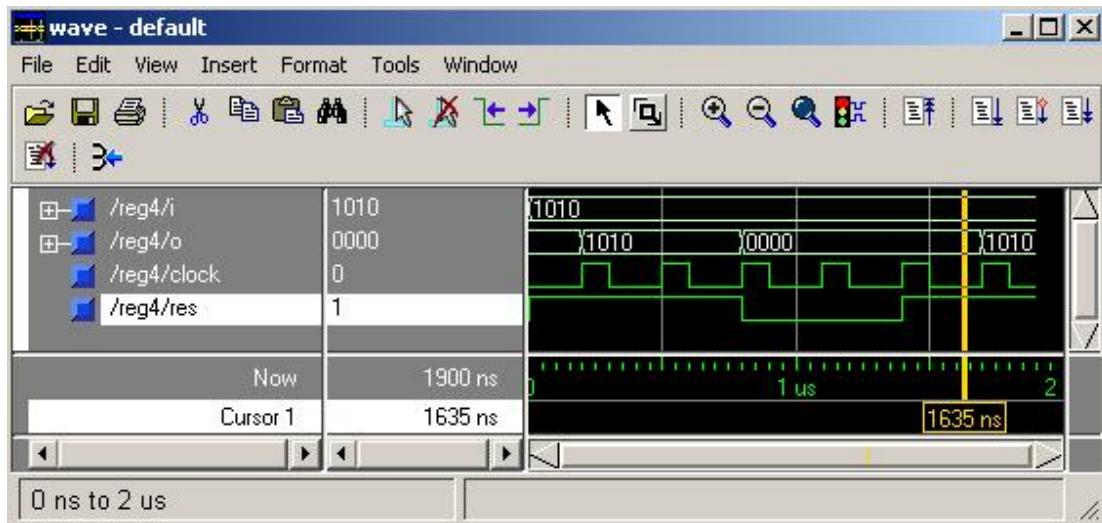Q2-vi

The following figure shows the operation of the Register that has 4 D-flip flops.



Q3-i

Entity ACC Is

```
port( reset , clk : in BIT ; a : inout  BIT_vector(3 downto 0);
      b : in  BIT_vector(3 downto 0));
```

End ACC;

Q3-ii

Architecture Arch1 of ACC is

```
signal sum : Bit_Vector(3 downto 0);
signal out_of_reg : bit_vector(3 downto 0);
signal ci : bit:= '0';
signal c3 : bit;
```

```
component Reg4
Port(i:In Bit_Vector(3 downto 0);clock,res:IN BIT;o:OUT bit_Vector(3 downto 0));
End component ;
```

```
component CLA4
port ( a , b : IN Bit_Vector(3 downto 0) ; s : OUT Bit_Vector(3 downTo 0) ;
      Cin : in Bit; C3 : out Bit) ;
End component ;
```

Begin

```
Addi : CLA4 PORT MAP(a,b,sum,ci,c3);
rege : Reg4 PORT MAP(sum,clk,reset,out_of_reg);
```

```
process (out_of_reg)
```


```
Begin
```

```
a <= out_of_reg;
```


```
end process ;
```

```
End Arch1;
```

Q3-iii

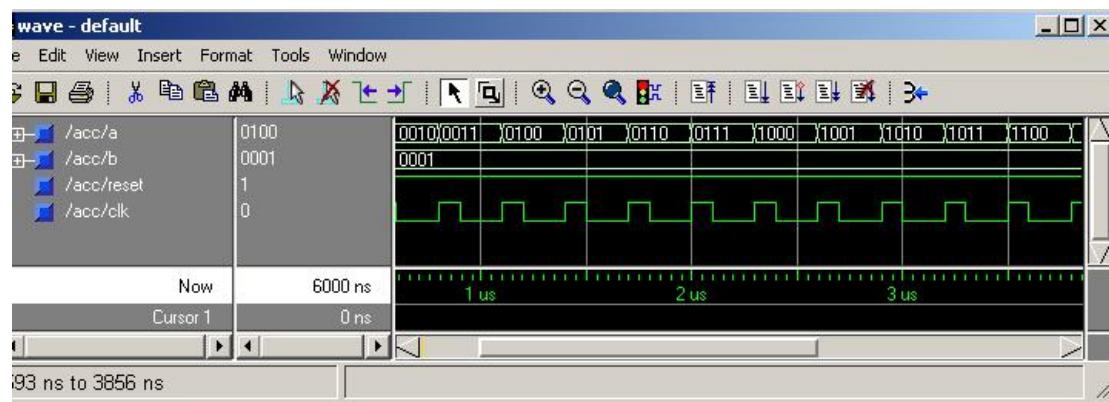

up counter

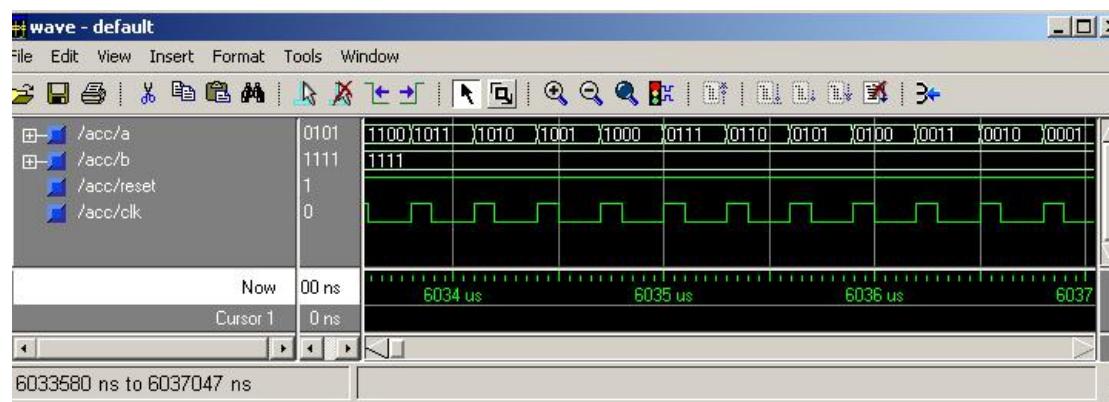

down counter