

## COE 405, Term 131

### Design & Modeling of Digital Systems

#### HW# 1 Solution

**Due date: Sunday, Sep. 29**


- Q.1.** Consider the two functions  $f = abc + a'b'c'$  and  $g = ab + a'c$ .
- (i) Implement the function  $f$  using a single 4x1 MUX.
  - (ii) Compute the complement of  $f$ .
  - (iii) Compute the function  $f \oplus g$  based on orthonormal basis expansion.
- Q.2.** It is required to design a combinational circuit that computes the equation  $Y = 5 * X$ , where  $X$  is an  $n$ -bit unsigned number.
- (i) Design the circuit as a modular circuit where each module receives a single bit of the input,  $X_i$ .
  - (ii) Derive the truth table of your 1-bit module in (i).
  - (iii) Derive minimized two-level sum-of-product equations for your 1-bit module circuit.
  - (iv) Verify the correctness of your design by modeling and simulating a 4-bit circuit using logicworks.
  - (v) Assume that the delay of a gate is related to the number of its inputs, i.e. the delay of an inverter is 1, the delay of a 2-input gate is 2, etc. Compute the maximum propagation delay of your  $n$ -bit circuit.
  - (vi) Verify the correctness of your maximum propagation delay calculation by measuring the longest delay for a 4-bit circuit using logicworks.

## HW#1 Solution

$$\text{Q1. } f = abc + \bar{a}\bar{b}\bar{c}$$

$$g = ab + \bar{a}c$$
 
$$\text{(i) } f = \bar{a}\bar{b} [\bar{c}] + \bar{a}b [0] \\ + a\bar{b} [0] + ab [c]$$



$$\text{(ii) } \bar{f} = \bar{a}\bar{b} [c] + \bar{a}b [1] \\ + a\bar{b} [1] + ab\bar{c} \\ = \bar{a}\bar{b}c + \bar{a}b + a\bar{b} + ab\bar{c}$$


$$\text{(iii) } g = \bar{a}\bar{b} [c] + \bar{a}b [c] \\ + a\bar{b} [0] + ab [1]$$

$$f \oplus g = \bar{a}\bar{b} [1] + \bar{a}b [c] \\ + a\bar{b} [0] + ab [\bar{c}] \\ = \bar{a}\bar{b} + \bar{a}bc + ab\bar{c}$$

Q2.  $Y = 5 \times X$

 (i) By analyzing the problem, we can deduce that the largest carry-out is 4. Thus, we need 3 bits to be transferred between the modules.

The interface for the 1-bit module is as follows:



(ii) Truth Table:

$x_i$	$C_{in2}$	$C_{in1}$	$C_{in0}$	$C_{out2}$	$C_{out1}$	$C_{out0}$	$Y_i$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	1
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
1	0	0	0	0	1	0	1
1	0	0	1	0	1	1	0
1	0	1	0	0	0	0	0
1	0	1	1	0	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	1	0	0	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	1

(iii)

$x_1 C_{in2}$ \ $C_{in1} C_{in0}$	00	01	11	10
00	0	0	0	0
01	0	x	x	x
11	1	x	x	x
10	0	0	1	0

$$C_{out2} = x_1 C_{in2} + x_1 C_{in1} C_{in0}$$

$x_1 C_{in2}$ \ $C_{in1} C_{in0}$	00	01	11	10
00	0	0	0	0
01	1	x	x	x
11	0	x	x	x
10	1	1	0	1

$$C_{out1} = \bar{x}_1 C_{in2} + x_1 \bar{C}_{in2} \bar{C}_{in1} + x_1 \bar{C}_{in2} \bar{C}_{in0}$$


$x_1 C_{in2}$ \ $C_{in1} C_{in0}$	00	01	11	10
00	0	0	1	1
01	0	x	x	x
11	0	x	x	x
10	0	1	0	1



$$C_{out0} = \bar{x}_1 C_{in1} + C_{in1} \bar{C}_{in0} + x_1 \bar{C}_{in1} C_{in0}$$

$x_1 C_{in2}$ \ $C_{in1} C_{in0}$	00	01	11	10
00	0	1	1	0
01	0	x	x	x
11	1	x	x	x
10	1	0	0	1

$$Y_i = \bar{x}_1 C_{in0} + x_1 \bar{C}_{in0}$$

(iv)

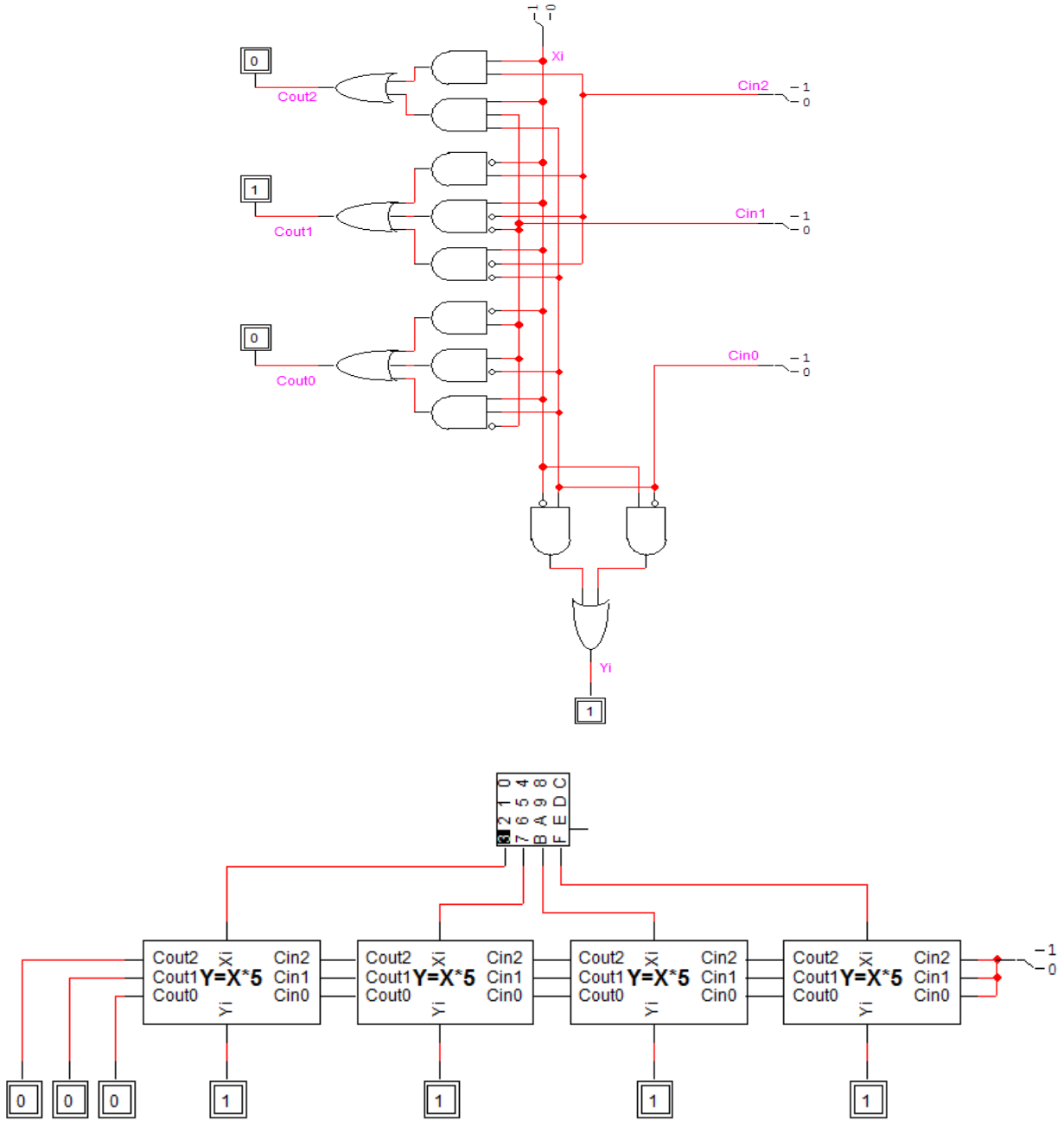

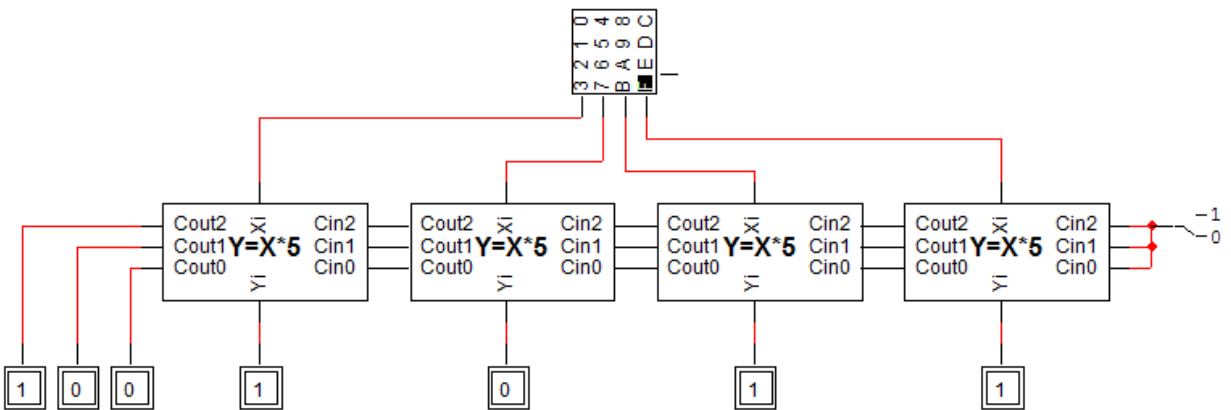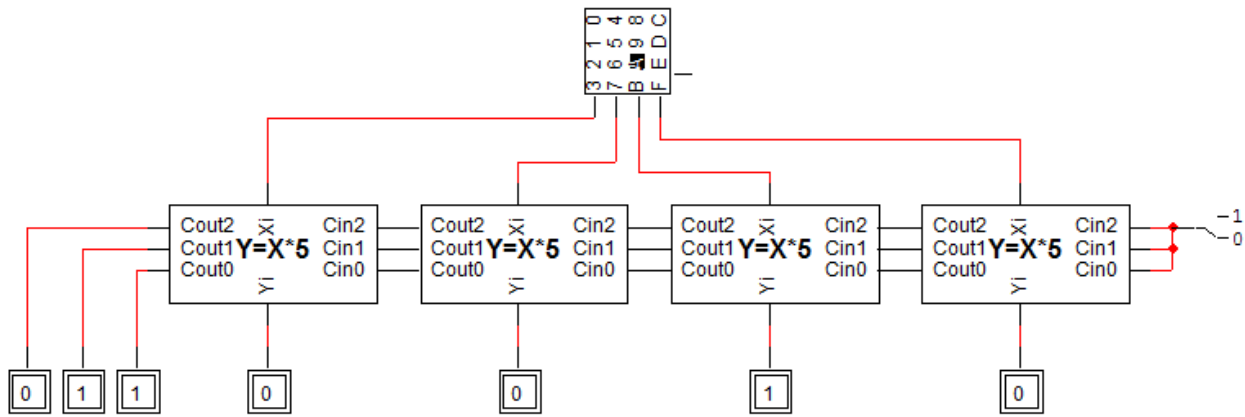

(v) To simplify the analysis, I add an inverter delay to any gate that has one of the inputs inverted. A very quick analysis by computing the longest delay across one cell, one can deduce that the longest delay across a cell is 7. Thus, having 4 cells the worst case delay is estimated to be  $4 \times 7 = 28$ .

(vi) To verify our analysis we changed X from 0 to 13 and computed the difference from the time X has changed ( $=2110$ ) to the time when Y3 has changed ( $=2138$ ) giving a total delay  $=2138 - 2110 = 28$ .

