

COE 405, Term 152

Design & Modeling of Digital Systems


HW# 1 Solution

Due date: Thursday, Feb. 11

Q.1. Consider the two functions $f = a \oplus b \oplus c$ and $g = a'b + a'c + bc$.

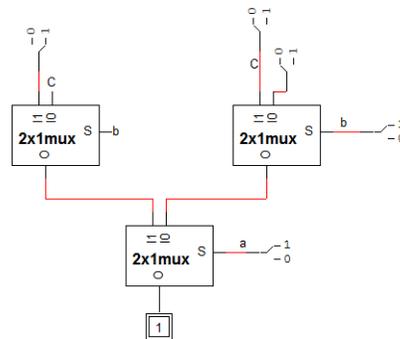(i) Implement the function g using only 2x1 MUXs.

$$g = a' [b'c] + a [b + c] = a' [b' [0] + b [c]] + a [b' [c] + b [1]]$$



(ii) Compute the function $f \oplus g$ based on orthonormal basis expansion.

$$f = a'b' [c] + a'b [c'] + ab' [c'] + ab [c]$$


$$g = a'b' [0] + a'b [c] + ab' [c] + ab [1]$$

$$f \oplus g = a'b' [c] + a'b [1] + ab' [1] + ab [c'] = a'b'c + a'b + ab' + abc' = a'c + a'b + ab' + ac'$$

Q.2. It is required to design a combinational circuit that computes the equation $Y = 3 * X - 1$, where X is an n -bit signed 2's complement number.

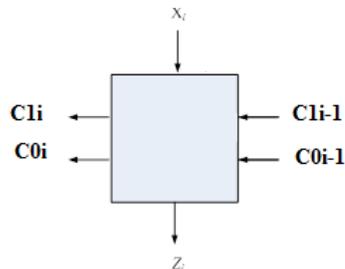(i) Design the circuit as a modular circuit where each module receives a single bit of the input, X_i .

This circuit can be designed by assuming that we have a borrow feeding the first cell or by representing -1 in 2's complement as $11 \dots 111$ and adding this 1 ion each cell. I will follow the second approach. We need to represent carry-out values in the range 0 to 3. Thus, we need to signals to represent Carry out values.



(ii) Derive the truth table of your 1-bit module in (i).

C_{i-1}	C_{0i-1}	X_i	C_{1i}	C_{0i}	Z_i
0	0	0	0	0	1
0	0	1	1	0	0
0	1	0	0	1	0
0	1	1	1	0	1
1	0	0	0	1	1
1	0	1	1	1	0
1	1	0	1	0	0
1	1	1	1	1	1

(iii) Derive minimized two-level sum-of-product equations for your 1-bit module circuit.

	00	01	11	10
0	1 0	0 1	1 3	0 2
1	1 4	0 5	1 7	0 6

$$Z = (C_{0i-1} \oplus X_i)'$$


	00	01	11	10
0	0 0	0 1	0 3	1 2
1	1 4	1 5	1 7	0 6





$$C_{0i} = C_{1i-1} C_{0i-1}' + C_{1i-1} X_i + C_{1i-1}' C_{0i-1} X_i' = C_{1i-1} (C_{0i-1}' + X_i) + C_{1i-1}' C_{0i-1} X_i' = C_{1i-1} \oplus (C_{0i-1} X_i')$$



	00	01	11	10
0	0 0	1 1	1 3	0 2
1	0 4	1 5	1 7	1 6

$$C_{1i} = X_i + C_{1i-1} C_{0i-1}$$

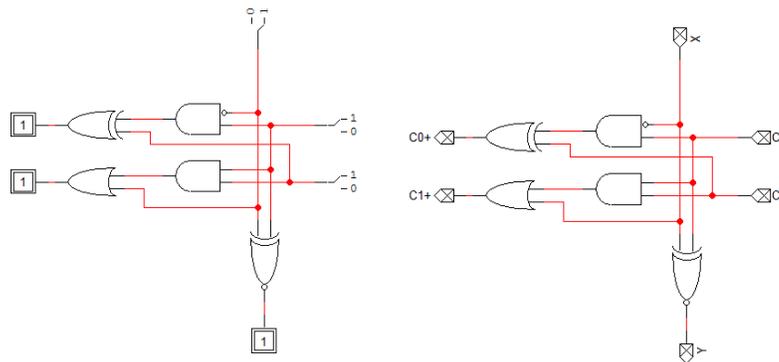(iv) Verify the correctness of your design by modeling and simulating a circuit to compute the required equation assuming X is a 4-bit number using logicworks.



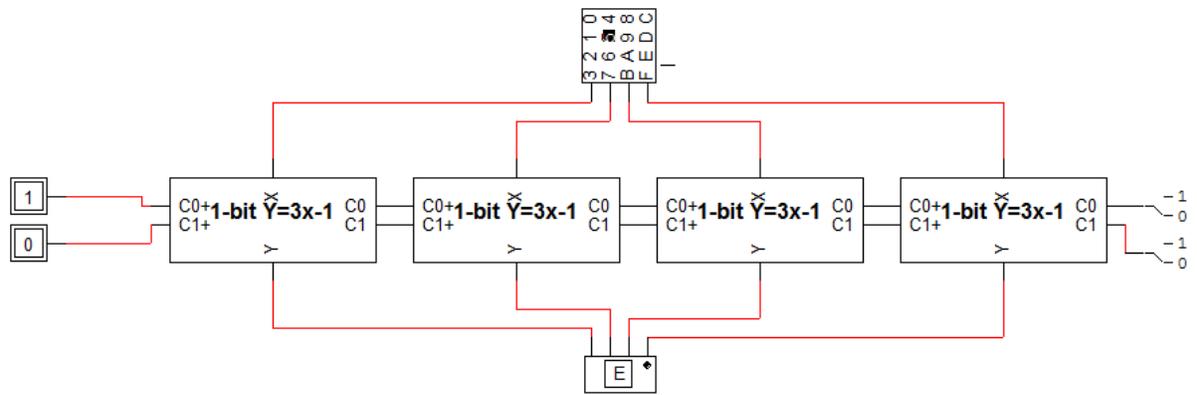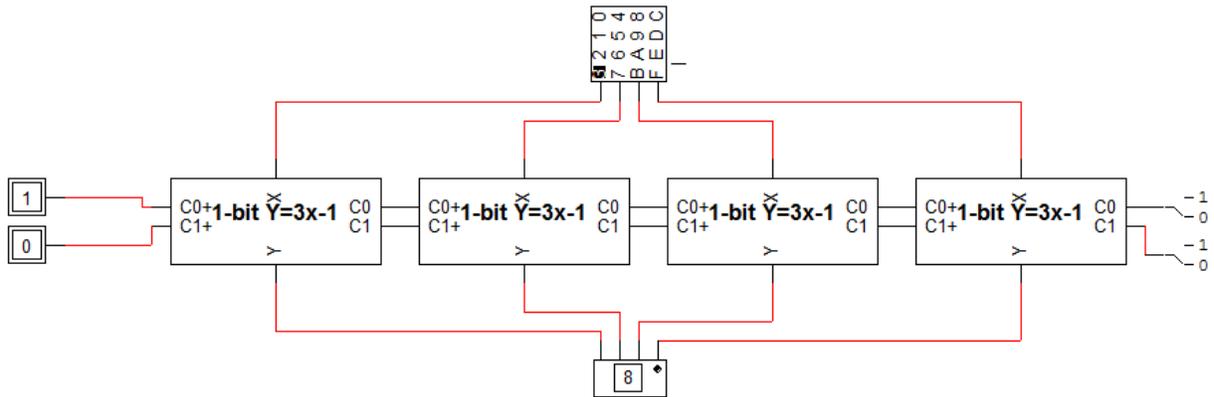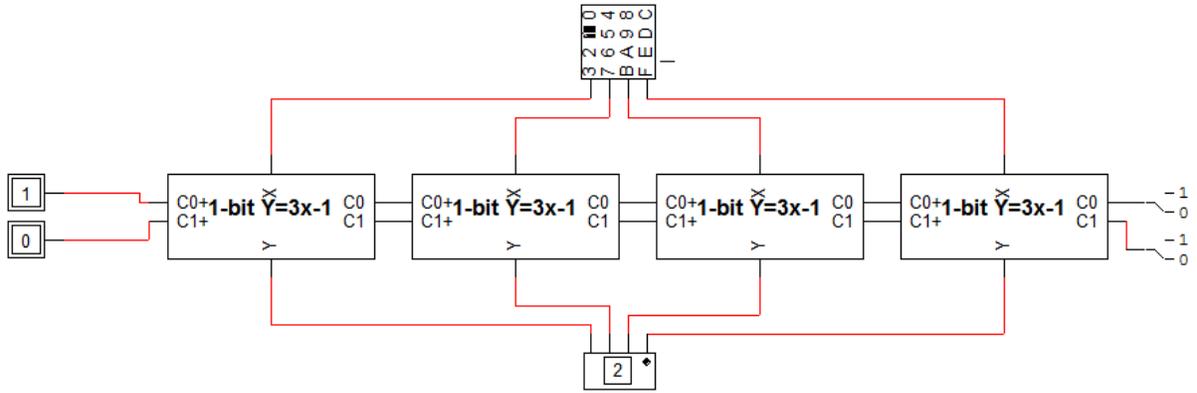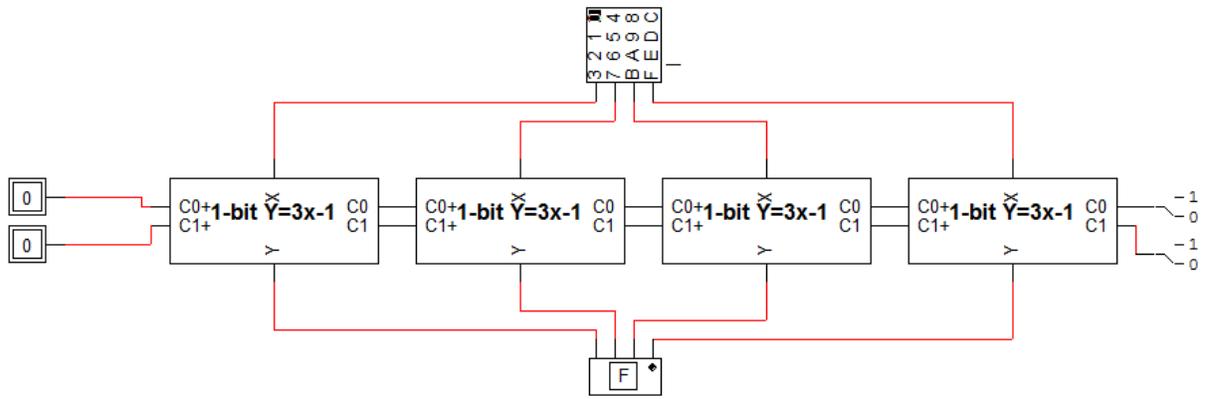

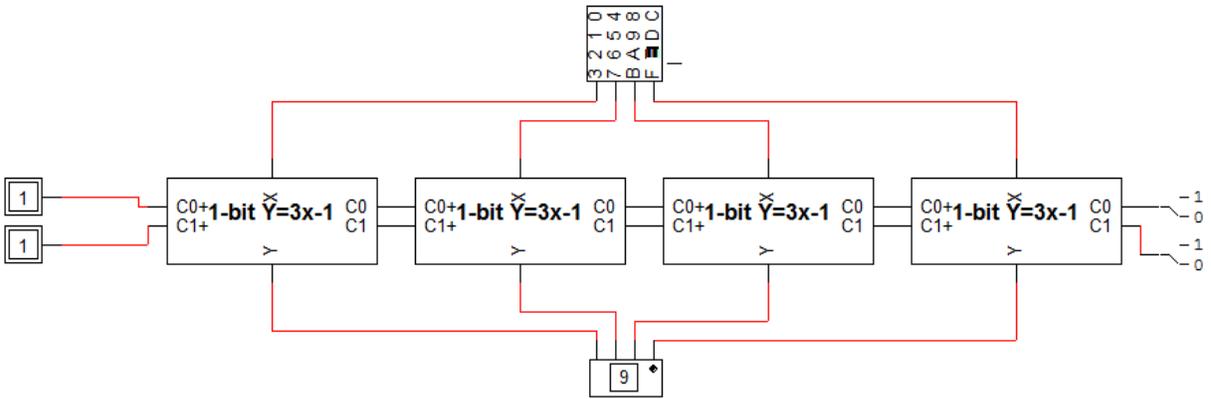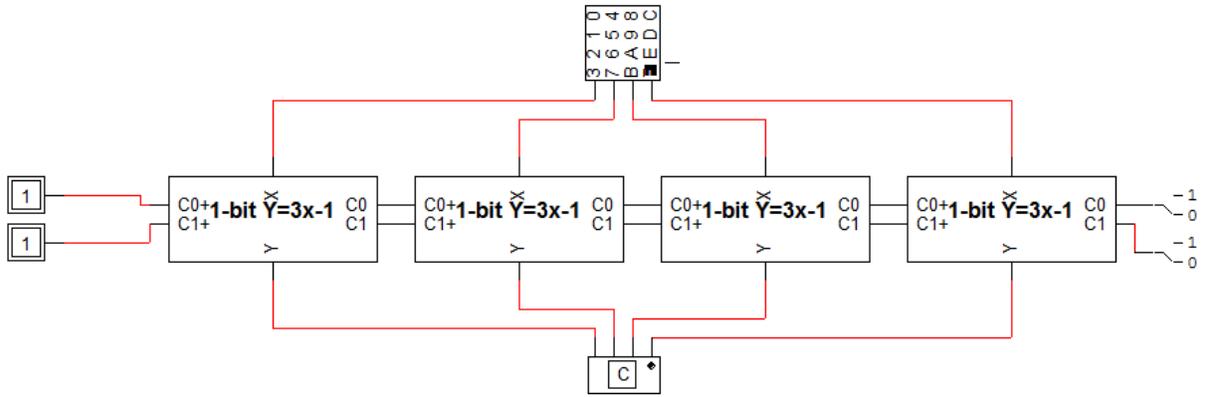

Note that for values whose correct result will not fit in 4-bits such as values ≥ 6 will not produce correct results. We need to use larger number of cells to ensure that the correct output will fit.

