

COE 405, Term 062

Design & Modeling of Digital Systems


HW# 2 Solution

Due date: Monday, March 26, 2007

- Q.1.** It is required to design an **8-bit shift register**. The shift register should be able to shift or rotate either left or right based on the following table:

S1 S0	Operation
00	Shift left
01	Shift right
10	Rotate left
11	Rotate right

 The reset is a synchronous reset and the shift register is rising-edge triggered. Assume that the shifted bit is based on the input SI. The interface description of the 8-bit shifter is shown below.



- (i)** Describe an Entity **Shifter8** for the 8-bit shift register.

```
Entity Shifter is
Generic (N: Integer :=8);
Port (clk, reset, S1, S0, SI : IN Bit;
      S : Buffer Bit_Vector(N-1 Downto 0));
End;
```

- (ii)** Model a behavioral Architecture **Behave** for this 8-bit shift register. Verify its correctness by simulation.


```
Architecture behave of shifter is
begin
  process(clk)
```

```

begin
    if (clk = '1' and clk'event) then
        if(reset='1') then s <= (N-1 Downto 0 =>'0');

        elsif(s0='0' and s1='0') then
            s <=s(N-2 downto 0)&si;
        elsif(s0='1' and s1='0') then
            s <=si&s(N-1 downto 1);
        elsif(s0='0' and s1='1') then
            s <=s(N-2 downto 0 )&s(N-1);
        elsif(s0='1' and s1='1') then
            s <=s(0)&s(N-1 downto 1);
        end if;
    end if;
end process;
end behave;

```

 

- (iii) Model a structural Architecture **Struct** for this 8-bit shift register. Make your model generic using GENERATE statement to instantiate the required components such that your design can be extended into a shift register of any size by changing just a size parameter. Use configuration statement to configure the bounding of used components to entities. Verify the correctness of your model by simulation.

Entity DFF is
PORT(CLK, RESET, D: IN Bit; Q: OUT BIT);
END;
Architecture BV of DFF is
Begin
Process(CLK)
Begin
If (CLK='1' and CLK'Event) Then
If (Reset='1')Then

```

        Q <= '0';
    Else
        Q <= D;
    End if;
End if,
End Process;
End;

```

Entity Mux4x1 is

Port (I0, I1, I2, I3, S1, S0: IN Bit; O: OUT BIT);

End;

Architecture BV of Mux4x1 is

Begin

Process(I0, I1, I2, I3, S1, S0)

Variable T: Bit_Vector (1 Downto 0);

Begin

T := S1 & S0;

Case T is

When "00" => O <= I0;

When "01" => O <= I1;

When "10" => O <= I2;

When "11" => O <= I3;

End Case;

End Process;

End;

Architecture ST of Shifter is

Component DFF

PORT(CLK, RESET, D: IN Bit; Q: OUT BIT);

END Component;

Component Mux4x1

Port (I0, I1, I2, I3, S1, S0: IN Bit; O: OUT BIT);

End Component;

For ALL: DFF Use Entity Work.DFF(BV);

For ALL: Mux4x1 Use Entity Work.Mux4x1(BV);

Signal MO, SO: Bit_Vector(N-1 Downto 0);

Begin

MX0: Mux4x1 PORT MAP (SI, SO(1), SO(N-1), SO(1), S1, S0, MO(0));

DF0: DFF PORT MAP (CLK, RESET, MO(0) , SO(0));

GS: For I IN 1 To N-2 Generate


 MXI: Mux4x1 PORT MAP (SO(I-1), SO(I+1), SO(I-1), SO(I+1), S1, S0, MO(I));

 DFI: DFF PORT MAP (CLK, RESET, MO(I) , SO(I));

```

End Generate;
MXL: Mux4x1 PORT MAP (SO(N-2), SI, SO(N-2), SO(0), S1, S0, MO(N-1));
DFL: DFF PORT MAP (CLK, RESET, MO(N-1) , SO(N-1) );
S <= SO;
End;

```

 

Q.2. (Problem 4.15)

Given the following signal assignments, show all transactions placed on each signal. At each event, show transactions that are appended, overwritten, and expired. Show resulting waveforms on each signal.

Architecture dataflow of signals IS

Type qit is ('0', '1', 'Z', 'X');

Signal a, b, c: qit := '0';

Begin

a <= NOT a after 10ns WHEN NOW <= 30 ns;

b <= 'Z', a after 25 ns, '0' after 35 ns;

c <= '1', a after 5 ns, b after 20 ns;

End dataflow;

Time	0	δ	2δ	5 ns	10 ns	$10 + \delta$	15 ns
A	0	0	0	0	1	1	1
	('1', 10 ns)	('1', 10 ns)	('1', 10 ns)	('1', 5 ns)	('0', 10 ns)	('0', 10 ns)	('0', 5 ns)
B	0	Z	Z	Z	Z	Z	Z
	('Z', δ) ('0', 25 ns) ('0', 35 ns)	('0', 25 ns) ('0', 35 ns)	('0', 25 ns) ('0', 35 ns)	('0', 20 ns) ('0', 30 ns)	($'0'$, 15 ns) ($'0'$, 25 ns) ('Z', δ) ('1', 25 ns) ('0', 35 ns)	('1', 25 ns) ('0', 35 ns)	('1', 20 ns) ('0', 30 ns)
C	0	1	1	0	0	1	1
	('1', δ) ('0', 5 ns) ('0', 20 ns)	($'0'$, 5 ns) ($'0'$, 20 ns)	('0', 5 ns) ('Z', 20 ns)	('Z', 15 ns)	($'Z'$, 10 ns) ('1', δ) ('1', 5 ns) ('Z', 20 ns)	('1', 5 ns) ('Z', 20 ns)	('Z', 15 ns)

Time	20 ns	$20 + \delta$	25 ns	30 ns	$30 + \delta$	35 ns	40 ns
A	0	0	0	1	1	1	0
	('1', 10 ns)	('1', 10 ns)	('1', 5 ns)	('0', 10 ns)	('0', 10 ns)	('0', 5 ns)	-----
B	Z	Z	Z	Z	Z	Z	Z
	($'1'$, 15 ns) ($'0'$, 25 ns) ('Z', δ) ('0', 25 ns) ('0', 35 ns)	('0', 25 ns) ('0', 35 ns)	('0', 20 ns) ('0', 30 ns)	($'0'$, 15 ns) ($'0'$, 25 ns) ('Z', δ) ('1', 25 ns) ('0', 35 ns)	('1', 25 ns) ('0', 35 ns)	('1', 20 ns) ('0', 30 ns)	($'1'$, 15 ns) ($'0'$, 25 ns) ('Z', δ) ('0', 25 ns) ('0', 35 ns)
C	1	1	0	0	1	1	1
	($'Z'$, 10 ns) ('1', δ) ('0', 5 ns) ('Z', 20 ns)	('0', 5 ns) ('Z', 20 ns)	('Z', 15 ns)	($'Z'$, 10 ns) ('1', δ) ('1', 5 ns) ('Z', 20 ns)	('1', 5 ns) ('Z', 20 ns)	('Z', 15 ns)	($'Z'$, 10 ns) ('1', δ) ('0', 5 ns) ('Z', 20 ns)

Time	$40 + \delta$	45 ns	60 ns	65 ns	$65 + \delta$	70 ns	75 ns	85
A	0	0	0	0	0	0	0	0
	----	----	----	----	----	----	----	----
B	Z	Z	Z	0	0	0	0	0
	('0', 25 ns) ('0', 35 ns)	('0', 20 ns) ('0', 30 ns)	('0', 5 ns) ('0', 15 ns)	('0', 10 ns)	('0', 10 ns)	('0', 5 ns)	----	----
C	1	0	Z	Z	1	0	0	0
	('0', 5 ns) ('Z', 20 ns)	('Z', 15 ns)	----	('1', δ) ('0', 5 ns) ('0', 20 ns)	('0', 5 ns) ('0', 20 ns)	('0', 15 ns)	('0', 10 ns)	----

