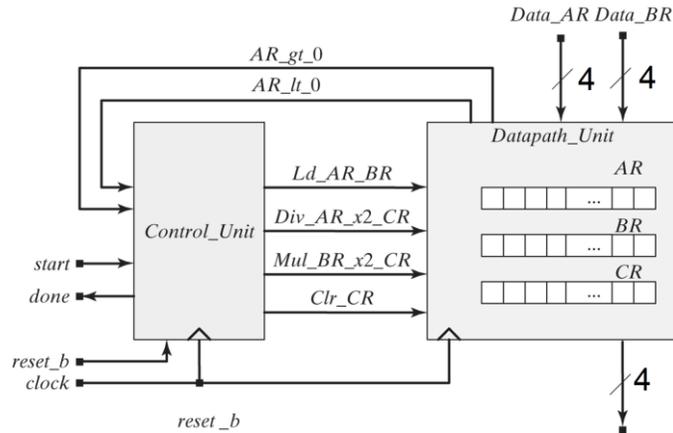


Design & Modeling of Digital Systems


HW# 3

Due date: Saturday, March 16

- Q.1.** The block diagram below shows the datapath and controller for a machine that transfers two 4-bit signed numbers in 2's complement representation into registers AR and BR, divides the number in AR by 2 and transfers the result to register CR if the number in AR is negative, multiplies the number in BR by 2 and transfers the result to register CR if the number in AR is positive but non-zero, and if the number in AR is zero, clears register CR to 0.



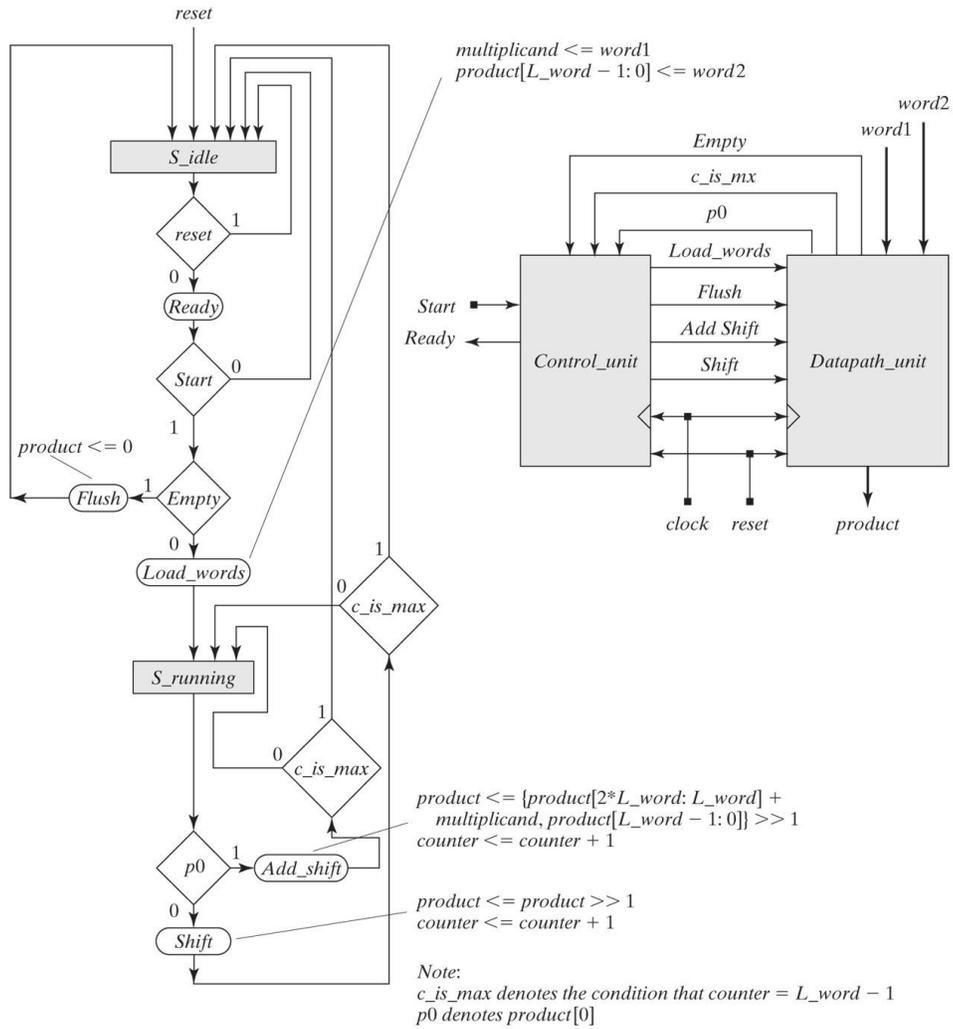- (i) Develop an ASMD chart for the machine.
 - (ii) Show the design of the data-path and control unit of the machine.
 - (iii) Implement the machine and verify its correct functionality by simulation.
- Q.2.** It is required to design an unsigned 4-bit sequential multiplier. The multiplier is assumed to have an 8-bit register to hold the result, a 4-bit register to hold the multiplicand and a 3-bit counter. When reset is 1, the multiplicand, the product and counter registers are reset. When operation is started, the multiplicand register is loaded with word1 while the least significant 4-bits of the product are loaded with word2. The block diagram and the ASMD chart of the sequential multiplier are given below. *Ready* signals that the unit is ready to accept a command to multiply. If word1 or word2 are 0, *Empty* is set to 1. *Flush* loads the product with 0. *C_is_mx* is set when the counter is equal to 3. *P0* is the least significant bit of the product i.e. product[0].



- (i) Show the design of the data-path and control unit of the 4-bit sequential multiplier.
- (ii) Implement the machine and verify its correct functionality by simulation.