


COE 405, Term 152

Design & Modeling of Digital Systems


HW# 4

Due date: Tuesday, March 22

 Q.1. An iterative design of a combinational circuit that computes the equation $Y=3*X-1$, where X is an n -bit signed 2's complement number is given below:



 - (i) Write a Verilog model to model the given 1-bit cell using primitive gates. Model the delay of AND and OR gates as 5ps, while the delay of XOR and XNOR gates as 8 ps.
- (ii) Write a Verilog model for modeling the circuit given below computing the equation $Y=3*X-1$ assuming X is a 4-bit number by instantiating 4 cells:



- (iii) Write a test bench to test the correctness of your Verilog model by applying the following input patterns $X_3X_2X_1X_0=\{0000, 0001, 0011, 0101, 1111, 1110\}$. Apply consecutive inputs patterns after a delay of 20ps.
- (iv) Determine the longest delay of your 4-bit circuit.
- (v) Write a test bench to verify the longest delay of your 4-bit circuit.

*This assignment can be solved based on a group of two students. The solution should be well organized. Submit a soft copy of your solution in a zip file including your Verilog models. Your solution should be submitted in a **word file** that contains the following items:*

- i. Your name and ID*
- ii. Assignment number*
- iii. Problem statement*
- iv. Your solution*
- v. Include snapshots of simulation output to illustrate the correctness of your models.*