


## COE 405, Term 152

### Design & Modeling of Digital Systems

#### HW# 7

Due date: Sunday, May 1

 **Q.1.** Consider the logic network below with inputs  $\{a, b, c, d, e\}$  and output  $\{k\}$ :



Assume that the delay of the inverter gate is 1 and that the delay of the 2-input NAND gate is 2. Also, assume that the input data-ready times are zero except for input  $a$ , which is equal to 2.

- (i) Compute the data ready times and slacks for all vertices in the network.
  - (ii) Determine the topological critical path.
  - (iii) Suggest an implementation of the function  $k$  using only inverters and 2-input NAND gates to reduce the delay of the circuit to the minimum possible and determine the maximum propagation delay in the optimized circuit. Has the area been affected?
- Q.2.** It is required to design a circuit to compute the equation  $Y=A+B-C-D$ , where  $A, B, C$  and  $D$  are  $N$ -bit inputs. Assume that inputs are available only during the first cycle when a **START** input is asserted. Assume that a **DONE** signal will be set when the result is ready and the result will remain held until the next Start operation.
- (i) Show a schedule of the operations with minimum latency (i.e., clock cycles) assuming that the clock cycle is limited by the time for performing one addition/subtraction operation. Store the output  $Y$  in a register.
  - (ii) Show the Data Path design of your circuit indicating all the control signals and the used adder/subtractor sizes.
  - (iii) Show the ASMD diagram of your control unit.

- (iv) Write the necessary Verilog modules to module the data path unit, control unit and the overall circuit.
- (v) Write a test bench to test the correct operation of your circuit. Include simulation snapshots.
- (vi) Implement your circuit on FPGA assuming  $N=2$  bits. Include a link for a video snapshot to demonstrate correct functionality of your circuit.

*This assignment can be solved based on a group of two students. The solution should be well organized. Submit a soft copy of your solution in a zip file including your Verilog models. Your solution should be submitted in a **word file** that contains the following items:*

- i. Your name and ID*
- ii. Assignment number*
- iii. Problem statement*
- iv. Your solution*
- v. Include snapshots of simulation output to illustrate the correctness of your models.