

Name:

Id#


COE 405, Term 031

Design & Modeling of Digital Systems

Quiz# 1

Date: Sunday, October 12, 2003

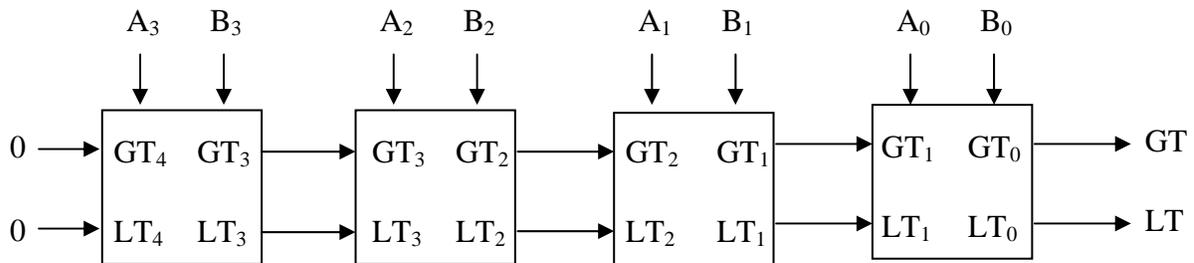Q.1. It is required to model a 4-bit comparator that compares two 4-bit numbers $A=A_3A_2A_1A_0$ and $B=B_3B_2B_1B_0$, and produces two outputs GT and LT. If $A>B$, then the output signal GT is set to 1 and LT is set to 0. If $A<B$, then the output signal LT is set to 1, and GT is set to 0. Otherwise both signals will be set to 0, which indicates that the two numbers are equal (i.e. $A=B$). The 4-bit comparator circuit can be designed in a modular way as shown below:



The equations for the 1-bit magnitude comparator can be found to be:

$$GT_i = GT_{i+1} + \overline{LT_{i+1}} A_i \overline{B_i}$$

$$LT_i = LT_{i+1} + \overline{GT_{i+1}} A_i B_i$$

- (i) Describe an Entity **COMP** for a 1-bit magnitude comparator.
- (ii) Model an Architecture **Comp** for this 1-bit COMP using concurrent statements.
- (iii) Describe an Entity **COMP4** for a 4-bit magnitude comparator.
- (iv) Model Architecture **Struct** for the 4-bit magnitude comparator (**COMP4**) using instantiations of the Entity **COMP**.