

Name:

Id#


COE 405, Term 152

Design & Modeling of Digital Systems

Quiz# 1

Date: Thursday, Feb. 11, 2016

 - Q.1.** Assume that the area and delay of a gate is related to the number of its inputs i.e., a 2-input AND gate has an area and delay = 2. Consider the given circuit below implementing the function F:



- (i) Determine the area and maximum delay of this circuit.
- (ii) Provide an implementation of this function with an improved delay and determine its area and maximum delay.
- Q.2.** Consider the function:  $F(A, B, C, D) = AB + \overline{A}BC + BCD + \overline{A}\overline{D}$
- (i) Compute the expansion of  $F$  using the **Orthonormal Basis**  $\{\phi_1 = \overline{A}\overline{B}, \phi_2 = \overline{A}B, \phi_3 = A\overline{B}, \phi_4 = AB\}$ .
- (ii) Compute the function  $\overline{F}$  utilizing the orthonormal based expansion of the function.

**Q.3.** It is required to design a combinational circuit that computes the equation  $Z=2X + Y - 1$ , where X and Y are n-bit signed 2's complement numbers.

- (i) Design the circuit as a modular iterative circuit where each module receives a single bit of the inputs,  $X_i$  and  $Y_i$ .
- (ii) Derive the truth table of your 1-bit module in (i).