


COE 405, Term 021

Design & Modeling of Digital Systems

Quiz# 1

Date: Monday, October 7, 2002

 - Q.1.** It is required to model a 4-bit adder/subtractor. The interface description of the 4-bit adder/subtractor is shown below, where **op** determines the operation. When $op=0$, the operation $A+B$ is performed, otherwise $A-B$ is performed.



- (i) Describe an Entity **FAS** for a 1-bit full adder/subtractor.
- (ii) Model an Architecture **Conc** for this 1-bit FAS using concurrent statements.
- (iii) Describe an Entity **AS4** for a 4-bit adder/subtractor using the interface names given above.
- (iv) Model Architecture **Struct** for the 4-bit adder/subtractor (**AS4**) using instantiations of the Entity **FAS**.

(i)

```
Entity FAS IS
    port (A, B, Cin, OP: IN BIT; Sum, Carry: OUT BIT);
END FAS;
```

(ii)

Architecture concurrent of FAS IS

signal t: BIT;

Begin

t <= b xor op;

sum <= a xor t xor cin;

carry <= (a and t) or (a and cin) or (t and cin);

End concurrent;

(iii)

Entity FAS4 IS

port (A, B: IN Bit_vector(3 downto 0); cin, op: IN bit;

sum: OUT bit_vector(3 downto 0); cout: OUT BIT);

End FAS4;

(iv)

Architecture structural of FAS4 IS

signal c0, c1, c2: bit;

component FAS

port (A, B, Cin, OP: IN BIT; Sum, Carry: OUT BIT);

End Component;

Begin

b0: FAS port map (A(0), b(0), cin, op, sum(0), c0);

b1: FAS port map (A(1), b(1), c0, op, sum(1), c1);

b2: FAS port map (A(2), b(2), c1, op, sum(2), c2);

b3: FAS port map (A(3), b(3), c2, op, sum(3), cout);

End structural;