


COE 405, Term 152

Design & Modeling of Digital Systems

Quiz# 1

Date: Thursday, Feb. 11, 2016

 - Q.1.** Assume that the area and delay of a gate is related to the number of its inputs i.e., a 2-input AND gate has an area and delay = 2. Consider the given circuit below implementing the function F:



- (i) Determine the area and maximum delay of this circuit.

Area = 8, Maximum Delay = 8

- (ii) Provide an implementation of this function with an improved delay and determine its area and maximum delay.

$F = E + D (C + A B) = E + D C + D A B$

Area = 8, Maximum Delay = 6

- Q.2.** Consider the function: $F(A, B, C, D) = AB + \overline{A}BC + BCD + \overline{A}\overline{D}$

- (i) Compute the expansion of F using the **Orthonormal Basis** $\{\emptyset_1 = \overline{A}\overline{B}, \emptyset_2 = \overline{A}B, \emptyset_3 = A\overline{B}, \emptyset_4 = AB\}$.


$F = A'B'(D') + A'B(C+D') + AB'(0) + AB(1)$

- (ii) Compute the function \overline{F} utilizing the orthonormal based expansion of the function.

$F' = A'B'(D) + A'B(C'D) + AB'(1) + AB(0)$
 $= A'B'D + A'B'C'D + AB' = A'B'D + A'C'D + AB'$

Q.3. It is required to design a combinational circuit that computes the equation $Z=2X + Y - 1$, where X and Y are n-bit signed 2's complement numbers.

 (i) Design the circuit as a modular iterative circuit where each module receives a single bit of the inputs, X_i and Y_i .



(ii) Derive the truth table of your 1-bit module in (i).

C_{1i-1}	C_{0i-1}	X_i	Y_i	C_{1i}	C_{0i}	Z_i
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	1
0	0	1	1	1	0	0
0	1	0	0	0	1	0
0	1	0	1	0	1	1
0	1	1	0	1	0	0
0	1	1	1	1	0	1
1	0	0	0	0	1	1
1	0	0	1	1	0	0
1	0	1	0	1	0	1
1	0	1	1	1	1	0
1	1	0	0	1	0	0
1	1	0	1	1	0	1
1	1	1	0	1	1	0
1	1	1	1	1	1	1