

Name:

Id#


COE 405, Term 131

Design & Modeling of Digital Systems


Quiz# 3

Date: Thursday, Nov. 28, 2013

 Q.1. It is required to model an n-bit iterative magnitude comparator. A 4-bit comparator is shown below:



 The model for a 1-bit comparator is as follows:



Write a parametrizable Verilog model for modeling an n-bit comparator with a default of n=4.

Q.2. The ASMD chart given below describes a state machine that counts 1's in a word and terminates activity as soon as possible. The machine remains in its reset state, S_idle , until an external agent asserts $start$. This action asserts the output, $load_temp$, which will cause $data$ to be loaded into register $temp$ when the state makes a transition to $S_counting$ at the next active edge of clk . The machine remains in $S_counting$ while $temp$ contains a 1. Two actions occur concurrently at each subsequent clock: (1) $temp$ is shifted towards its LSB and (2) $temp[0]$ is added to bit_count . When $temp$ finally has a 1 in only the LSB, the machine's state moves to $S_waiting$, where $done$ is asserted. The state remains in $S_waiting$ until $start$ is reasserted. Assume that when the synchronous $reset$ input is asserted the machine is reset to the state S_idle and bit_count and $temp$ are initialized to 0.

- (i) Write a Verilog model for modeling the data-path unit.
- (ii) Write a Verilog model for modeling the control unit using the following state assignment: $S_idle=00$, $S_counting=01$, and $S_waiting=10$.

