

Name:

Id#

COE 405, Term 181

Design & Modeling of Digital Systems

Quiz# 3

Date: Thursday, October 18, 2018

- Q.1.** Consider the given FSM that has 7 states, one input (X) and one output (Z), represented by the following state table:

Present State	Next State		Output (Z)	
	X=0	X=1	X=0	X=1
S0	S1	S2	1	0
S1	S3	S4	1	1
S2	S4	S6	0	0
S3	S5	S4	0	0
S4	S5	S1	1	1
S5	S3	S4	0	0
S6	S1	S2	0	0

- (i) Determine the equivalent states.
- (ii) Reduce the state table into minimum number of states and show the reduced state table.

Q.2. It is required to design a sequential circuit using Mealy model that computes the equation $Z=3*X-2*Y$, where X and Y are unsigned numbers that will be fed serially. Assume that the circuit has an asynchronous Reset input that resets the machine to the reset state. Draw the state diagram for your sequential circuit. Make sure that your state machine is minimal and that it does not have any redundant state.