


COE 405, Term 122

Design & Modeling of Digital Systems

Quiz# 4

Date: Monday, April 29, 2013

 Q.1. Consider the logic network below with inputs $\{a, b, c, d, e, f\}$ and output $\{X\}$:



Assume that the delay of a gate is related to the number of its inputs i.e. the delay of a 2-input AND gate is 2. Also, assume that the input data-ready times are zero for all inputs except input a , which has a data-ready time of 2.

- (i) Compute the data ready times and slacks for all vertices in the network.
- (ii) Determine the topological critical path.
- (iii) Suggest an implementation of the function X to reduce the delay of the circuit to the minimum possible and determine the maximum propagation delay in the optimized circuit. Has the area been affected?

(i)	Data Ready Time	Required Time	Slack
	$t_a = 2$	$\bar{t}_a = \min(4-2, 4-2) = 2$	$S_a = 2 - 2 = 0$
	$t_b = 0$	$\bar{t}_b = \min(4-2, 4-2) = 2$	$S_b = 2 - 0 = 2$
	$t_c = 0$	$\bar{t}_c = \min(4-2, 4-2) = 2$	$S_c = 2 - 0 = 2$
	$t_d = 0$	$\bar{t}_d = \min(4-2, 4-2) = 2$	$S_d = 2 - 0 = 2$
	$t_e = 0$	$\bar{t}_e = 8$	$S_e = 8 - 0 = 8$
	$t_f = 0$	$\bar{t}_f = 8$	$S_f = 8 - 0 = 8$
	$t_g = 4$	$\bar{t}_g = 4$	$S_g = 4 - 4 = 0$
	$t_h = 4$	$\bar{t}_h = 4$	$S_h = 4 - 4 = 0$
	$t_i = 2$	$\bar{t}_i = 4$	$S_i = 4 - 2 = 2$
	$t_j = 2$	$\bar{t}_j = 4$	$S_j = 4 - 2 = 2$
	$t_k = 8$	$\bar{t}_k = 8$	$S_k = 8 - 8 = 0$
	$t_x = 11$	$\bar{t}_x = 11$	$S_x = 11 - 11 = 0$

(ii) The topological critical paths are:


$\{a, g, k, x\}$ and $\{a, h, k, x\}$

(iii) To optimize the delay of the network, we need to improve the delay of nodes in the critical paths.

k can be factored into $(a+h)(c+d)$

Then, x can be implemented as

follows:

 


The resulting delay is 6.
 Number of literals is 10.


Thus, we have improved the delay
 from 11 to 6 and area from 15 literals
 to 10 literals.

Q.2. Determine possible circuits that will be synthesized by each of the following modules:

 
- (i) module m1 (output y, input e1, e2, x1, x2);
 assign y = e1?x1:e2?x2:y;
 endmodule



 - (ii) module m2 (output y, input e1, e2, x1, x2);
 assign y = e1?x1:e2?x2:1'bx;
 endmodule



 
- (iii) module m3 #(parameter size=2)(
 output reg y,
 input [size-1:0] a, b);
 integer k;
 always @ (a, b) begin
 for (k=size-1; k>=0; k=k-1) begin
 if (a[k] != b[k])
 y = 0;
 end
 end
 endmodule



```

(iv) module m4 #(parameter size=3)(
    output reg y,
    input [size-1:0] x );
    always @ (x) begin
        y = 0;
        if (x[0]) y=1;
        else if (x[1]) y=1;
        else if (x[2]) y=1;
    end
endmodule


```

 

```

(v) module m5 #(parameter size=3)(
    output reg y,
    input [size-1:0] x );
    integer k;
    always @ (x) begin
        y = 1;
        for (k=1; k<size; k=k+1)
            y = y & x[k];
        if (!x[0]) y = 1'bz;
    end
endmodule

```

 

```

(vi) module m6 (
    output reg y,
    input x1, x2, x3);
    always @ (x1, x2, x3) begin
        if (x1) y = x2 ^ x3;
    end
endmodule

```

