
VHDL Coding Styles for Synthesis

Dr. Aiman H. El-Maleh
Computer Engineering Department
King Fahd University of Petroleum & Minerals

Outline...

- **Synthesis overview**
- **Synthesis of primary VHDL constructs**
 - Constant definition
 - Port map statement
 - When statement
 - With statement
 - Case statement
 - For statement
 - Generate statement
 - If statement
 - Variable definition
- **Combinational circuit synthesis**
 - Multiplexor
 - Decoder
 - Priority encoder
 - Adder
 - Tri-state buffer
 - Bi-directional buffer

...Outline

- **Sequential circuit synthesis**
 - Latch
 - Flip-flop with asynchronous reset
 - Flip-flop with synchronous reset
 - Loadable register
 - Shift register
 - Register with tri-state output
 - Finite state machine
- **Efficient coding styles for synthesis**

11-3

General Overview of Synthesis...

- **Synthesis is the process of translating from an abstract description of a hardware device into an optimized, technology specific gate level implementation.**
- **Synthesis may occur at many different levels of abstraction**
 - Behavioral synthesis
 - Register Transfer Level (RTL) synthesis
 - Boolean equations descriptions, netlists, block diagrams, truth tables, state tables, etc.
- **RTL synthesis implements the register usage, the data flow, the control flow, and the machine states as defined by the syntax & semantics of the HDL.**

11-4

...General Overview of Synthesis

- **Forces driving the synthesis algorithm**
 - HDL coding style
 - Design constraints
 - Timing goals
 - Area goals
 - Power management goals
 - Design-For-Test rules
 - Target technology
 - Target library design rules
- **The HDL coding style used to describe the targeted device is technology independent.**
- **HDL coding style determines the initial starting point for the synthesis algorithms & plays a key role in generating the final synthesized hardware.**

11-5

VHDL Synthesis Subset

- **VHDL is a complex language but only a subset of it is synthesizable.**
- **Primary VHDL constructs used for synthesis:**
 - Constant definition
 - Port map statement
 - Signal assignment: $A \leq B$
 - Comparisons: = (equal), /= (not equal), > (greater than), < (less than), >= (greater than or equal), <= (less than or equal)
 - Logical operators: **AND, OR, NAND, NOR, XOR, XNOR, NOT**
 - 'if' statement
 - **if** (presentstate = CHECK_CAR) **then**
 - **end if** | **elsif**
 - 'for' statement (used for looping in creating arrays of elements)
 - Other constructs are '**with**', '**when**', '**when else**', '**case**', '**wait**'. Also ":= " for variable assignment.

11-6

Outline

- **Synthesis overview**
- **Synthesis of primary VHDL constructs**
 - Constant definition
 - Port map statement
 - When statement
 - With statement
 - Case statement
 - For statement
 - Generate statement
 - If statement
 - Variable definition
- **Combinational circuit synthesis**
 - Multiplexor
 - Decoder
 - Priority encoder
 - Adder
 - Tri-state buffer
 - Bi-directional buffer

11-7

Constant Definition...

```
library ieee;
use ieee.std_logic_1164.all;
entity constant_ex is
    port (in1 : in std_logic_vector (7 downto 0); out1 : out
          std_logic_vector (7 downto 0));
end constant_ex;
architecture constant_ex_a of constant_ex is
    constant A : std_logic_vector (7 downto 0) := "00000000";
    constant B : std_logic_vector (7 downto 0) := "11111111";
    constant C : std_logic_vector (7 downto 0) := "00001111";
begin
    out1 <= A when in1 = B else C;
end constant_ex_a;
```

11-8

...Port Map Statement...

```
library ieee;
use ieee.std_logic_1164.all;
entity portmap_ex is
    port (in1, in2, in3 : in std_logic; out1 : out std_logic);
end portmap_ex;
architecture portmap_ex_a of portmap_ex is
    component sub
        port (a, b : in std_logic; c : out std_logic);
    end component;
    signal temp : std_logic;
```


11-11

...Port Map Statement...

```
begin
    u0 : sub port map (in1, in2, temp);
    u1 : sub port map (temp, in3, out1);
end portmap_ex_a;
use work.all;
configuration portmap_ex_c of portmap_ex is
    for portmap_ex_a
        for u0,u1 : sub use entity work.sub (sub_a);
        end for;
    end for;
end portmap_ex_c;
```

11-12


Port Map Statement...

 

11-13

When Statement

 
```
library ieee;  
use ieee.std_logic_1164.all;  
entity when_ex is  
    port (in1, in2 : in std_logic; out1 : out std_logic);  
end when_ex;  
architecture when_ex_a of when_ex is  
begin  
    out1 <= '1' when in1 = '1' and in2 = '1' else '0';  
end when_ex_a;
```



11-14

With Statement
 
```
library ieee;
use ieee.std_logic_1164.all;
entity with_ex is
    port (in1, in2 : in std_logic; out1 : out std_logic);
end with_ex;
architecture with_ex_a of with_ex is
begin
    with in1 select out1 <= in2 when '1',
                    '0' when others;
end with_ex_a;
```




11-15

Case Statement...

```
library ieee;
use ieee.std_logic_1164.all;
entity case_ex is
    port (in1, in2 : in std_logic; out1,out2 : out std_logic);
end case_ex;
architecture case_ex_a of case_ex is
    signal b : std_logic_vector (1 downto 0);
begin
    process (b)
    begin
        case b is
            when "00"|"11" => out1 <= '0'; out2 <= '1';
            when others => out1 <= '1'; out2 <= '0';
        end case;
    end process;
    b <= in1 & in2;
end case_ex_a;
```

11-16

...Case Statement

 


11-17

For Statement...

```
library ieee;
use ieee.std_logic_1164.all;
entity for_ex is
    port (in1 : in std_logic_vector (3 downto 0); out1 : out
          std_logic_vector (3 downto 0));
end for_ex;
architecture for_ex_a of for_ex is
begin
    process (in1)
    begin
        for0 : for i in 0 to 3 loop
            out1 (i) <= not in1(i);
        end loop;
    end process;
end for_ex_a;
```

11-18

...For Statement

 

11-19


Generate Statement

```
signal A,B:BIT_VECTOR (3 downto 0);
signal C:BIT_VECTOR (7 downto 0);
signal X:BIT;
```

...

```
GEN_LABEL:
```

 
```
  for I in 3 downto 0 generate
    C(2*I+1) <= A(I) nor X;
    C(2*I) <= B(I) nor X;
  end generate GEN_LABEL
```



11-20

If Statement
 
```
library ieee;
use ieee.std_logic_1164.all;
entity if_ex is
  port (in1, in2 : in std_logic; out1 : out std_logic);
end if_ex;
architecture if_ex_a of if_ex is
begin
  process (in1, in2)
  begin
    if in1 = '1' and in2 = '1' then out1 <= '1';
    else out1 <= '0';
    end if;
  end process;
end if_ex_a;
```



11-21

Variable Definition...

```
library ieee;
use ieee.std_logic_1164.all;
entity variable_ex is
  port (a : in std_logic_vector (3 downto 0); b : in std_logic_vector
        (3 downto 0); c : out std_logic_vector (3 downto 0));
end variable_ex;
architecture variable_ex_a of variable_ex is
begin
  process (a,b)
    variable carry : std_logic_vector (4 downto 0);
    variable sum : std_logic_vector (3 downto 0);
```

11-22


Outline

- **Synthesis overview**
- **Synthesis of primary VHDL constructs**
 - Constant definition
 - Port map statement
 - When statement
 - With statement
 - Case statement
 - For statement
 - Generate statement
 - If statement
 - Variable definition
- **Combinational circuit synthesis**
 - Multiplexor
 - Decoder
 - Priority encoder
 - Adder
 - Tri-state buffer
 - Bi-directional buffer

11-25

Multiplexor Synthesis...

 
```
library ieee;
use ieee.std_logic_1164.all;
entity mux is
    port (in1, in2, ctrl : in std_logic; out1 : out std_logic);
end mux;
architecture mux_a of mux is
begin
    process (in1, in2, ctrl)
    begin
        if ctrl = '0' then out1 <= in1;
        else out1 <= in2;
        end if;
    end process;
end mux_a;
```



11-26

...Multiplexor Synthesis
 
```
entity mux2to1_8 is
  port ( signal s: in std_logic; signal zero,one: in std_logic_vector(7
        downto 0); signal y: out std_logic_vector(7 downto 0) );
end mux2to1_8;
architecture behavior of mux2to1_8 is
begin
  y <= one when (s = '1') else zero;
end behavior;
```



11-27

2x1 Multiplexor using Booleans

```
architecture boolean_mux of mux2to1_8 is
  signal temp: std_logic_vector(7 downto 0);
begin
  temp <= (others => s);
  y <= (temp and one) or (not temp and zero);
end boolean_mux;
```

- The *s* signal cannot be used in a Boolean operation with the *one* or *zero* signals because of type mismatch (*s* is a *std_logic* type, *one/zero* are *std_logic_vector* types)
- An internal signal of type *std_logic_vector* called *temp* is declared. The *temp* signal will be used in the Boolean operation against the *zero/one* signals.
- Every bit of *temp* is set equal to the *s* signal value.

11-28

2x1 Multiplexor using a Process

```
architecture process_mux of mux2to1_8 is
begin
  comb: process (s, zero, one)
  begin
    y <= zero;
    if (s = '1') then
      y <= one;
    end if;
  end process comb;
end process_mux ;
```

11-29


Decoder Synthesis...

```
library ieee;
use ieee.std_logic_1164.all;
entity decoder is
  port (in1, in2 : in std_logic; out00, out01, out10, out11 : out std_logic);
end decoder;
architecture decoder_a of decoder is
begin
  process (in1, in2)
  begin
    if in1 = '0' and in2 = '0' then out00 <= '1';
    else out00 <= '0';
    end if;
    if in1 = '0' and in2 = '1' then out01 <= '1';
    else out01 <= '0';
    end if;
```

11-30

...Decoder Synthesis
 
```
if in1 = '1' and in2 = '0' then out10 <= '1';
else out10 <= '0';
end if;
if in1 = '1' and in2 = '1' then out11 <= '1';
else out11 <= '0';
end if;
end process;
end decoder_a;
```



11-31

3-to-8 Decoder Example...

```
entity dec3to8 is
  port (signal sel: in std_logic_vector(2 downto 0); signal en: in std_logic;
        signal y: out std_logic_vector(7 downto 0));
end dec3to8;
architecture behavior of dec3to8 is
begin
  process (sel, en)
  Begin
    y <= "11111111";
    if (en = '1') then
      case sel is
        when "000" => y(0) <= '0';   when "001" => y(1) <= '0';
        when "010" => y(2) <= '0';   when "011" => y(3) <= '0';
        when "100" => y(4) <= '0';   when "101" => y(5) <= '0';
        when "110" => y(6) <= '0';   when "111" => y(7) <= '0';
        when others => Null;
      end case;
    end if;
  end process;
end behavior;
```


11-32

...3-to-8 Decoder Example...

```
entity dec3to8 is
    port (signal sel: in std_logic_vector(2 downto 0); signal en: in std_logic;      signal y: out
          std_logic_vector(7 downto 0));
end dec3to8;
architecture behavior of dec3to8v is
    signal t: std_logic_vector(7 downto 0);
begin
    process (sel, en)
    Begin
        t <= "00000000";
        if (en = '1') then
            case sel is
                when "000" => t(0) <= '1';   when "001" => t(1) <= '1';
                when "010" => t(2) <= '1';   when "011" => t(3) <= '1';
                when "100" => t(4) <= '1';   when "101" => t(5) <= '1';
                when "110" => t(6) <= '1';   when "111" => t(7) <= '1';
                When others => Null;
            end case;
        end if;
    end process;
    Y <= Not t;
end behavior;
```

11-35

3-to-8 Decoder Example...

 

11-36


Architecture of Generic Decoder

```
library ieee;
use ieee.std_logic_1164.all;
entity generic_decoder is
  Generic(K: Natural :=3);
  port (signal sel: in std_logic_vector(K-1 downto 0); signal en: in std_logic;
        signal y: out std_logic_vector(2**K-1 downto 0));
end generic_decoder;
architecture behavior of generic_decoder is
begin
  process (sel, en)
  begin
    y <= (others => '0');
    for i in y'range loop
      if ( en = '1' and Bin2Int(sel) = i ) then
        y(i) <= '1';
      end if ;
    end loop;
  end process;
end behavior;
```

Bin2Int is a function to convert
from **std_logic_vector** to **integer**

11-37

Architecture of Generic Decoder

 

11-38

A Common Error in Process Statements...

- When using processes, a common error is to forget to assign an output a default value.
 - ALL outputs should have DEFAULT values
- If there is a logical path in the model such that an output is not assigned any value
 - the synthesizer will assume that the output must retain its current value
 - a latch will be generated.
- Example: In *dec3to8.vhd* do not assign 'y' the default value of B"1111111"
 - If *en* is 0, then 'y' will not be assigned a value
 - In the new synthesized logic, all 'y' outputs are latched

11-39


...A Common Error in Process Statements...

```
entity dec3to8 is
  port (signal sel: in std_logic_vector(3 downto 0); signal en: in std_logic;
        signal y: out std_logic_vector(7 downto 0))
end dec3to8;
architecture behavior of dec3to8 is
begin
  process (sel, en)
    -- y <= "11111111";
    if (en = '1') then
      case sel is
        when "000" => y(0) <= '0';   when "001" => y(1) <= '0';
        when "010" => y(2) <= '0';   when "011" => y(3) <= '0';
        when "100" => y(4) <= '0';   when "101" => y(5) <= '0';
        when "110" => y(6) <= '0';   when "111" => y(7) <= '0';
      end case;
    end if;
  end process;
end behavior;
```

*No default value
assigned to y!!*

11-40

...A Common Error in Process Statements

 

11-41

Another Incorrect Latch Insertion Example...


```
entity case_example is
  port (in1, in2 : in std_logic; out1, out2 : out std_logic);
end case_example;
architecture case_latch of case_example is
  signal b : std_logic_vector (1 downto 0);
begin
  process (b)
  begin
    case b is
      when "01" => out1 <= '0'; out2 <= '1';
      when "10" => out1 <= '1'; out2 <= '0';
      when others => out1 <= '1';

    end case;
  end process;
  b <= in1 & in2;
end case_latch;
```

out2 has not been assigned a value for others condition!!

11-42

 ...Another Incorrect Latch Insertion Example



11-43

Avoiding Incorrect Latch Insertion

architecture case_nolatch of case_example is

 signal b : std_logic_vector (1 downto 0);

begin

 process (b)

 begin

 case b is

 when "01" => out1 <= '0'; out2 <= '1';

 when "10" => out1 <= '1'; out2 <= '0';


 when others => out1 <= '1'; out2 <= '0';

 end case;

 end process;

 b <= in1 & in2;

end case_nolatch;

 

11-44

Eight-Level Priority Encoder...

Entity priority is

```
Port (Signal y1, y2, y3, y4, y5, y6, y7: in std_logic;  
      Signal vec: out std_logic_vector(2 downto 0));
```

End priority;

Architecture behavior of priority is

Begin

```
Process(y1, y2, y3, y4, y5, y6, y7)
```

```
begin
```

```
  if (y7 = '1') then vec <= "111";      elsif (y6 = '1') then vec <= "110";
```

```
  elsif (y5 = '1') then vec <= "101";  elsif (y4 = '1') then vec <= "100";
```

```
  elsif (y3 = '1') then vec <= "011";  elsif (y2 = '1') then vec <= "010";
```

```
  elsif (y1 = '1') then vec <= "001";  else vec <= "000";
```


```
  end if;
```

```
end process;
```

End behavior;

11-45

...Eight-Level Priority Encoder...

 

11-46

Eight-Level Priority Encoder...

Architecture behavior2 of priority is

Begin

```
Process(y1, y2, y3, y4, y5, y6, y7)
```

```
begin
```

```
    vec <= "000";
```

```
    if (y1 = '1') then vec <= "001"; end if;
```

```
    if (y2 = '1') then vec <= "010"; end if;
```

```
    if (y3 = '1') then vec <= "011"; end if;
```

```
    if (y4 = '1') then vec <= "100"; end if;
```

```
    if (y5 = '1') then vec <= "101"; end if;
```

```
    if (y6 = '1') then vec <= "110"; end if;
```

```
    if (y7 = '1') then vec <= "111"; end if;
```

```
end process;
```

```
End behavior2;
```

*Equivalent 8-level
priority encoder.*

11-47

Ripple Carry Adder...

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity adder4 is
```

```
    port (Signal a, b: in std_logic_vector (3 downto 0);
```

```
          Signal cin : in std_logic;
```

```
          Signal sum: out std_logic_vector (3 downto 0);
```

```
          Signal cout : out std_logic);
```

```
end adder4;
```

```
architecture behavior of adder4 is
```

```
Signal c: std_logic_vector (4 downto 0);
```

```
begin
```

*C is a temporary signal
to hold the carries.*

11-48


...Ripple Carry Adder...

```
process (a, b, cin, c)
begin
  c(0) <= cin;
  for I in 0 to 3 loop
    sum(I) <= a(I) xor b(I) xor c(I);
    c(I+1) <= (a(I) and b(I)) or (c(I) and (a(I) or b(I)));
  end loop;
end process;
cout <= c(4);
End behavior;
```

- The Standard Logic 1164 package does not define arithmetic operators for the `std_logic` type.
- Most vendors supply some sort of arithmetic package for 1164 data types.
- Some vendors also support synthesis using the '+' operation between two `std_logic` signal types (Synopsis).

11-49


...Ripple Carry Adder

 

11-50

Tri-State Buffer Synthesis

 
```
library ieee;  
use ieee.std_logic_1164.all;  
entity tri_ex is  
    port (in1, control : in std_logic; out1 : out std_logic);  
end tri_ex;  
architecture tri_ex_a of tri_ex is  
begin  
    out1 <= in1 when control = '1' else 'Z';  
end tri_ex_a;
```



11-51

Bi-directional Buffer Synthesis
 
```
library ieee;  
use ieee.std_logic_1164.all;  
entity inout_ex is  
    port (io1, io2 : inout std_logic; ctrl : in std_logic);  
end inout_ex;  
architecture inout_ex_a of inout_ex is  
begin  
    io1 <= io2 when ctrl = '1' else 'Z';  
    io2 <= io1 when ctrl = '0' else 'Z';  
end inout_ex_a;
```



11-52


Outline

- **Sequential circuit synthesis**
 - Latch
 - Flip-flop with asynchronous reset
 - Flip-flop with synchronous reset
 - Loadable register
 - Shift register
 - Register with tri-state output
 - Finite state machine
- **Efficient coding styles for synthesis**

11-53

Sequential Circuits

 - **Sequential circuits consist of both combinational logic and storage elements.**
- **Sequential circuits can be**
 - *Moore*-type: outputs are a combinatorial function of Present State signals.
 - *Mealy*-type: outputs are a combinatorial function of both Present State signals and primary inputs.



11-54

Template Model for a Sequential Circuit

```
entity model_name is
  port ( list of inputs and outputs );
end model_name;
architecture behavior of model_name is
  internal signal declarations
begin
  -- the state process defines the storage elements
  state: process ( sensitivity list -- clock, reset, next_state inputs )
  begin
    vhdl statements for state elements
  end process state;
  -- the comb process defines the combinational logic
  comb: process ( sensitivity list -- usually includes all inputs )
  begin
    vhdl statements which specify combinational logic
  end process comb;
end behavior;
```


11-55

Latch Synthesis...

```
library ieee;
use ieee.std_logic_1164.all;
entity latch_ex is
  port (clock, in1 : in std_logic; out1 : out std_logic);
end latch_ex;
architecture latch_ex_a of latch_ex is
begin
  process (clock, in1)
  begin
    if (clock = '1') then
      out1 <= in1;
    end if;
  end process;
end latch_ex_a;
```

11-56

...Latch Synthesis

 

11-57


Flip-Flop Synthesis with Asynchronous Reset...

```
library ieee;
use ieee.std_logic_1164.all;
entity dff_asyn is
    port( reset, clock, d: in std_logic; q: out std_logic);
end dff_asyn;
architecture dff_asyn_a of dff_asyn is
begin
    process (reset, clock)
    begin
        if (reset = '1') then
            q <= '0';
        elsif clock = '1' and clock'event then
            q <= d;
        end if;
    end process;
end dff_asyn_a;
```

•Note that the reset input has precedence over the clock in order to define the asynchronous operation.

11-58

 ...Flip-Flop Synthesis with Asynchronous Reset




11-59

Flip-Flop Synthesis with Synchronous Reset...

```
library ieee;
use ieee.std_logic_1164.all;
entity dff_syn is
    port( reset, clock, d: in std_logic; q: out std_logic);
end dff_syn;
architecture dff_syn_a of dff_syn is
begin
    process (clock)
    begin
        if clock = '1' and clock'event then
            if (reset = '1') then q <= '0';
            else q <= d;
            end if;
        end if;
    end process;
end dff_syn_a;
```

11-60

 ...Flip-Flop Synthesis with Synchronous Reset



11-61

8-bit Loadable Register with Asynchronous Clear...

```
library ieee;
use ieee.std_logic_1164.all;
entity reg8bit is
    port( reset, clock, load: in std_logic;
          din: in std_logic_vector(7 downto 0);
          dout: out std_logic_vector(7 downto 0));
end reg8bit;
architecture behavior of reg8bit is
    signal n_state, p_state: std_logic_vector(7 downto 0);
begin
    dout <= p_state;
    comb: process (p_state, load, din)
    begin
        n_state <= p_state;
        if (load = '1') then n_state <= din; end if;
    end process comb;
end architecture;
```


11-62

...8-bit Loadable Register with Asynchronous Clear...

```

state: process (clock , reset)
begin
  if (reset = '0') then p_state <= (others => '0');
  elsif (clock = '1' and clock'event) then
    p_state <= n_state;
  end if;
end process state;
End behavior;


```

 

- The state process defines a storage element which is 8-bits wide, rising edge triggered, and had a low true asynchronous reset.
- Note that the reset input has precedence over the clock in order to define the asynchronous operation.

11-63

 ...8-bit Loadable Register with Asynchronous Clear



11-64

4-bit Shift Register...

```
library ieee;
use ieee.std_logic_1164.all;
entity shift4 is
    port( reset, clock: in std_logic;  din: in std_logic;
          dout: out std_logic_vector(3 downto 0));
end shift4;
architecture behavior of shift4 is
    signal n_state, p_state: std_logic_vector(3 downto 0);
begin
    dout <= p_state;
    state: process (clock, reset)
    begin
        if (reset = '0') then  p_state <= (others => '0');
        elsif (clock = '1' and clock'event) then
            p_state <= n_state;
        end if;
    end process state;
```

11-65


...4-bit Shift Register...

```
    comb: process (p_state, din)
    begin
        n_state(0) <= din;
        for l in 3 downto 1 loop
            n_state(l) <= p_state(l-1);
        end loop;
    end process comb;
End behavior;
```

- Serial input *din* is assigned to the D-input of the first D-FF.
- For loop is used to connect the output of previous flip-flop to the input of current flip-flop.

11-66

...4-bit Shift Register

 

11-67

Register with Tri-State Output...

```

library ieee;
use ieee.std_logic_1164.all;
entity tsreg8bit is
    port( reset, clock, load, en: in std_logic;
          signal din: in std_logic_vector(7 downto 0);
          signal dout: out std_logic_vector(7 downto 0));
end tsreg8bit;
architecture behavior of tsreg8bit is
    signal n_state, p_state: std_logic_vector(7 downto 0);
begin
    dout <= p_state when (en='1') else "ZZZZZZZZ";
    comb: process (p_state, load, din)
    begin
        n_state <= p_state;
        if (load = '1') then n_state <= din; end if;
    end process comb;


```

• Z assignment used to specify tri-state capability.

11-68

...Register with Tri-State Output...

 
```
state: process (clock , reset)
begin
    if (reset = '0') then p_state <= (others => '0');
    elsif (clock = '1' and clock'event) then
        p_state <= n_state;
    end if;
end process state;
End behavior;
```



11-69


...Register with Tri-State Output

 Modified for ITC student library (no longer a 40131 device, but I guess it's still compatible)



11-70

Finite State Machine Synthesis...

 

11-71

...Finite State Machine Synthesis...

```
library ieee;
use ieee.std_logic_1164.all;
entity state_ex is
    port (in1, clock, reset : in std_logic; out1 :
          out std_logic_vector (1 downto 0));
end state_ex;
architecture state_ex_a of state_ex is
    signal cur_state, next_state : std_logic_vector (1 downto 0);
begin
    process (clock, reset)
    begin
        if clock = '1' and clock'event then
            if reset = '0' then cur_state <= "00";
            else cur_state <= next_state;
            end if;
        end if;
    end process;
```


11-72

...Finite State Machine Synthesis...

```
process (in1, cur_state)
begin
  case cur_state is
    when "00" => if in1 = '0' then next_state <= "10"; out1 <= "00";
                  else next_state <= "01"; out1 <= "10";
                  end if;
    when "01" => if in1 = '0' then next_state <= cur_state;
                  out1 <= "01";
                  else next_state <= "10 "; out1 <= "10";
                  end if;
    when "10" => next_state <= "11"; out1 <= "10";
    when "11" => next_state <= "00"; out1 <= "10";
    when others => null;
  end case;
end process;
end state_ex_a;
```

11-73

...Finite State Machine Synthesis

 

11-74

Outline

- **Sequential circuit synthesis**
 - Latch
 - Flip-flop with asynchronous reset
 - Flip-flop with synchronous reset
 - Loadable register
 - Shift register
 - Register with tri-state output
 - Finite state machine
- **Efficient coding styles for synthesis**

11-75

Key Synthesis Facts

- **Synthesis ignores the after clause in signal assignment**
 - `C <= A AND B` after 10ns
 - May cause mismatch between pre-synthesis and post-synthesis simulation if a non-zero value used
 - The preferred coding style is to write signal assignments without the after clause.
- **If the process has a static sensitivity list, it is ignored by the synthesis tool.**
- **Sensitivity list must contain all read signals**
 - Synthesis tool will generate a warning if this condition is not satisfied
 - Results in mismatch between pre-synthesis and post-synthesis simulation


11-76

Synthesis Static Sensitivity Rule

Original VHDL Code

```
Process(A, B)
Begin
  D <= (A AND B) OR C;
End process;
```


Pre-Synthesis Simulation

 

Synthesis View of Original VHDL Code

```
Process(A, B, C)
Begin
  D <= (A AND B) OR C;
End process;
```

Post-Synthesis Simulation

 

11-77

Impact of Coding Style on Synthesis Execution Time

Inefficient Synthesis Execution Time

```
Process(Sel, A, B, C, D)
Begin
  if Sel = "00" then Out <= A;
  elsif Sel = "01" then Out <= B;
  elsif Sel = "10" then Out <= C;
  else Out <= D;
  endif;
End process;
```

Efficient Synthesis Execution Time

```
Process(Sel, A, B, C, D)
Begin
  case Sel is
    when "00" => Out <= A;
    when "01" Out <= B;
    when "10" Out <= C;
    when "11" Out <= D;
  end case;
End process;
```

- Synthesis tool is capable of deducing that the if ...elsif conditions are mutually exclusive but precious CPU time is required.
- In case statement, when conditions are mutually exclusive.

11-78

Synthesis Efficiency Via Vector Operations

Inefficient Synthesis Execution Time

```
Process(Scalar_A, Vector_B)
Begin
  for k in Vector_B`Range loop
    Vector_C(k) <=Vector_B(k) and
      Scalar_A;
  end loop;
End process;
```

Efficient Synthesis Execution Time

```
Process(Scalar_A, Vector_B)
  variable Temp:
    std_logic_vector(Vector_B`Range)
  ;
Begin
  Temp := (others => Scalar_A);
  Vector_C <=Vector_B and Temp;
End process;
```

- Loop will be unrolled and analyzed by the synthesis tool.
- Vector operation is understood by synthesis and will be efficiently synthesized.

11-79

Three-State Synthesis

- A three-state driver signal must be declared as an object of type `std_logic`.
- Assignment of 'Z' infers the usage of three-state drivers.
- The `std_logic_1164` resolution function, resolved, is synthesized into a three-state driver.
- Synthesis does not check for or resolve possible data collisions on a synthesized three-state bus
 - It is the designer responsibility
- Only one three-state driver is synthesized per signal per process.

11-80

Example of the Three-State / Signal / Process Rule

```
Process(B, Use_B, A, Use_A)
```

```
Begin
```

```
  D_Out <= 'Z';
```

```
  if Use_B = '1' then
```

```
    D_Out <= B;
```


```
  end if;
```

```
  if Use_A = '1' then
```

```
    D_Out <= A;
```

```
  end if;
```

```
End process;
```

 

• Last scheduled assignment has priority

11-81

Latch Inference & Synthesis Rules...

- A latch is inferred to satisfy the VHDL fact that signals and process declared variables maintain their values until assigned new ones.
- Latches are synthesized from if statements if all the following conditions are satisfied
 - Conditional expressions are not completely specified
 - An else clause is omitted
 - Objects conditionally assigned in an if statement are not assigned a value before entering this if statement
 - The VHDL attribute `EVENT is not present in the conditional if expression.
- If latches are not desired, then a value must be assigned to the target object under all conditions of an if statement (without the `EVENT attribute).

11-82

...Latch Inference & Synthesis Rules


- **For a case statement, latches are synthesized when it satisfies all of the following conditions:**
 - An expression is not assigned to a VHDL object in every branch of a case statement,
 - VHDL objects assigned an expression in any case branch are not assigned a value before the case statement is entered.
- **Latches are synthesized whenever a for...loop statement satisfies all of the following conditions**
 - for...loop contains a next statement
 - Objects assigned inside the for...loop are not assigned a value before entering the enclosing for...loop

11-83

For...Loop Statement Latch Example

```
Process(Data_In, Copy_Enable)
Begin
  for k in 7 downto 0 loop
    next when Copy_Enable(k)='0';
    Data_Out(k) <= Data_in(k);
  end loop;
End process;
```

Seven latches will be synthesized

 

11-84

Flip-Flop Inference & Synthesis Rules...

- **Flip-flops are inferred by either**
 - Wait until....
 - Wait on... is not supported by synthesis
 - Wait for... is not supported by synthesis
 - If statement containing `EVENT
- **Synthesis accepts any of the following functionally equivalent statements for inferring a FF**
 - Wait until Clock='1';
 - Wait until Clock`Event and Clock='1';
 - Wait until (not Clock`Stable) and Clock='1';

11-85

...Flip-Flop Inference & Synthesis Rules

- **Synthesis does not support the following Asynchronous description of set and reset signals**
 - Wait until (clock='1') or (Reset='1')
 - Wait on Clock, Reset
- **When using a synthesizable wait statement only synchronous set and reset can be used.**
- **If statement containing the VHDL attribute `EVENT cannot have an else or an elsif clause.**

11-86

Alternative Coding Styles for Synchronous FSMs

- **One process only**
 - Handles both state transitions and outputs
- **Two processes**
 - A synchronous process for updating the state register
 - A combinational process for conditionally deriving the next machine state and updating the outputs
- **Three processes**
 - A synchronous process for updating the state register
 - A combinational process for conditionally deriving the next machine state
 - A combinational process for conditionally deriving the outputs