

King Fahd University of Petroleum & Minerals Computer Engineering Dept

**COE 202 – Fundamentals of Computer
Engineering**

Term 081

Dr. Ashraf S. Hasan Mahmoud

Rm 22-148-3

Ext. 1724

Email: ashraf@kfupm.edu.sa


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

1

Sequential Circuit

- Definition

 


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

2

Storage Elements

 - Storage can be constructed logic with delay, such as a buffer by connecting the output to the input. The signal must not undergo inversion in the loop or the system will be unstable or *astable*
- Positive Feedback – stability issues and dependence on propagation delay.




1/11/2009

Dr. Ashraf S. Hasan Mahmoud

3

Synchronous Circuits

- Asynchronous: input changes at any time may result in the any of the outputs or internally stored information (called state) to change.
 - Such circuits are difficult to design because of dependence on propagation delays and their interaction with timing of input changes.
- Synchronous: sequential makes use of clock signals so that the storage elements (and outputs) only change at discrete instants of time in relation to the clock signal.
 - Clocked synchronous circuits provide some degree of independence on timing variations related to gate propagation delays.

 


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

4

SR Latch

- Definition: A storage element that maintains binary state indefinitely (as long as power is applied), until directed by an input signal to switch to its other state
- Has two inputs: S and R, and two outputs: Q and Q'
- Notes:
 - S=1, R=0 → set state (i.e. Q = 1, and Q' = 0)
 - S=0, R=1 → reset state (i.e. Q = 0, and Q' = 1)
 - S=0, R=0 → keep state (i.e. new Q = old Q, new Q' = old Q')
 - S=1, R=1 → undefined

 

S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1
1	1	0	0

(a) Logic diagram

(b) Function table



1/11/2009

Dr. Ashraf S. Hasan Mahmoud

5

SR Latch – Timing Diagram and Stability

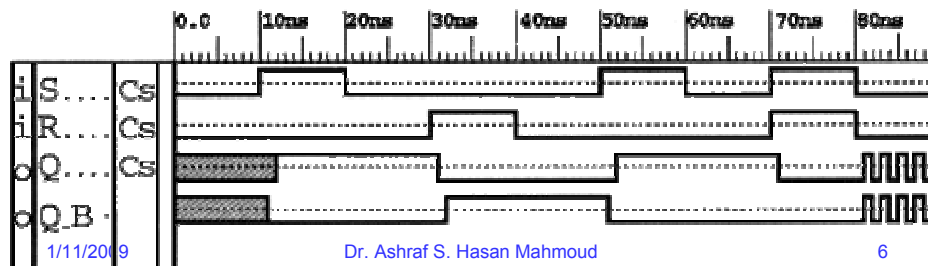 - Note: the outputs are NOW a function of time as well as the inputs
- Stability issue: When SR latch in the undefined state 00 and then both S and R are simultaneously changed to 00 – oscillations appear!!
 - What is the period of the oscillations?




1/11/2009

Dr. Ashraf S. Hasan Mahmoud

6

SR Latch – NAND Gates Implementation

 - Very similar to the NOR gates implementation
- Notes:
 - $S=0, R=1 \rightarrow$ set state (i.e. $Q = 1$, and $Q' = 0$)
 - $S=1, R=0 \rightarrow$ reset state (i.e. $Q = 0$, and $Q' = 1$)
 - $S=1, R=1 \rightarrow$ keep state (i.e. new $Q =$ old Q , new $Q' =$ old Q')
 - $S=0, R=0 \rightarrow$ undefined



S	R	Q	Q'	
0	1	1	0	Set state
1	1	1	0	
1	0	0	1	Reset state
1	1	0	1	
0	0	1	1	Undefined


1/11/2009

(a) Logic diagram Hasan Mahmoud

 (b) Function table

SR Latch with Gating

- The inputs S and R are not always visible to the latch
 - Depending on the value of C
- Control signal C
- When enabled (i.e. $C = 1$):
 - You can write a 0 to Q by $S=0, R=1$
 - You can write a 1 to Q by $S=1, R=0$
 - You can keep the state by $S=0, R=0$
- It is still possible to drive the latch into the undefined state!!



C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; Set state
1	1	1	Undefined

SR latch with control input


1/11/2009

(a) Logic diagram Hasan Mahmoud

 (b) Function table 8

Gated D-Latch

- With this controlled input D-Latch it is NOT possible to drive it into the invalid state
 - Both inputs CAN NOT be active at the same time
- When enabled (i.e. $C = 1$):
 - You can write a 0 to Q by $D=0$
 - You can write a 1 to Q by $D=1$



C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

(b) Function table

9

Flip-Flops

- Problems with previous latches:
 - When C is enabled – the latch is in *transparent* mode. i.e. changes in S and R will be reflected in changes to its state – so it is still possible to drive the SR latch into the undefined state and then to instability.
- Solutions:
 - Master-Slave flip-flop
 - Edge-triggered flip-flop


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

10

Master-Slave Flip-Flop

 - Master-Slave FF: two SR latches connected as shown in figure.
- How is the transparency problem solved?
- Is the undefined state problem solved?
- Pulse-triggered flip-flop:
 - It can respond to input during the clock pulse
- You should be able to reproduce the timing diagram




1/11/2009

Dr. Ashraf S. Hasan Mahmoud

11

Master-Slave JK Flip-Flop

 - How is the transparency problem solved?
- Is the undefined state problem solved?
- Yes, it is impossible to drive the latches into the undefined state
 - The SR inputs to the first latch can never be both 1s at the same time.
- Note this flip-flop can
 - Keep the state ($J=0, K=0$),
 - Go into reset state ($J=0, K=1$),
 - Go into set state ($J=1, K=0$), and
 - Invert the state ($J=1, K=1$)



J	K	Next State of Q	
0	0	Q	Keep state
0	1	0	Reset state
1	0	1	Set state
1	1	\bar{Q}	Invert state

(b) Functional Table of JK Flip-Flop


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

12

Edge-Triggered Flip-Flop

 - This flip-flop responds only to the rising (+ve) edge of the clock or to the falling (-ve) edge of the clock signal.
- Can you generate the timing diagram for a given input D signal?




1/11/2009

Dr. Ashraf S. Hasan Mahmoud

13

Positive Edge Triggered JK Flip-Flop

 


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

14

Timing Issues - Again

- Propagation Delay: times it takes for an input to appear at the output is called the propagation delay.
 - t_{PHL} : time it takes for an input to cause the output to change from logic-level-high to logic-level-low.
 - t_{PLH} : delay associated when an input change causes the output to change from logic-level-low to logic-level-high.
- The overall propagation delay is average of t_{PHL} and t_{PLH}

 


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

15

Timing Issues - Again

 - Setup Time (T_s): a constant duration for which the inputs must be held prior to the arrival of the clock transition
- Hold Time (T_h): refers to the duration for which the inputs must not change after the arrival of the transition



If the setup and hold times are violated, a gate may produce an unknown logic signal at its output. This condition is called as *meta-stability*.


1/11/2009

Dr. Ashraf S. Hasan Mahmoud


16

Standard Graphics Symbols


- (a) Latch Symbols

 

- (b) Master-Slave Flip-Flops

 

- (c) Edge-Triggered Flip-Flops

 


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

17

Asynchronous Inputs

- Special inputs for setting or resetting them asynchronously
 - Independent of the clock input
- The *direct set* and *direct reset* signals are called *preset* and *clear*, respectively
- Examining the function table:
 - When $S=0, R=1$, the FF is set regardless of the clock and the JK inputs
 - When $S=1, R=0$, the FF is reset regardless of the clock and the JK inputs
 - For the JK to operate normally, S and R should be 1 and 1.

 

(a) Graphic symbols

S	R	C	J	K	Q	\bar{Q}
0	1	X	X	X	1	0
1	0	X	X	X	0	1
0	0	X	X	X	Undefined	
1	1	↑	0	0	No change	
1	1	↑	0	1	0	1
1	1	↑	1	0	1	0
1	1	↑	1	1	Complement	

(b) Function table

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

18

Flip-Flop Characteristic Tables

Table 6-7

(a) JK Flip-Flop				(b) SR Flip-Flop			
J	K	Q(t+1)	Operation	S	R	Q(t+1)	Operation
0	0	Q(t)	No change	0	0	Q(t)	No change
0	1	0	Reset	0	1	0	Reset
1	0	1	Set	1	0	1	Set
1	1	Q'(t)	Complement	1	1	?	Undefined

(c) D Flip-Flop			(d) T Flip-Flop		
D	Q(t+1)	Operation	T	Q(t+1)	Operation
0	0	Reset	0	Q(t)	No change
1	1	Set	1	Q'(t)	Complement

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

19

JK Flip-Flop Characteristic Equation

- Using table on previous slide, one can write:

	00	01	11	10
0	0	1	0	0
1	1	1	0	1

J	K	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q(t+1) = J\overline{Q(t)} + \overline{K}Q(t)$$

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

20

SR Flip-Flop Characteristic Equation

- Using table on slide 19, one can write:

RQ(t)	00	01	11	10
S				
0	0	1	0	0
1	1	1	X	X

S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

$$Q(t+1) = S + \bar{R}Q(t)$$

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

21

D Flip-Flop Characteristic Equation

- Using table slide 19, one can write:

$$Q(t+1) = D$$

D	Q(t)	Q(t+1)
0	0	0
0	1	0
1	0	1
1	1	1

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

22

T Flip-Flop Characteristic Equation

- Using table on slide 19, one can write:

$$Q(t+1) = T \oplus Q(t)$$

T	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0


Flip-Flop Excitation Tables

Table 6-7

(a) JK Flip-Flop				(b) SR Flip-Flop			
Q(t)	Q(t+1)	J	K	Q(t)	Q(t+1)	S	R
0	0	0	X	0	0	0	X
0	1	1	X	0	1	1	0
1	0	X	1	1	0	0	1
1	1	X	0	1	1	X	0

(c) D Flip-Flop			(d) T Flip-Flop		
Q(t)	Q(t+1)	D	Q(t)	Q(t+1)	T
0	0	0	0	0	0
0	1	1	0	1	1
1	0	0	1	0	1
1	1	1	1	1	0

State Machine Design

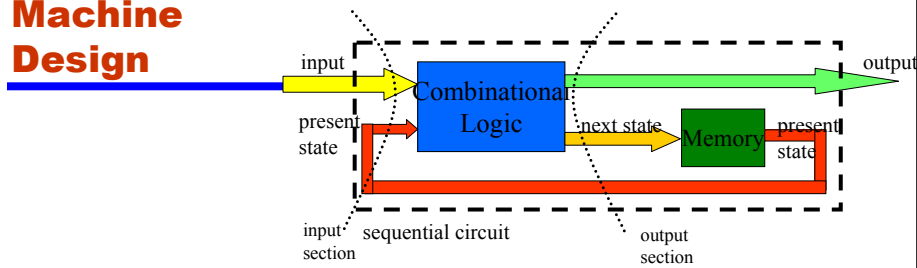

Present State		Input	Output	Next State		Flip-Flop Inputs			
A	B	X	Y	A	B	J_A	K_A	J_B	K_B
0	0	0	1	0	1	0	X	1	X
0	0	1	0	0	0	0	X	0	X
0	1	0	1	1	1	1	X	X	0
0	1	1	1	1	0	1	X	X	1
1	0	0	1	1	1	X	0	1	X
1	0	1	0	1	0	X	0	0	X
1	1	0	0	0	0	X	1	X	1
1	1	1	1	1	1	X	0	X	0

1/1

input section

output section – derived from problem specification or state diagram

derived from excitation table of the particular flip-flop we use as memory

25

Example

- **Problem:**
 - Write characteristic equations for each type of flip-flops, using the information in Table 6-7. A characteristic equation gives the function $Q(t+1)$ in terms of $Q(t)$ and the input variables to the flip-flop.
 - Use the characteristic equation for the JK flip-flop to find equations $A(t+1)$ and $B(t+1)$ from the flip-flop input equations corresponding to Table shown on next slide.
- **Solution:**
 - Refer to previous slides for the development of characteristic equations

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

26

Example – cont'd

• Solution (cont'd):

b)

- The columns J_A, K_A (for flip flop A) and J_B, K_B (for flip flop B) are obtained with the aid of the excitation table
- To obtain the equations for J_A, K_A, J_B and K_B we do K-maps in terms of the inputs

Present State		Input	Next State		Flip-Flop Inputs			
A	B	X	A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	X	1	X
0	0	1	0	0	0	X	0	X
0	1	0	1	1	1	X	X	0
0	1	1	1	0	1	X	X	1
1	0	0	1	1	X	0	1	X
1	0	1	1	0	X	0	0	X
1	1	0	0	0	X	1	X	1
1	1	1	1	1	X	0	X	0

This is input

This is derived from problem specification or state diagram

This is derived from excitation table of the particular flip-flop

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

27

Example – cont'd

• Solution (cont'd):

b) From the K-maps

$$J_A = B(t),$$

$$K_A = B(t)X',$$

while

$$J_B = X',$$

$$K_B = A(t)X' + A'(t)X$$

Present State		Input	Next State		Flip-Flop Inputs			
A	B	X	A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	X	1	X
0	0	1	0	0	0	X	0	X
0	1	0	1	1	1	X	X	0
0	1	1	1	0	1	X	X	1
1	0	0	1	1	X	0	1	X
1	0	1	1	0	X	0	0	X
1	1	0	0	0	X	1	X	1
1	1	1	1	1	X	0	X	0

This is input

This is derived from problem specification or state diagram

This is derived from excitation table of the particular flip-flop

BX \ A	00	01	11	10
0	0	0	1	1
1	X	X	X	X

K-map for J_A

BX \ A	00	01	11	10
0	X	X	X	X
1	0	0	0	1

K-map for K_A

BX \ A	00	01	11	10
0	1	0	X	X
1	1	0	X	X

K-map for J_B

BX \ A	00	01	11	10
0	X	X	1	0
1	X	X	0	1

K-map for K_B

1/11/2009

Dr. Ashraf S. H:

28

Example – cont'd

- **Solution (cont'd):**

b) Finally, Using the characteristic equation for the A JK flip-flop:

$$A(t+1) = J_A A(t)' + K_A A(t) \rightarrow$$

$$\begin{aligned} A(t+1) &= B(t)A(t)' + (B(t)X)'A(t) \\ &= B(t)A(t)' + B(t)'A(t) + XA(t) \end{aligned}$$

- Same for the B JK flip-flop:

$$B(t+1) = J_B B(t)' + K_B B(t) \rightarrow$$

$$B(t+1) = X'B(t)' + (A(t)X' + A'(t)X)B(t)$$

$$B(t+1) = X'B(t)' + A(t)B(t)X + A'(t)B(t)X'$$

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

29

Sequence Recognizer


- **Problem:** Design a circuit to recognize the occurrence of the bits 1101 (input from left to right) on an input line X by making an output signal Z equal to 1; Otherwise Z is equal to 0

- **Solution:**

Sequential circuit with one input X and one output Z

- Examples of operation:

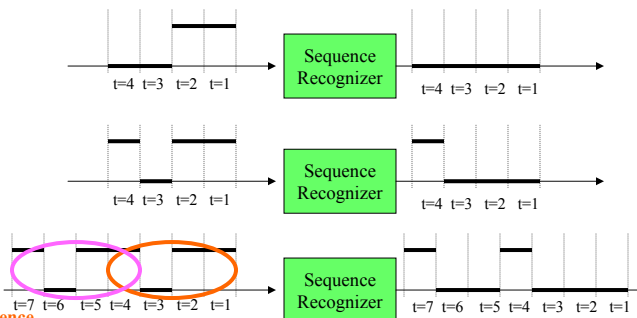1. No sequence – Z remains zero
2. sequence occurs – Z is one
3. Two overlapping sequences – Z is one twice!



1/11/2009

1st sequence
2nd sequence Dr. Ashraf S. Hasan Mahmoud

30

Sequence Recognizer – State Diagram

- Solution (cont'd):**

You always start from an initial state → State S_0


To remember first '1' of sequence → State S_1

To remember two consecutive 1s of sequence → State S_2

To remember '110' sequence → State S_3

Note an arrival of S_1 while in state S_3 should make the output $Z = 1$, and move to state S_0 to remember this '1' which could be the first digit of another 1101 sequence

Arc label: X/Z

 



1/11/2009

Dr. Ashraf S. Hasan Mahmoud

31

Sequence Recognizer – State Table

- Solution (cont'd):**

  

Present State	Next State		Output Z	
	X = 0	X = 1	X = 0	X = 1
S_0	S_0	S_1	0	0
S_1	S_0	S_2	0	0
S_2	S_3	S_2	0	0
S_3	S_0	S_1	0	1

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

32


Sequence Recognizer – State Table (2)

• **Solution (cont'd):**

Present State	Next State		Output Z	
	X = 0	X = 1	X = 0	X = 1
S ₀	S ₀	S ₁	0	0
S ₁	S ₀	S ₂	0	0
S ₂	S ₃	S ₂	0	0
S ₃	S ₀	S ₁	0	1

State Code Assignment (Grey Coding):

S₀ → 00
 S₁ → 01
 S₂ → 11
 S₃ → 10

 

Present State	Next State		Output Z	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	00	11	0	0
11	10	11	0	0
10	00	01	0	1

1/11/2009

Dr. Ashraf S. Hasan Mahmoud


33

Sequence Recognizer – State Table (3)

• **Solution (cont'd):**

Present State	Next State		Output Z	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	00	11	0	0
11	10	11	0	0
10	00	01	0	1

 -Another way of writing the state table
 - Four states → we need two flip-flops A & B
 (in general if number of states is n, then we require log₂n flip-flops)



Present State		Input X	Next State		Output Z
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	0
1	1	1	1	1	0

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

34

Sequence Recognizer – Design Using D Flip-Flops

• **Solution (cont'd):**

Present State			Next State			Output
A	B	X	A	B	Z	
0	0	0	0	0	0	
0	0	1	0	1	0	
0	1	0	0	0	0	
0	1	1	1	1	0	
1	0	0	0	0	0	
1	0	1	0	1	1	
1	1	0	1	0	0	
1	1	1	1	1	0	

(c) D Flip-Flop

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1



-The characteristic equation for the D flip-flop is $Q(t+1) = D$
 → The D input is the same as the desired next state

Present State			Next State			Output	D Flip-Flops Input	
A	B	X	A	B	Z	D _A	D _B	
0	0	0	0	0	0	0	0	
0	0	1	0	1	0	0	1	
0	1	0	0	0	0	0	0	
0	1	1	1	1	0	1	1	
1	0	0	0	0	0	0	0	
1	0	1	0	1	1	0	1	
1	1	0	1	0	0	1	0	
1	1	1	1	1	0	1	1	

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

35

Sequence Recognizer – Design Using D Flip-Flops (2)

• **Solution (cont'd):**

Present State			Next State			Output	D Flip-Flops Input	
A	B	X	A	B	Z	D _A	D _B	
0	0	0	0	0	0	0	0	
0	0	1	0	1	0	0	1	
0	1	0	0	0	0	0	0	
0	1	1	1	1	0	1	1	
1	0	0	0	0	0	0	0	
1	0	1	0	1	1	0	1	
1	1	0	1	0	0	1	0	
1	1	1	1	1	0	1	1	



-Use K-maps to get D_A and D_B in terms of the states A and B and the input X
 -Use K-map to get Z in terms of states A and B and the input X

BX	00	01	11	10	
A					
0	0	0	1	0	D _A = AB + BX
1	0	0	1	1	

BX	00	01	11	10	
A					
0	0	1	1	0	D _B = X
1	0	1	1	0	

BX	00	01	11	10	
A					
0	0	0	0	0	Z = AB'X
1	0	1	0	0	

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

36


Sequence Recognizer – Design Using D Flip-Flops (3)

- Solution (cont'd):**

$$D_A = AB + BX$$

$$D_B = X$$

$$Z = AB'X$$

 


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

37

Let's Check Our Design – Timing Diagram

 

Machine STATES:

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

38

Let's Check Our Design – Timing Diagram – cont'd

• Important Notes

- The value of the input prior to the positive edge is the value used to generate the rest of the outputs
 - In other words, the input signal is sampled at the positive-edge instant minus epsilon – these samples constitute the input signal X
- Positive-edge triggered FFs respond to the input existing prior to the positive edge of the clock – and their output (state) lasts till the next positive edge at least
- The combination logic (AND gate for this example) for producing Z responds to instantaneously to signals at the input of this combination logic – regardless of the clock signal

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

39

Sequence Recognizer – Design Using JK Flip-Flops

• Solution (cont'd):

-Use the excitation table for the JK flip-flop
-To fill the J/K entries for each flip-flop

Present State			Input			Next State			Output		
A	B	X	A	B	Z	A	B	Z	A	B	Z
0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1	0	0	1	0
0	1	0	0	0	0	0	0	0	0	0	0
0	1	1	1	1	0	1	1	0	1	1	0
1	0	0	0	0	0	0	0	0	0	0	0
1	0	1	0	1	1	0	1	1	0	1	1
1	1	0	1	0	0	1	0	0	1	0	0
1	1	1	1	1	0	1	1	0	1	1	0

(a) JK Flip-Flop

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0



Present State			Input			Next State			JK Flip-Flop Input		JK Flip-Flop Input	
A	B	X	A	B	Z	A	B	Z	J _A	K _A	J _B	K _B
0	0	0	0	0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	0	1	0	0	X	1	X
0	1	0	0	0	0	0	0	0	0	X	X	1
0	1	1	1	1	0	1	1	0	1	X	X	0
1	0	0	0	0	0	0	0	0	X	1	0	X
1	0	1	0	1	1	0	1	1	X	1	1	X
1	1	0	1	0	0	1	0	0	X	0	X	1
1	1	1	1	1	0	1	1	0	X	0	X	0

1/11/2009

Dr. Ashraf S. Hasan Mahmoud





40

Sequence Recognizer – Design Using JK Flip-Flops (2)

• Solution (cont'd):

Present State			Input			Next State			Output		JK Flip-Flop Input	
A	B	X	A	B	Z	J_A	K_A	J_B	K_B			
0	0	0	0	0	0	0	X	0	X			
0	0	1	0	1	0	0	X	1	X			
0	1	0	0	0	0	0	X	X	1			
0	1	1	1	1	0	1	X	X	0			
1	0	0	0	0	0	X	1	0	X			
1	0	1	0	1	1	X	1	1	X			
1	1	0	1	0	0	X	0	X	1			
1	1	1	1	1	0	X	0	X	0			

    -Use K-maps to get D_A and D_B in terms of the states A and B and the input X
 -Use K-map to get Z in terms of states A and B and the input X



1/11/2009

Dr. Ashraf S. Hasan Mahmoud

41


Sequence Recognizer – Design Using JK Flip-Flops (3)

• Solution (cont'd):

$$J_A = BX \quad K_A = B'$$

$$J_B = X \quad K_B = X'$$

$$Z = AB'X$$

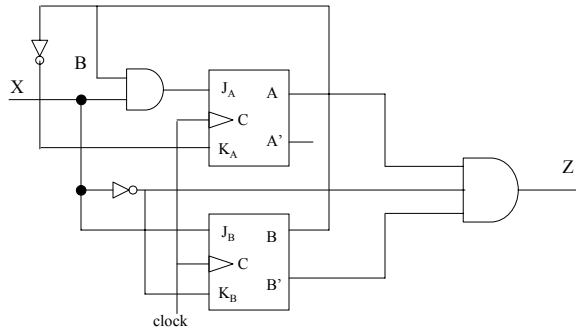


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

42

Mealy and Moore Type Finite State Machines

 - Mealy Machine:
 - In a Mealy machine, the outputs are a function of the present state and the value of the inputs as shown in figure.
 - The outputs may change asynchronously in response to any change in the inputs.




1/11/2009

Dr. Ashraf S. Hasan Mahmoud

43

Mealy and Moore Type Finite State Machines – cont'd

- Moore Machine:
 - In a Moore machine the outputs depend only on the present state as shown in figure.
 - A combinational logic block maps the inputs and the current state into the necessary flip-flop inputs to store the appropriate next state just like Mealy machine.
 - However, the outputs are computed by a combinational logic block whose inputs are only the flip-flops state outputs.
 - The outputs change synchronously with the state transition triggered by the active clock edge

 

1/11/2009


Dr. Ashraf S. Hasan Mahmoud

44

Sequence Recognizer – Mealy Machine Example

- Problem: Design a sequence recognizer (state machine) that outputs '1' if the input is '1' for three consecutive clocks – Use MEALY DESIGN – using D flip-flops
- Solution: State diagram is as shown
State table is as shown

Arc label: X/Z

 

Present State		Input	Next State		Output	D Flip-Flops Input	
A	B	X	A	B	Z	D _A	D _B
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	0	0	0	0	0
0	1	1	1	0	0	1	0
1	0	0	0	0	0	0	0
1	0	1	1	0	1	1	0

1/11/2009


Dr. Ashraf S. Hasan Mahmoud

45

Sequence Recognizer – Mealy Machine Example – cont'd

- Solution: The D flip-flops inputs are:

Present State		Input	Next State		Output	D Flip-Flops Input	
A	B	X	A	B	Z	D _A	D _B
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	1
0	1	0	0	0	0	0	0
0	1	1	1	0	0	1	0
1	0	0	0	0	0	0	0
1	0	1	1	0	1	1	0

 

BX \ A	00	01	11	10
0	0	0	1	0
1	0	1	x	x

$$D_A = AX + BX$$

BX \ A	00	01	11	10
0	0	1	0	0
1	0	0	x	x


$$D_B = A'B'X$$

BX \ A	00	01	11	10
0	0	0	0	0
1	0	1	x	x

$$Z = AX$$



 Notice we chose to use D flip-flops that respond on -ve clock edge




1/11/2009

46

Sequence Recognizer – Mealy Machine Example – cont'd

- Solution: Timing Diagram

 


$$D_A = AX + BX$$

$$D_B = A'B'X$$

$$Z = AX$$

False output (or output glitch)
 → This is a problem

1/11/2009

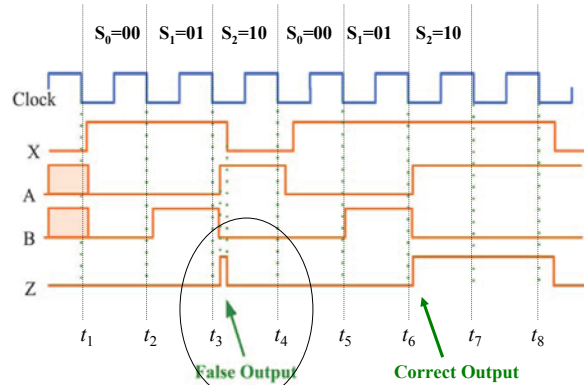

Sequence Recognizer – Moore Machine Example

- Problem: Design a sequence recognizer (state machine) that outputs '1' if the input is '1' for three consecutive clocks – Use MOORE DESIGN – using D flip-flops

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

48


Sequence Recognizer – Moore Machine Example – cont'd

- Solution – State diagram is as shown
- Observations:
 - States: are of the form AB/Z where Z is the output
 - Arc format: X where X is the input
- States codes:
 - $S_0 = 00, S_1 = 01, S_2 = 10, S_3 = 11$

	Present State		Input	Next State		Output	D Flip-Flops Input	
	A	B		A	B		D_A	D_B
S_0	0	0	0	0	0	0	0	0
	0	0	1	0	1	0	0	1
S_1	0	1	0	0	0	0	0	0
	0	1	1	1	0	0	1	0
S_2	1	0	0	0	0	0	0	0
	1	0	1	1	1	0	1	1
S_3	1	1	0	0	0	1	0	0
	1	1	1	1	1	1	1	1

1/11/2009

Function of present state ONLY

 

49

Sequence Recognizer – Moore Machine Example – cont'd

- Solution:

	Present State		Input	Next State		Output	D Flip-Flops Input	
	A	B		A	B		D_A	D_B
0	0	0	0	0	0	0	0	0
	0	0	1	0	1	0	0	1
0	0	1	0	0	0	0	0	0
	0	1	1	1	0	0	1	0
1	0	0	0	0	0	0	0	0
	1	0	1	1	1	0	1	1
1	1	0	0	0	0	1	0	0
	1	1	1	1	1	1	1	1

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

BX	00	01	11	10
A	0	0	1	0
0	0	0	1	0
1	0	1	1	0

$$D_A = AX + BX$$

BX	00	01	11	10
A	0	1	0	0
0	0	1	0	0
1	0	1	1	0

$$D_B = B'X + AX$$

B	0	1
A	0	0
0	0	0
1	0	1

$$Z = AB$$

50


Sequence Recognizer – Moore Machine Example – cont'd

- Solution: circuit

$$D_A = AX + BX$$

$$D_B = B'X + AX$$

$$Z = AB$$

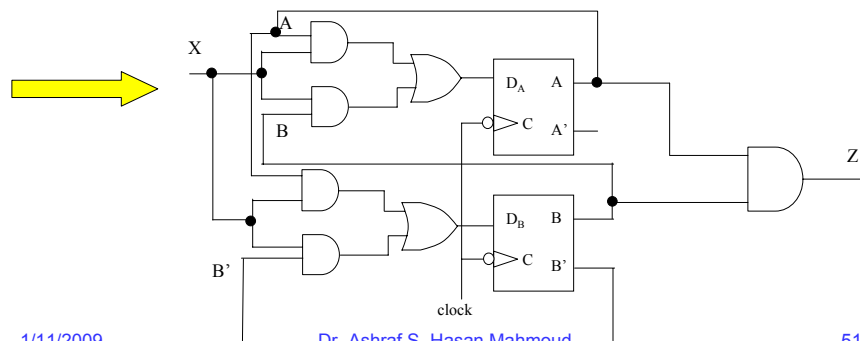

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

51


Sequence Recognizer – Moore Machine Example – cont'd

- Solution: Timing Diagram

$$D_A = AX + BX$$

$$D_B = B'X + AX$$

$$Z = AB$$

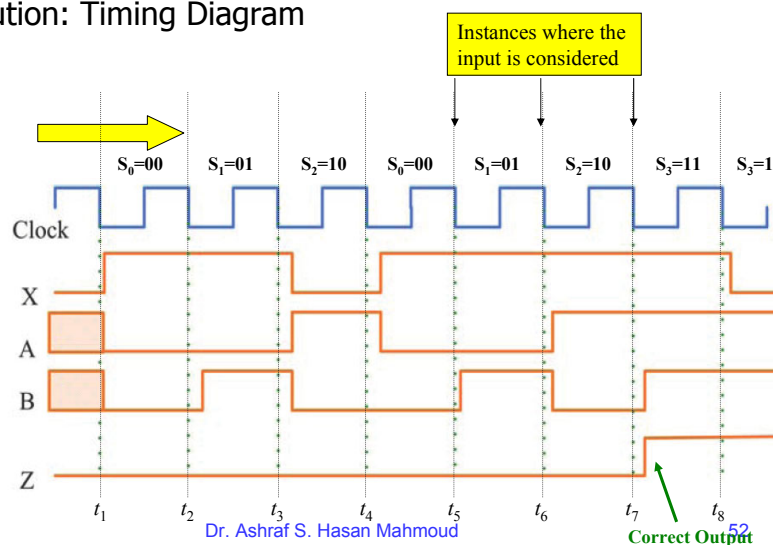

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

Correct Output 52

Serial Two's Complementer – Problem 6-15

- Problem:** A serial two's complementer is to be designed. A binary integer of arbitrary length is presented to the serial two's complementer least significant bit first on input X. When a given bit is presented on input X, the corresponding output bit is to appear during the same clock cycle on output Z. To indicate that a sequence is complete and that the circuit is to be initialized to receive another sequence, input Y becomes 1 for one clock cycle. Otherwise, Y is 0
 - Find the state diagram for the serial two's complementer
 - Find the state table for the serial two's complementer
 - Design the circuit using *D* flip-flops
 - Design the circuit using *JK* flip-flops

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

53

Serial Two's Complementer – Problem 6-15

- Solution:**


Remember to complement $A_n A_{n-1} \dots A_1 A_0$, we scanned the binary digits from LSB to MSB, skipping all zeros and passing the first 1 bit. All subsequent bits are complemented. The result is the two's complement of $A_n A_{n-1} \dots A_1 A_0$

Example: 2's complement of (10110100) is equal to (01001100)

Example: 2's complement of (0011) is equal to (1101)

Example: 2's complement of (000) is equal to (000)

 Example: 2's complement of (10) is equal to (10)



1/11/2009

Dr. Ashraf S. Hasan Mahmoud

54

Serial Two's Complementer – Problem 6-15 – State Diagram

- Solution (cont'd):**

Two inputs X: the binary bits in serial

Y: indicator when number is complete


Scanning the binary number, we switch between two modes:

copying binary digits till first 1 is found

inverting subsequent bits

Hence TWO states are needed – need to remember that we passed the one

 Because we have four inputs, each state has FOUR departing arcs



1/11/2009

Dr. Ashraf S. Hasan Mahmoud

55

Serial Two's Complementer – Problem 6-15 – State Diagram (2)

- Solution (cont'd):**

State S_0 : initial state (copying X to Z without inverting bits)


1. if zero arrives (input patterns 00 or 01) on X it is copied to Z –

2. if one arrives (input pattern 11) on X it is also copied to Z if Y is 1 (i.e last bit of number)

 3. if one arrives and it is not last bit (input pattern 10) then it is copied to Z but circuit moves to the other state – to start complementing bits

State S_1 : (copying X to Z while inverting bits) till Y = 1

when Y = 1, another number is about to start – move to initial state S_0



1/11/2009

Dr. Ashraf S. Hasan Mahmoud


56

Serial Two's Complementer – Problem 6-15 – State Table

- Solution (cont'd):**

2 States → need one flip-flop

Let $S_0 = 0$, while $S_1 = 1$

 

Present State	Inputs		Next State	Output
	Q(t)	X Y		
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	0	1
1	0	0	1	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	0

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

57

Serial Two's Complementer – Problem 6-15 – Implementation Using D Flip-Flops

- Solution (cont'd):**

Present State	Inputs		Next State	Output	D-Flip-Flop Input
Q(t)	X	Y	Q(t+1)	Z	D_0
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	1	1	1
0	1	1	0	1	0
1	0	0	1	1	1
1	0	1	0	1	0
1	1	0	1	0	1
1	1	1	0	0	0

(c) D Flip-Flop

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

XY	00	01	11	10
Q(t)	0	0	0	1
Q(t)	1	1	0	1

$$D_0 = QY' + XY'$$

XY	00	01	11	10
Q(t)	0	0	1	1
Q(t)	1	1	0	0

$$Z = Q'X + QX'$$

1/11/2009

Dr. Ashraf S. Hasan Mahmoud


58

Serial Two's Complementer – Problem 6-15 – Implementation Using D Flip-Flops (2)

- Solution (cont'd):**

$$D_Q = QY' + XY'$$

$$Z = Q'X + QX'$$

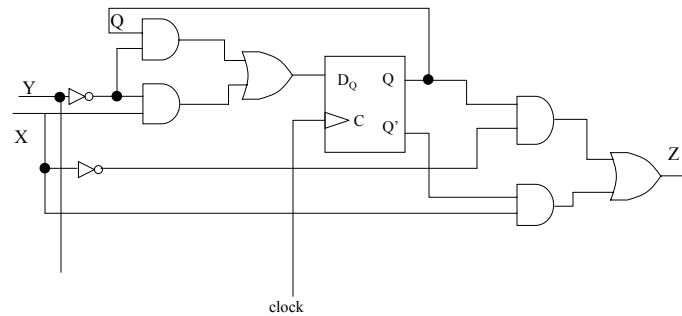


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

59

 Let's Check Our Design – Timing Diagram For Serial Complementer



1/11/2009

Dr. Ashraf S. Hasan Mahmoud

60

Serial Two's Complementer – Problem 6-15 – Implementation Using JK Flip-Flops

• **Solution (cont'd):**

Present State	Inputs		Next State	Output	JK-Flip-Flop Input	
Q(t)	X	Y	Q(t+1)	Z	J _Q	K _Q
0	0	0	0	0	0	X
0	0	1	0	0	0	X
0	1	0	1	1	1	X
0	1	1	0	1	0	X
1	0	0	1	1	X	0
1	0	1	0	1	X	1
1	1	0	1	0	X	0
1	1	1	0	0	X	1

(a) JK Flip-Flop

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

XY	00	01	11	10
Q(t)	0	0	0	1
1	x	x	x	x

$$J_Q = XY'$$

XY	00	01	11	10
Q(t)	x	x	x	x
1	0	1	1	0

$$K_Q = Y$$

XY	00	01	11	10
Q(t)	0	0	1	1
1	1	1	0	0

$$Z = Q'X + QX'$$

61


Serial Two's Complementer – Problem 6-15 – Implementation Using JK Flip-Flops (2)

• **Solution (cont'd):**

$$J_Q = XY'$$

$$K_Q = Y$$

$$Z = Q'X + QX'$$

 

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

62

More Examples: Problem 6-14

- Problem:** Design a sequential circuit with two D flip-flops A and B and one input X. When $X = 0$, the state of the circuit remains the same. When $X = 1$, the circuit goes through the state transitions 00 to 10 to 11 to 01, and back to 00, and then repeats.


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

63

Problem 6 -14 – State Diagram / Table

- Solution:**

 

BX	00	01	11	10
A	0	1	0	0
1	1	1	0	1

$D_A = AX' + B'X$

BX	00	01	11	10
A	0	0	0	1
1	0	1	1	1

$D_B = AX + BX'$

Present State		Input	Next State	
A	B	X	A	B
0	0	0	0	0
0	0	1	1	0
0	1	0	0	1
0	1	1	0	0
1	0	0	1	0
1	0	1	1	1
1	1	0	1	1
1	1	1	0	1

Note that the output in this case is the states AB

1/11/2009

Dr. Ashraf S. Hasan Mahmoud


64

Problem 6-14 – Circuit Implementation

- Solution:**

$$D_A = AX' + B'X$$

$$D_B = AX + BX'$$

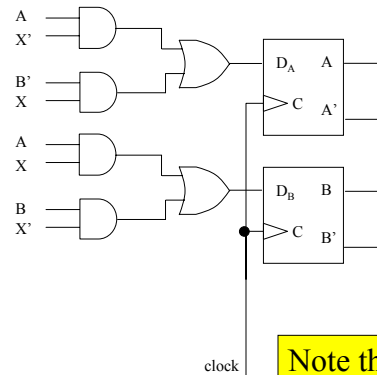

Note that the output in this case is the states AB

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

65

Another Example: Problem 6-5

- Problem:** A sequential circuit with two D flip-flops A and B, two inputs X and Y, and one output Z is specified by the following input equations:

$$D_A = X'Y + XA; D_B = X'B + XA; Z = XB$$

- Draw the logic diagram of the circuit
- Derive the state table
- Derive the state diagram

This is NOT a design problem – should be much easier than the ones presented earlier!


1/11/2009

Dr. Ashraf S. Hasan Mahmoud


66

Problem 6-5:

- Solution:**

 

Present State		Inputs		Next State		Output
A	B	X	Y	A	B	Z
0	0	0	0	0	0	0
0	0	0	1	1	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	1	0
0	1	0	1	1	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	0
1	0	1	1	1	1	0
1	1	0	0	0	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

 

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

67

Yet Another Example: Up/Down Counter with Enable

- Problem:** Design a sequential circuit with two JK flip-flops A and B and two inputs X and E. If $E = 0$, the circuit remains in the same state, regardless of the input X. When $E = 1$ and $X = 1$, the circuit goes through the state transitions from 00 to 01 to 10 to 11, back to 00, and then repeats. When $E = 1$ and $X = 0$, the circuit goes through the state transitions from 00 to 11 to 10 to 01, back to 00 and then repeats.


1/11/2009

Dr. Ashraf S. Hasan Mahmoud

68

Example: State Diagram/Table

• **Solution:**

 

Arc Label: EX

(a) JK Flip-Flop

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Present State		Inputs		Next State		FF Inputs			
A	B	E	X	A	B	J _A	K _A	J _B	K _B
0	0	0	0	0	0	0	X	0	X
0	0	0	1	0	0	0	X	0	X
0	0	1	0	1	1	1	X	1	X
0	0	1	1	0	1	0	X	1	X
0	1	0	0	0	1	0	X	X	0
0	1	0	1	0	1	0	X	X	0
0	1	1	0	0	0	0	X	X	1
0	1	1	1	1	0	1	X	X	1
1	0	0	0	1	0	X	0	0	X
1	0	0	1	1	0	X	0	0	X
1	0	1	0	0	1	X	1	1	X
1	0	1	1	1	1	X	0	1	X
1	1	0	0	1	1	X	0	X	0
1	1	0	1	1	1	X	0	X	0
1	1	1	0	1	0	X	0	X	1
1	1	1	1	0	0	X	1	X	1

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

69

Example – Logic Circuit

• **Solution:**

EX	AB	00	01	11	10
00	00	0	0	0	1
00	01	0	0	1	0
00	11	x	x	x	x
00	10	x	x	x	x

$J_A = BEX + B'EX'$

EX	AB	00	01	11	10
00	00	x	x	x	x
00	01	x	x	x	x
00	11	0	0	1	0
00	10	0	0	0	1


$K_A = BEX + B'EX'$

EX	AB	00	01	11	10
00	00	0	0	1	1
00	01	x	x	x	x
00	11	x	x	x	x
00	10	0	0	1	1

$J_B = E$

EX	AB	00	01	11	10
00	00	x	x	x	x
00	01	0	0	1	1
00	11	0	0	1	1
00	10	x	x	x	X

$K_B = E$

 

1/11/2009

Dr. Ashraf S. Hasan Mahmoud

70

Recommended Set of Problems

- **Problems Of INTEREST:**

- Problems with "s" are solved in this slides package