

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
COLLEGE OF COMPUTER SCIENCES & ENGINEERING

COMPUTER ENGINEERING DEPARTMENT

COE-202 – Fundamentals of Computer Engineering

January 13th, 2009 – Major Exam #2

Student Name:

Student Number:

Exam Time: 90 mins

- Do not open the exam book until instructed
- The use of programmable calculators and cell phone calculators is not allowed – only basic calculators are permitted
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

Question No.	Max Points	
1	50	
2	40	
3	50	
4	30	

Total: 170

Q.1) (50 points) Mark the following statements with either TRUE (T) or FALSE (F)


1	The XOR gate is a universal gate since it can implement all basic (AND, OR, NOT) operations.	F
2	A priority encoder has a valid line which indicates whether the output is valid or not.	T
3	Two 2-to-4 line decoders with enable signals can be connected to form a 4-to-16 line decoder.	F
4	A quadruple 4-to-1 line multiplexer has four select lines (S3, S2, S1, S0) select lines and one output line.	F
5	The partial adder circuit is a circuit that adds two bits and generate the sum and carry.	F
6	The decoder circuit has n inputs and 2^n outputs.	T
7	The ripple carry adder is built using n parallel half adders with all input bits applied simultaneously to produce the sum.	F
8	The logic diagram of the demultiplexer is identical to that of the decoder with the enable signal.	T
9	An 8-to-1 multiplexer can be used to implement any function of 4 variables with no added logic gates except perhaps for inverters.	T
10	An 2-to-1 multiplexer can be used to implement any function of 3 variables with no added logic gates except perhaps for inverters.	F
11	The 2^n -to-1 multiplexer can be used to implement n logic functions with the use of n external OR gates	F
12	The adder logic circuit can be also used to perform 2's complement subtraction	T
13	The carry lookahead adder does not suffer from extended delay to generate the required carry signals unlike the ripple carry adder	T
14	The clocked SR latch is an edge sensitive device.	F
15	The JK flip flop is a memory element that can store two bits.	F
16	For a NOR SR latch, the input 00 and the SR lines lead to an undefined state.	F
17	The master-slave flip-flop consists of two latches connected in series and an inverter.	T

18	A 4-to-16 decoder can be connected to a 16-to-4 encoder to perform BCD to excess-three code conversion without the need for external logic gates.	T
19	A clocked SR latch can not go into the undefined state.	F
20	A positive edge triggered flip-flop means the flip-flop changes state while the clock signal is positive.	F
21	Flip-flops often provide means to set or reset the flip-flop asynchronously regardless of its inputs.	T
22	The average propagation delay for a device is the average of T_{setup} and T_{hold} .	F
23	The setup time for a flip-flop is the minimum time required for the input to maintain its level (0 or 1) after the application of the clock transition of the pulse.	F
24	A 3-to-8 line decoder can be used to implement all possible functions of 1, 2, or 3 variables.	T
25	The characteristic equation for a D flip-flop is given by $Q(t+1) = D$.	T

Q.2) (40 points) Choose the most appropriate answer for the following questions:

1. The logic circuit shown represents most closely the architecture of a

 - a. **Simple Latch**
- b. SR Latch with Enable
- c. D Latch with Enable
- d. D Flip-Flop
- e. JK Flip-Flop



2. Which of the following will correctly complete the JK flip-flop truth table shown below?


					J	K	Q _n	Q _{n+1}						
					-----			-----						
a.	0	b.	0	c.	0	d.	0	e.	1	0	0	0		?
	1		1		0		0		1	0	1	1		?
	1		0		1		1		0	1	0	1		?
	0		0		1		0		1	1	1	1		?

3. Which of the following will correctly complete the D flip-flop truth table shown below?

					D	Q _n	Q _{n+1}						
					-----		-----						
a.	1	b.	1	c.	0	d.	0	e.	0	0	0		?
	1		1		0		0		1	0	1		?
	1		0		0		1		1	1	0		?
	1		1		1		1		0	1	1		?

4. An 8-line to 1-line multiplexer is connected as shown, where output Y = F(x,y,z) and z is the least significant input. Which of the following functions does Y generate?

 - a) **$F(x,y,z) = z$**
- b) $F(x,y,z) = y$
- c) $F(x,y,z) = z'$
- d) $F(x,y,z) = x$
- e) $F(x,y,z) = x + y'$




5. Which of the following is the correct output expression for an eight to one MUX? (D_i is the ith input to the mux while m_i is the ith minterm for the selection variables)

- a) $Y = D(m_0 + m_1 + m_2 + \dots + m_7)$
- b) **$Y = D_0 \cdot m_0 + D_1 \cdot m_1 + D_2 \cdot m_2 + \dots + D_7 \cdot m_7$**
- c) $Y = m_0' + m_1' + m_2' + \dots + m_7'$
- d) $Y = D_0 \cdot m_0' + D_1 \cdot m_1' + D_2 \cdot m_2' + \dots + D_7 \cdot m_7'$
- e) $Y = D \cdot m_0 + D \cdot m_1 + D \cdot m_2 + \dots + D \cdot m_7$

6. A 3-to-8-line decoder is connected as shown. Where x , y and z are inputs (z is the least significant input digit) and F is an output. Which of the following expressions correctly describes F ?

 - a) $F(x,y,z) = z$
- b) $F(x,y,z) = x$
- c) $F(x,y,z) = z'$
- d) $F(x,y,z) = yz$**
- e) $F(x,y,z) = x'$




7. A circuit which gates one input of data line to one of 2^n output lines is defined as a

- a) MUX
- b) DeMUX**
- c) Encoder
- d) Decoder
- e) ROM

8. A 3-to-8-line decoder is connected as shown, where x , y , and z are inputs (z is the least significant input digit) and F is an output. $F = 1$ when

 - a) All 3 inputs are logical 0
- b) 2 out of 3 inputs are logical 0
- c) 1 out of 3 inputs are logical 0**
- d) No input is logical 0
- e) None of the above




9. A circuit which translates n input lines into an m -bit code word, where $n \leq 2^m$ is defined as a

- a) MUX
- b) DeMUX
- c) Encoder**
- d) Decoder
- e) ROM

10. Which of the following correctly describes output Y_i (0 to 7) of the 3-to-8-line decoder, where m_i is the i^{th} minterm of the three variables applied to the input lines 2^0 , 2^1 , 2^2 , and E is the enable input?

 - a) $Y_i = m_i * E$
- b) **$Y_i = (m_i * E)'$**
- c) $Y_i = (m_i * E)'$
- d) $Y_i = (m_i * E)$
- e) $Y_i = (m_i * E)'$



Q.3) (50 points) We would like to design a circuit that adds three bits X, Y and Cin and produces the sum bit S and the carry out bit Cout.

- 1) (10 points) Write the true table for the functions S and Cout. In your truth table X should be the MSB, and Cin should be the LSB.
- 2) (10 points) Implement the functions S and Cout using a 3-to-8 decoder.
- 3) (10 points) Implement the function S using a 2²-to-1 MUX.
- 4) (20 points) Implement the function Cout using a 2¹-to-1 MUX.


For parts (2), (3), and (4) **DO NOT FORGET TO LABEL** the decoder/MUX pins correctly to correspond to the variables in the truth table.

Solution

(1) The truth table for functions S and Cout is as follows:


X	Y	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

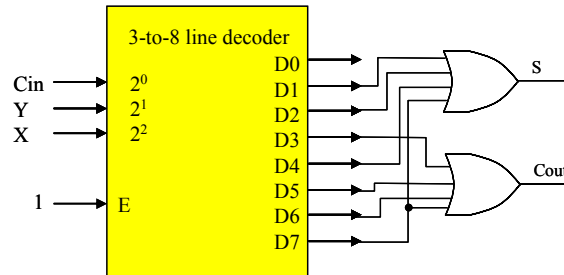(2) The implementation of functions S and Cout using a 3-to-8 line decoder is as follows:




(3) The implementation of the function S using a 4-to-1 MUX is as follows:

X	Y	Cin	S
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 

(4) The implementation of the function Cout using a 2-to-1 MUX is as follows:

X	Y	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

Q.4) (30 points) Design a combinational circuit that takes a BCD digit as input represented by the four bits A3A2A1A0 and produces an output F. F should be 1 if the BCD digit is valid (i.e. between 0 and 9, inclusive) and should be zero otherwise. Implement the circuit as a sum of products.

Solution:

The truth table for the required is as shown. Note the function $F(A3, A2, A1, A0)$ is equal to 1 for binary codes 0000, 0001, ..., and 1001. The function $F(A3, A2, A1, A0)$ is equal to 0 otherwise.

The corresponding K-map is as shown. Therefore, $F(A3, A2, A1, A0) = A3' + A2'A1'$.

The circuit implementation is as shown also in figure below.

Digit	A3	A2	A1	A0	F
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	0

