

***COMPUTER ENGINEERING DEPARTMENT***

**COE-202 – Fundamentals of Computer Engineering (section 02)**

**Student Name:**

**Student Number:**

---

**Q1. (20 points)** Given the function  $F(A,B,C,D) = AB'C' + AC + A'CD'$

- Plot the K-Map for  $F(A,B,C,D)$
- Determine the Prime Implicants and the Essential Prime Implicants for function  $F(A,B,C,D)$ .
- Simplify the function  $F(A,B,C,D)$  in the form of sum of products
- Simplify the function  $F(A,B,C,D)$  in the form of product of sums
- Implement the circuit in part (d) with NOR gates.