

**Assignment 8 (Due this Wed.)**  
**COE360 (052) – Dr. M. Elrabaa**

Q1) Implement the following Function in CMOS using minimum number of transistors:


$$\overline{\mathbf{F} = \mathbf{A} (\mathbf{B} + \mathbf{C} (\mathbf{D} + \mathbf{E} (\mathbf{G} + \mathbf{H} )) )}$$

Q2) Implement the following Function in CMOS using minimum number of transistors:

$$\mathbf{F} = \mathbf{A} (\mathbf{B} + \overline{\mathbf{C}} \cdot \mathbf{D} + \mathbf{E} \cdot \mathbf{G})$$

Q3) Re-do Q2 above assuming that inputs are available in true and complement form.

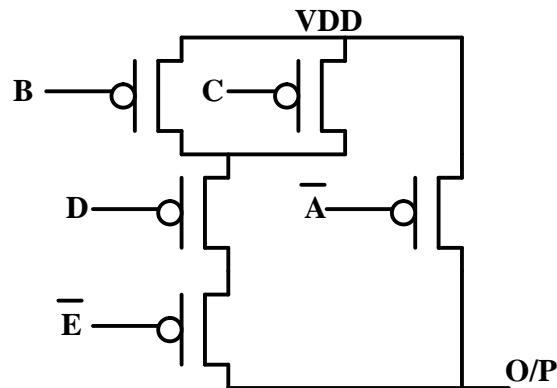Q4) The following schematic shows the PMOS (PU) block of a CMOS gate. Complete the schematic of the gate (i.e. the NMOS PD block) and specify the function implemented by this gate.



Q5) Implement the following logic block in CMOS gates:

- 1) Using minimum number of logic levels
- 2) Using minimum number of transistors

