

 






The following layouts of CMOS circuits:




 
1. Obtain the circuit schematic with transistors sizes (W/L) in microns (assume a $1\mu\text{m}$ technology)
2. What is the function of this circuit?







 

Here are some layouts to see ...

    


    

    

nMOS network graph

Common Euler path :
E - D - A - B - C

 

pMOS network graph

