

King Fahd University of Petroleum and Minerals
College of Computer Science and Engineering
Computer Engineering Department

COE 202: Digital Logic Design (3-0-3)
Term 101 (Fall 2010)
Major Exam 2
Sunday, December 26th, 2010

Time: 120 minutes

Name: _____ **ID:** _____ **Section:** _____

Notes:

- Do not open the exam book until instructed
- Calculators are not allowed (basic, advanced, cell phones, etc.)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

Question	Maximum Points	Your Points
1	10	
2	10	
3	20	
4	15	
5	15	
6	20	
Total	90	


Question 1.

(10 points)


Fill in the Spaces: (Show all work done to reach your answer)

a. For a 4-input function, $F(A, B, C, D)$, which of the following expressions represents the prime implicant having the largest area on the function's K-map?:

- (i) $AB+C+CD$
- (ii) $AB\overline{C}\overline{D}$
- (iii) $\overline{A}C$

b. The symbol  is an equivalent representation of the _____ gate.

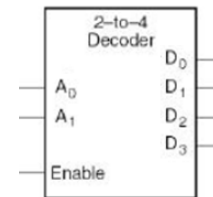
c. Given five 2-to-4 decoders with Enable (similar to the one shown opposite), the largest decoder we can build without any additional components is a _____-to-_____ decoder.



d. For $XYZ = 100$, the function $F(X, Y, Z) = X \oplus Y \oplus Z$ is _____(0/1). This function can be used to generate and detect _____ even/odd parity in digital communications.

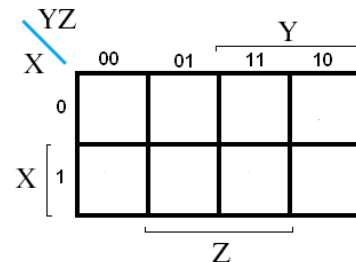
e. Represent the function $F(X, Y, Z)$ given below on the opposite K-map:

$$F(X, Y, Z) = (\overline{X} + Z) \cdot (X + Y + \overline{Z}) \cdot (X + \overline{Y} + Z)$$



f. In the priority encoder shown opposite, the output $Y_2Y_1Y_0 = 101$. Circle any statements that can correctly describe the status at inputs D_0 - D_7 , with all other inputs being in a don't care condition:

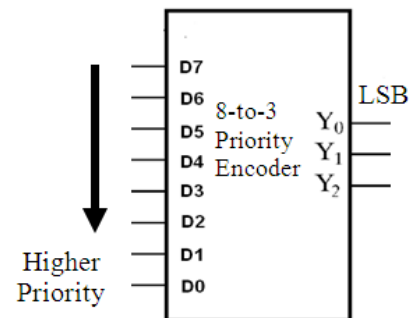
- i. $D_3 = 1$ and $D_5 = 1$
- ii. $D_6 = 1$ and $D_5 = 1$
- iii. $D_1 = 1$ and $D_2 = 1$
- iv. $D_0 = 1$ and $D_2 = 1$



(20 Points)**Question 3.**

Consider the function $F(W, X, Y, Z) = \overline{W}YZ + \overline{W}\overline{Z} + WYZ$

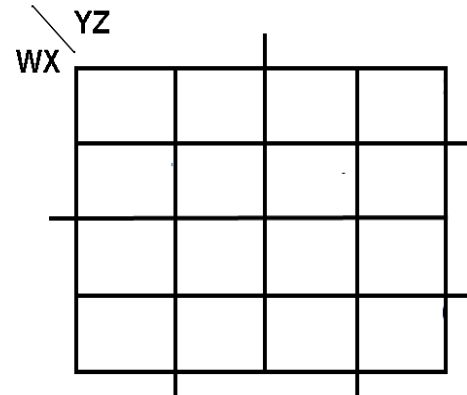a. Represent the function on the K-map opposite, showing both the 1s and 0s of the function.



b. Express $F(W, X, Y, Z) = \Sigma m(\underline{\hspace{2cm}})$

c. Express $F(W, X, Y, Z) = \Pi M(\underline{\hspace{2cm}})$

d. Use the K-map to minimize the expression above for F to 4 literals

e. Draw the logic diagram for a 2-level implementation of $F(W, X, Y, Z) = \overline{W}YZ + \overline{W}\overline{Z} + WYZ$ using only NAND gates. Assume that both the true and complemented forms of each variable are readily available.

Question 4.**(15 Points)**Given the following K-map for a function F :

(a) List all Essential Prime Implicants

CD \ AB	00	01	11	10
00				
01	1	1		
11	1		1	1
10		1	1	1

(b) Provide a minimized **SOP** expression of F (c) Provide a minimized **POS** expression of F


Question 5. Given the function

(15 Points)


$$F(A,B,C) = \prod M(0,1,3,4,6,7)$$

a. Implement F using two 2-to-4 decoders (each has an enable En input), an inverter and a NOR.

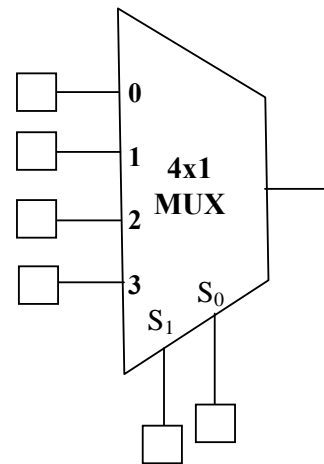b. Implement F using the 4-to-1 MUX shown below. Show how you obtained your solution.



c. Convert the following logic circuit to NAND-only:

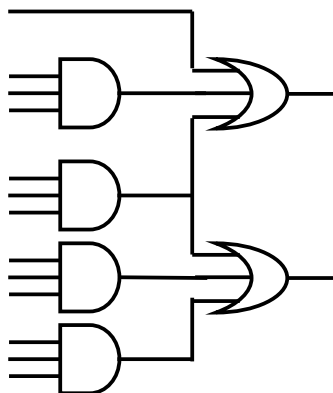

Question 6.**(20 Points)**

Use any number of the following MSI components: **inverters, decoders, encoders, multiplexers, adders, and/or magnitude comparators**, to design a circuit that takes two 4-bit binary numbers $A = A_3A_2A_1A_0$ and $B = B_3B_2B_1B_0$ and a 2-bit user selection input $S = S_1S_0$. The circuit should produce a 5-bit output $O = O_4O_3O_2O_1O_0$ according to the following table:

S_1S_0	O is equal to
00	$\text{Max}(A, B)$
01	$\text{Min}(A, B)$
10	$2 \times A$
11	$A - B$

Note that you must clearly label the MSI part used together with all inputs and outputs.