

King Fahd University of Petroleum and Minerals
College of Computer Sciences and Engineering
Department of Computer Engineering

COE 202 – Fundamentals of Computer Engineering (T081)

CAD Assignment # 02 (due date & time: Saturday 24/01/2009 during class period)

***** Show all your work. No credit will be given if work is not shown! *****

Using the “*LogiSim*” tool, build the circuit of Problem # 1 of Homework # 05. Label the clock as well as all flip-flops states, external input, X , and external output, F . Verify that your circuit is functioning properly. To build the circuit you need to load libraries from the “Project → Load Library → Built-in Library” submenu.

Save your circuit and name the file “*CAD02_yourStudentID.circ*”.

Deliverables:

1. Send a soft copy of your circuit file to both myself (marwan@kfupm.edu.sa) and the grader (s200572490@kfupm.edu.sa) with the “subject” line being “*COE202-CAD02-yourStudentID*”.
2. Submit a printout of the circuit window. Make sure that the entire circuit appears in the printout.
3. Submit snapshots of the circuit output for all possible state transitions.