

King Fahd University of Petroleum and Minerals
College of Computer Sciences and Engineering
Department of Computer Engineering

COE 202 – Fundamentals of Computer Engineering (T102)

Homework # 04 (due date & time: Saturday 23/04/2011 during class period)

***** Show all your work. No credit will be given if work is not shown! *****

Problem # 1 (10 points):

Assume that both true and complement forms of the input variables are available. Provide an all-NAND implementation for the minimized expressions for the following:

- i. (5 points) $F(A, B, C, D) = \sum m(0, 1, 2, 3, 6, 7, 10, 11, 14, 15)$
- ii. (5 points) $F(A, B, C, D) = \prod M(4, 5, 6, 7, 8, 9, 14, 15)$

Problem # 2 (10 points):

Assume that both true and complement forms of the input variables are available. Provide an all-NOR implementation for the minimized expressions for the following:

- i. (5 points) $F(A, B, C, D) = \sum m(0, 1, 2, 3, 6, 7, 10, 11, 14, 15)$
- ii. (5 points) $F(A, B, C, D) = \prod M(4, 5, 6, 7, 8, 9, 14, 15)$

Problem # 3 (40 points):

Design a circuit that accepts two 2-bit unsigned numbers A (i.e. A_1A_0) and B (i.e. B_1B_0). The circuit produces $|A - B|$. Provide an all-NOR implementation of the circuit. Assume that both true and complement forms of the input variables are available.

Problem # 4 (10 points): Use a 4×16 non-inverted-output decoder and external gate(s) to implement the following function:

$$F(A, B, C, D) = \sum (2, 3, 5, 6, 8, 9, 14)$$

Problem # 5 (10 points): Repeat problem # 4 but use a 4×16 inverted-output decoder and external gate(s).

Problem # 6 (10 points): Repeat problem # 4 but use a 16×1 MUX and external gate(s).

Problem # 7 (10 points): Repeat problem # 4 but use an 8×1 MUX and external gate(s). Connect C , A , and D to S_2 , S_1 , and S_0 , respectively.