

King Fahd University of Petroleum and Minerals
College of Computer Sciences and Engineering
Department of Computer Engineering

COE 202 – Digital Logic Design (T112)

CAD Assignment # 01 (due date & time: Wednesday 04/04/2012 during class period)

***** Show all your work. No credit will be given if work is not shown! *****

Using the “*LogicWorks*” tool, build the circuit of Problem # 3 of Homework # 03 with only **NOR** gates. Label all inputs and outputs. Verify that your circuit is functioning properly by applying all input combinations.

Save your circuit and name the file “*CAD01_yourStudentID.ccf*”.

Deliverables:

1. Send a soft copy of your circuit file to both myself (marwan@kfupm.edu.sa) and the grader (s200832420@kfupm.edu.sa) with the “subject” line being “*COE202-CAD01-yourStudentID*”.
2. Submit a printout of the circuit window. Make sure that the entire circuit appears in the printout.
3. Submit a printout of the timing window after applying all input combinations. Make sure to zoom-in as far as you can inside the timing window before printing. Also, make sure that both the sets of inputs and the sets of outputs show up in the printout.