

King Fahd University of Petroleum and Minerals  
College of Computer Sciences and Engineering  
Department of Computer Engineering

COE 202 – Digital Logic Design (T131)

**Homework # 04 (due date & time: Sunday 24/11/2013 during class period)**

**\*\*\* Show all your work. No credit will be given if work is not shown! \*\*\***

**Problem # 1 (25 points):** Use a 4×16 **non-inverted-output decoder** and external gate(s) to implement the following function:

$$F(A, B, C, D) = C \cdot (\overline{A} + \overline{D}) \cdot (\overline{B} + \overline{D})$$

**Problem # 2 (25 points):** Repeat problem # 1 but use a 4×16 **inverted-output decoder** and external gate(s).

**Problem # 3 (25 points):** Repeat problem # 1 but use a 16×1 MUX and external gate(s).

**Problem # 4 (25 points):** Repeat problem # 1 but use an 8×1 MUX and external gate(s). Connect *C*, *B*, and *D* to *S*<sub>2</sub>, *S*<sub>1</sub>, and *S*<sub>0</sub>, respectively.