

King Fahd University of Petroleum and Minerals
College of Computer Sciences and Engineering
Department of Computer Engineering

COE 202 – Digital Logic Design (T161)

Homework # 04 (due date & time: Tuesday 29/11/2016 during class period)

*** Show all your work. No credit will be given if work is not shown! ***

Problem # 1 (20 points): Use a 4×16 decoder and external gate(s) to implement the following function:

$$F(A, B, C, D) = A.(\overline{C} + \overline{D}).(\overline{B} + \overline{D})$$

Problem # 2 (20 points): Repeat problem # 1 but use a 16×1 MUX and external gate(s).

Problem # 3 (20 points): Repeat problem # 1 but use an 8×1 MUX and external gate(s). Connect *C*, *B*, and *D* to *S*₂, *S*₁, and *S*₀, respectively.

Problem # 4 (40 points): Using minimal standard components such as decoders, multiplexers, adders, subtractors, and/or comparators, and any other necessary logic gates design a circuit that takes two 4-bit binary numbers $A = A_3A_2A_1A_0$ and $B = B_3B_2B_1B_0$ and a 2-bit user selection input $S = S_1S_0$. The circuit should produce a 5-bit output $O = O_4O_3O_2O_1O_0$ according to the following table:

| S_1S_0 | O is equal to |
|----------|--|
| 00 | Max(A, B) |
| 01 | Min(A, B) |
| 10 | $2 \times A$ |
| 11 | $ A - B $ (i.e. absolute value of ($A - B$)) |

Note that you don't need to show the internal implementation of the MSI components used in your design. **Properly label all components, their inputs and outputs.**