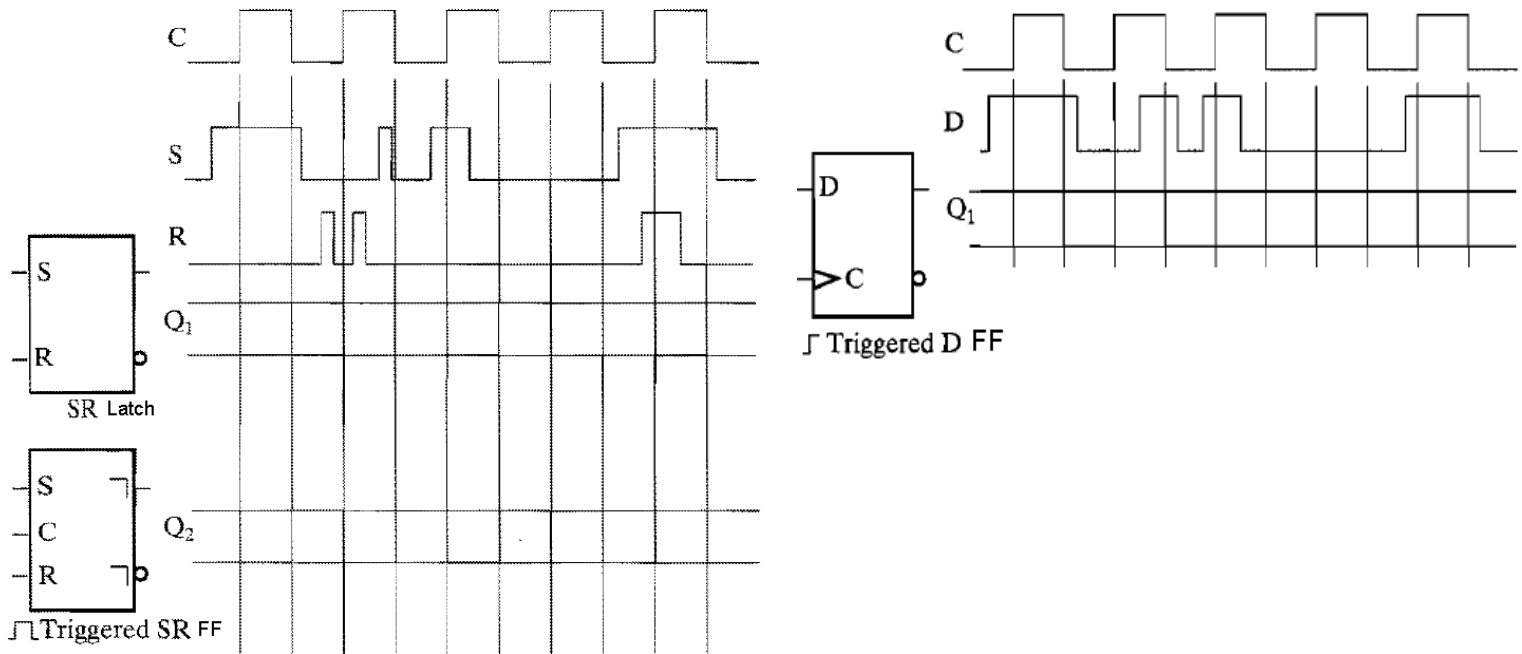



1. Carefully sketch the Q waveforms for each of the latches/flip flops below for the given input and clock signals.



2. Solve Problem 5-6 on page 299 of the textbook. In part (b) provide both the 2-D and the 1-D state tables.

 
3. Analyze the sequential circuit in the figure opposite and determine its performance in the form of:

- A one-dimensional state table.
- A two-dimensional state table.
- A state diagram



 4. Refer to the state diagram opposite and answer the following questions:

- Is the circuit Mealy or Moore type?
- How many states, flip-flops, external inputs, and external outputs?
- Using the symbolic states indicated, express the state diagram as:
  - A 2-dimensional state table.
  - A 1-dimensional state table.
- Rewrite the 1-dimensional state table after making state assignments that give states A to F the sequence of binary numbers starting at 0, i.e. A = 0, B = 1, C = 2, etc. respectively.
- Design the circuit using D flip-flops that have direct S, R inputs. Use the 1-dimensional state table in (e) to optimize the flip flop inputs and the external output(s) using K-maps. Assume that unused states are don't care conditions. Give optimized SOP Boolean expressions. Make optimum utilization of the don't care conditions for the combinational logic outputs.
- Give a complete logic diagram for the sequential machine. Include an external asynchronous INITIALIZE input that initializes the machine in state C.



5. We would like to design a sequential circuit that dynamically detects the occurrence of the sequence 10011 at its single external input. The output of the circuit will be normally 1, going to 0 only when the sequence is detected. For each of a Mealy and a Moore implementation of the circuit, give:

- a. A state diagram, marking states symbolically as A, B, C, etc.
- b. The number of states, state variables, flip flops.

6.

- a. Give the binary state table for a 3-bit down (decrementing) counter starting from state 111 as the present state. The counter goes through the counting sequence 7, 6, 5, 4, 3, 2, 1, 0, 7, ... etc. Assume state variables are ABC (where C is the LSB)
- b. Use a K-map to obtain an optimized SOP logic expression for bit B of the counter.