
 


Synchronous Sequential Circuit Problems

 Problem # 1: Two positive edge-triggered D flip-flops are connected as shown in the figure. Both flip-flops are initialized to 0 at the beginning. Fill in the timing diagram for the two outputs Q1 and Q0.



Problem # 2: Use as many as necessary of the following counter with minimal external gates to design a counter that counts from 0 to 20.




Synchronous Sequential Circuit Problems

Question 1


Draw the Mealy state diagram and state table for a serial even parity checker. The circuit receives a word of 4-bits serially on its single input X and produces the even parity bit after the fourth bit is received. The single output Z remains 0 except when the final (fourth) bit is received and the total number of 1's in the word is odd. The machine returns to the reset initial state after the 4th input bit. ~~Using the state assignment heuristics, indicate a possible good state assignment~~ (show all your work).

 Question 2

A +ive edge triggered D-FF has a setup time of 2 ns and a hold time of 3 ns. If the waveforms shown below are applied to this FF, circle the timing violations and label them with the letters S or H depending on whether the violations are setup or hold time violations.



A level sensitive D-latch has a setup time of 3 ns and a hold time of 2 ns. If the waveforms shown below are applied to this FF, draw the output waveform (Q) and mark the timing constraints you would place on the D-input to satisfy the minimum setup & hold times. Assume that the initial FF-state is $Q = 1$.

 

Question 3

- Write the excitation tables of the D and the JK Ffs
- Design the synchronous sequential circuit whose state transition table is shown below. Use a D-FF to implement y_0 and a JK-FF to implement y_1 .

PS $y_1 y_0$	NS, out $Y_1 Y_0, Z$	
	$x = 0$	$x = 1$
0 0	0 1, 0	0 1, 0
0 1	1 1, 0	0 0, 1
1 1	0 1, 0	1 0, 0
1 0	1 1, 0	0 1, 1

Question 4

Draw the state diagram of the Moore machine which has 2 inputs (X_1, X_2) and one output Z . The output of the machine is determined by the following:

Z **does not change** its value if $X_1 X_2 = 00$

Z becomes **1** if $X_1 X_2 = 01$

Z becomes **0** if $X_1 X_2 = 10$


Z **change its value** if two consecutive 11 are received at the inputs $X_1 X_2$

The reset input initializes the machine to a 0 output.

Question 5

The state transition table of state machine with a single input x and a single output Z is shown below. Draw the present state variables the next state variables, and the output Z for the shown input waveform x .

PS y1 y0	NS Y1, Y2		Output (Z)
	x=0	x=1	
0 0	0 0	0 1	0
0 1	1 0	1 1	1
1 1	0 1	1 1	0
1 0	0 1	1 1	1

 

Question 6

Draw the Mealy state diagram and state table for a serial even parity checker. The circuit receives a word of 4-bits serially on its single input X and produces the even parity bit after the fourth bit is received. The single output Z remains 0 except when the final (fourth) bit is received and the total number of 1's in the word is odd. The machine returns to the reset initial state after the 4th input bit. ~~Using the state assignment heuristics, indicate a possible good state assignment~~ (show all your work).

Question 7


A synchronous sequential circuit has two inputs X_1X_2 representing a binary number, N . If the present value of N is greater than the previous value, then the two output bits $Z_1Z_2 = 10$. If the present value of N is less than the previous value then the output $Z_1Z_2 = 01$, otherwise $Z_1Z_2 = 00$.

Derive the Mealy state diagram (*Hint*: The machine needs only five states).

Derive the Moore state diagram (*Hint*: The machine needs at least 11 states).

Question 8

Derive the state table and state diagram of the synchronous sequential circuit shown (X is an input to the circuit). Explain the circuit function.

 

Question 9

An up-down mod-4 binary counter has a single input x , such that it counts up if $x=0$ and counts down if $x=1$:

Draw the Mealy state diagram of the circuit.

Draw the state Moore diagram of the circuit.

Implement both circuits using *negative-edge triggered* D-FFs.

For the shown input waveforms, draw the present state variables, the output variables and next state variables (D-inputs of the FFs) in both implementations (Mealy & Moore). Assume *zero propagation delay* and an initial count of 00

How the two sets of waveforms are different? Explain.

