

*King Fahd University of Petroleum and Minerals*  
*College of Computer Science and Engineering*  
*Computer Engineering Department*

**COE 202: Digital Logic Design (3-0-3)**

**Term 092 (Spring 2010)**

**Final Exam**

**Sunday June 13, 2010**

**7:30 a.m. – 10:00 a.m.**

**Time: 150 minutes, Total Pages: 11**

**Name:** \_\_\_\_\_ **ID:** \_\_\_\_\_ **Section:** \_\_\_\_\_

**Notes:**




- Do not open the exam book until instructed
- Calculators are not allowed (basic, advanced, cell phones, etc.)
- Answer all questions
- All steps must be shown
- Any assumptions made must be clearly stated

<b>Question</b>	<b>Maximum Points</b>	<b>Your Points</b>
<b>1</b>	<b>9</b>	
<b>2</b>	<b>25</b>	
<b>3</b>	<b>15</b>	
<b>4</b>	<b>20</b>	
<b>5</b>	<b>25</b>	
<b>6</b>	<b>6</b>	
<b>Total</b>	<b>100</b>	

**Question 1.**

**( 9 points)**

Analyze the following counters and indicate their count ranges in **binary**:

   a.	 <p style="text-align: center;">Synchronous Clear</p>	<p>_____ to _____</p>
b.	 <p style="text-align: center;">Synchronous Load</p>	<p>_____ to _____</p>
c.	 <p style="text-align: center;">Synchronous Load</p>	<p>_____ to _____</p>


**Question 2.**

**(25 Points)**



Fill in the spaces

a. The figure shows connections to the D input of stage *i* in a multi-function register of D-type flip flops. Study the circuit and then fill in missing information in the table below only for supported register functions.

Mode Select I/Ps (S1 S0)	Register Function (where applicable)
	Shift upward
	No change in output
	Shift downward
	Clear register
	Load external data input

 


  b. For the clocked S-R latch using NAND gates shown, complete the waveform of the Q output for the given S, R, and clock (C) inputs.




Initially the Q output is at 0 logic. Ignore any propagation delays.

 c. The flip flop shown is known as the JK flip flop. For  $J = 1$  and  $K = 0$ , the next state of the flip flop  $Q(t+1)$  will be  $Q(t+1) = \underline{\hspace{2cm}}$  (select from  $Q(t)$ ,  $\overline{Q(t)}$ , 0, 1).





 d. In the PROM circuit shown, X indicates a connection. At address  $A2A1A0 = 010$ , the ROM stores the data  $D3D2D1D0 = \underline{\hspace{2cm}}$ .




e. In the sequential circuit shown, input  $X = 1$ . Clock transition  $t1$  in the figure below puts the circuit in the state  $AB = 01$ . Fill in the two spaces in the following table:

Time	State of the circuit
After transition $t2$	
After transition $t3$	

  

 
f. In the PLA programmable logic device shown, give the algebraic expressions for the logic functions F1 and F2.



F1 =

F2 =

 g. In the 4-stage shift register shown, the serial output is fed back as the serial input. Initially the register contents (Q outputs) ABCD are 1000. It takes \_\_\_\_\_ (how many) clock pulses for a '1' to appear at the serial out. At this time, the contents ABCD = \_\_\_\_\_.



h. A memory device has 16 K locations, each being 8-bit wide. This device has \_\_\_\_\_ (how many) address lines and \_\_\_\_\_ (how many) data lines.


**Question 3.****(15 Points)**

Design a 4-bit up/down binary counter with two control inputs  $S_1S_0$ . The counter operates according to the shown function table:


$S_1S_0$	Function
00	Stop Counting
01	Count up
10	Count down
11	Initialize the counter to 0

You may build the counter with **only** the following three components:


(1)

 

(2)

 

(3)

 


*Draw a block diagram of your design and clearly label all inputs.*

**Question 4.**

**(20 Points)**

Consider the sequential circuit shown and then answer the following questions:

 a. Provide Boolean expressions for the D inputs of the flip flops and the external output Y.




b. Is the circuit Mealy or Moore?

c. Use your answer in (a) above to complete the following two-dimensional table state table that gives the next state AB and the external output Y in terms of the present state AB and the external input X.

Present State AB	Next State AB		Output Y	
	X = 0	X = 1	X = 0	X = 1
00				
01				
10				
11				

 d. From the state table in c above, complete the state diagram shown below, indicating all state transitions and output values. States are given in the format **AB**.



e. What is the minimum number of clock pulses required to move the circuit from state **AB = 11** to state **AB = 10**?

f. To satisfy the requirement in (e) above, the input X should have the sequence \_\_\_\_\_.

**Question 5.****(25 Points)**

A synchronous sequential circuit has a single input  $x$  and two outputs  $Z_2 Z_1$ . The state transition table of this circuit is given below (same table in 2 different forms).

Present State $y_1 y_0$	$x$	Next State	Outputs ( $Z_2 Z_1$ )
0 0	0	0 0	1 1
0 0	1	0 1	1 0
0 1	0	1 0	0 1
0 1	1	1 1	0 0
1 0	0	0 1	1 0
1 0	1	1 1	1 0
1 1	0	0 1	0 0
1 1	1	1 1	0 0

Present State $y_1 y_0$	Next State		Outputs ( $Z_2 Z_1$ )	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
0 0	0 0	0 1	1 1	1 0
0 1	1 0	1 1	0 1	0 0
1 1	0 1	1 1	0 0	0 0
1 0	0 1	1 1	1 0	1 0

- a. Provide a minimized design for this circuit using gates and D Flip-Flops,
- b. Draw the logic diagram of the circuit.
- c. Classify each of the two outputs ( $Z_2 Z_1$ ) either as Moore type or Mealy type.
- d. **If** this synchronous sequential circuit is implemented using a single ROM and a single register:
  - i. Define the size of the required ROM, and its total capacity in bits.
  - ii. What is the size of the register in bits?
  - iii. Define the ROM Truth Table.
  - iv. Draw the block diagram of this implementation (**CLEARLY LABEL each element, its inputs and outputs and show how they are connected**)



Present State y1 y0	x	Next State	Outputs (Z <sub>2</sub> Z <sub>1</sub> )
0 0	0	0 0	1 1
0 0	1	0 1	1 0
0 1	0	1 0	0 1
0 1	1	1 1	0 0
1 0	0	0 1	1 0
1 0	1	1 1	1 0
1 1	0	0 1	0 0
1 1	1	1 1	0 0

Present State y1 y0	Next State		Outputs (Z <sub>2</sub> Z <sub>1</sub> )	
	x = 0	x = 1	x = 0	x = 1
0 0	0 0	0 1	1 1	1 0
0 1	1 0	1 1	0 1	0 0
1 1	0 1	1 1	0 0	0 0
1 0	0 1	1 1	1 0	1 0

- d. If the previous synchronous sequential circuit is implemented using a *single ROM* and a *single register*:
- Define the size of the required ROM, and its total capacity in bits.
  - What is the size of the register in bits?
  - Define the ROM Truth Table.
  - Draw the block diagram of this implementation (**CLEARLY LABEL each element, its inputs and outputs and show how they are connected**)

**Question 6.****(6 Points)**

A sequential circuit has 2 inputs  $x$  and  $y$  and an output  $Z$ . The output equals “1” when it receives 4<sup>th</sup> occurrence of equal inputs  $x = y$  (not necessarily consecutive). After receiving these occurrences, the circuit starts counting these occurrences over again. The circuit has an additional reset input  $R$  which resets the circuit into the initial state.

$x =$	0	0	1	0	1	1	0	1	0	0	0	1	1	0	0	1	1	1	0	
$y =$	1	1	1	1	0	0	0	1	1	0	0	0	1	1	0	0	0	1	1	
$Z =$	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	1	0

**Draw the Mealy state diagram of the circuit**

