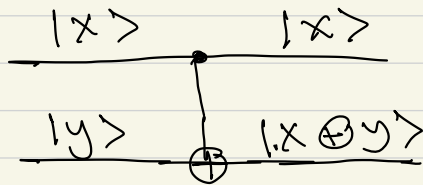


Lecture 12

12/10/20

• CNOT (Controlled-Not, $CNOT$)

- It takes two inputs, produces two outputs,



XOR \oplus		
x	y	
0	0	0
0	1	1
1	0	1
1	1	0

- $|x\rangle$ is a control bit that controls the out


- if $|x\rangle = 0$, $|0 \oplus y\rangle = |y\rangle$


- if $|x\rangle = 1$, $|1 \oplus y\rangle = |\neg y\rangle$

$$|x, y\rangle \longrightarrow |x, x \oplus y\rangle$$

	00	01	10	11
00	1	0	0	0
01	0	1	0	0
10	0	0	0	1
11	0	0	1	0

CNOT is reversible

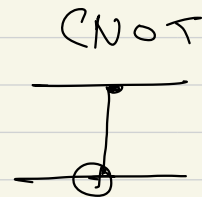


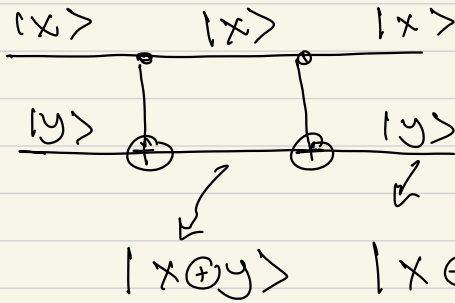

$$x \oplus x = 0$$

$$|0 \oplus y\rangle = |y\rangle$$

* Toffoli gate

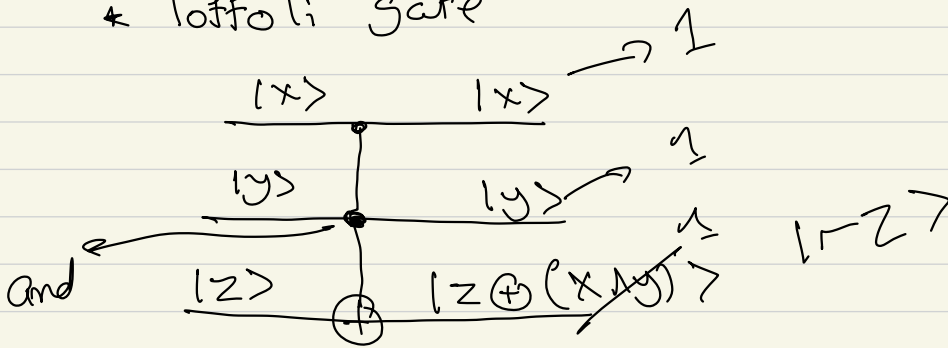


- Similar to CNOT, but it has two controlling bits

- $|z\rangle$ is flipped only when both $|x\rangle$ & $|y\rangle$ are $|1\rangle$

- Matrix of Toffoli gate


	000	001	010	011	100	101	110	111
000	1	0	0	0	0	0	0	0
001	0	1	0	0	0	0	0	0
010	0	0	1	0	0	0	0	0
011	0	0	0	1	0	0	0	0
100	0	0	0	0	1	0	0	0
101	0	0	0	0	0	1	0	0
110	0	0	0	0	0	0	0	1
111	0	0	0	0	0	0	1	0

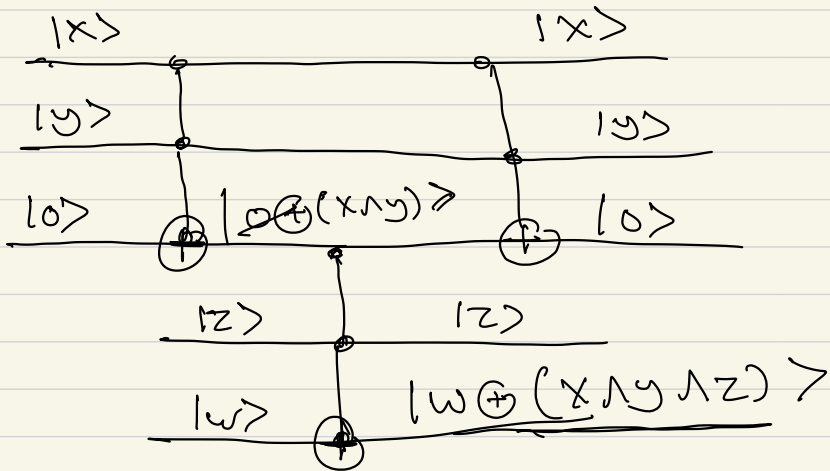• Can we have a gate with 3 controlling bits?




• Toffoli gate is a universal gate


• AND gate

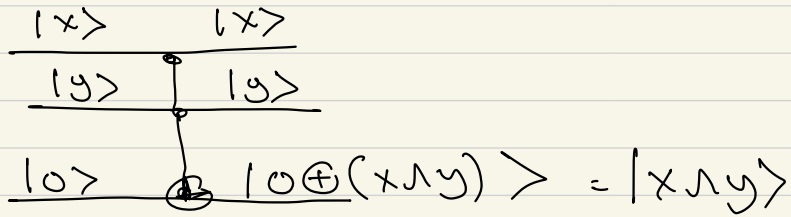

• NOT

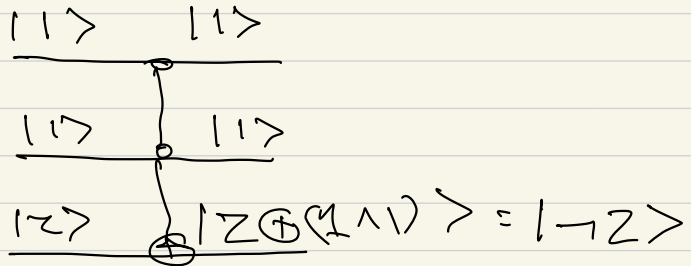


• Fan-out

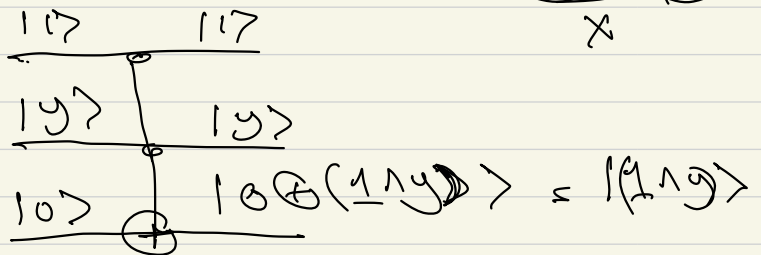

$100 \rightarrow 100$
 $1(1) \rightarrow 1(1)$

* Fredkin gate

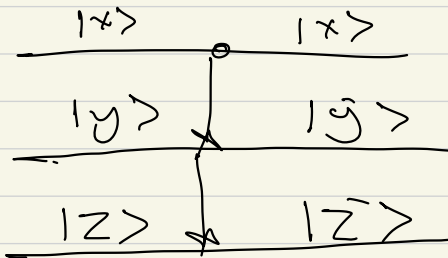

- $|x\rangle$ is a controlling bit


- if $|x\rangle = 0$, $|y\rangle = |y\rangle$ & $|z\rangle = |z\rangle$

- if $|x\rangle = 1$, $|z\rangle = |y\rangle$ & $|y\rangle = |z\rangle$

$$|0, y, z\rangle \mapsto |0, y, z\rangle$$


$$|1, y, z\rangle \mapsto |1, z, y\rangle$$

	000	001	010	011	100	101	110	111
000	1	0	0	0	0	0	0	0
001	0	1	0	0	0	0	0	0
010	0	0	1	0	0	0	0	0
011	0	0	0	1	0	0	0	0
100	0	0	0	0	1	0	0	0
101	0	0	0	0	0	0	1	0
110	0	0	0	0	0	1	0	0
111	0	0	0	0	0	0	0	1


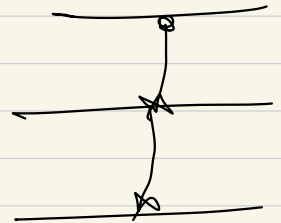


* Fredkin gate is a universal gate

- AND gate

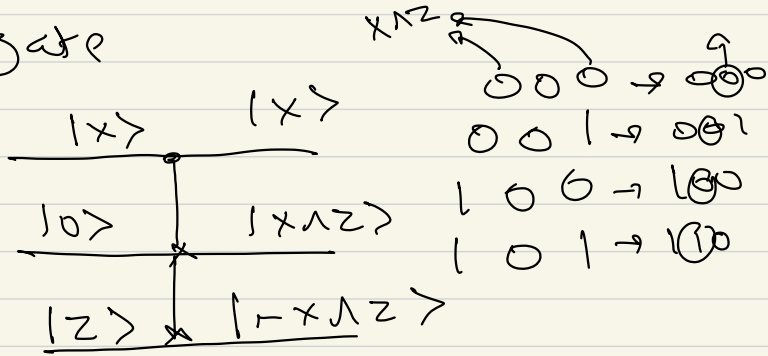

- NOT gate

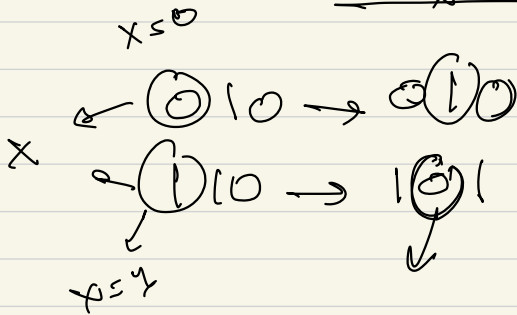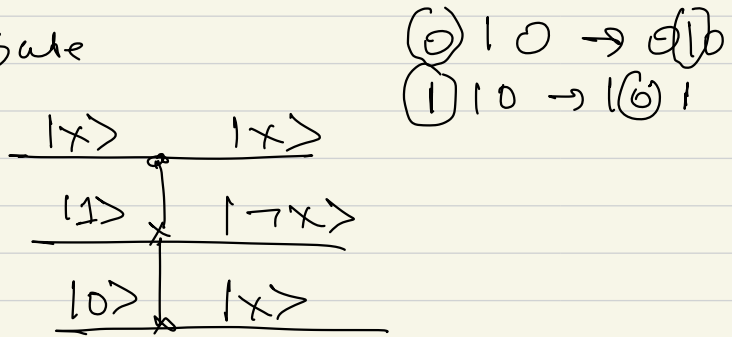

Sec 5.4 Quantum gate

Def 5.4.1 : A quantum gate is simply an operator that acts on qubits. Such an operator will be represented by unitary matrices.

← Example of quantum gates

1 - Identity

2 - NOT gate


3 - CNOT

4 - Toffoli

5 - Fredkin

6 - Hadamard
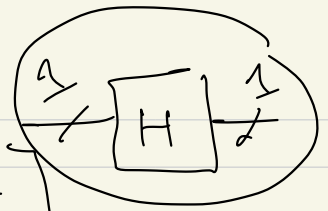
$$H = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & 1 \\ 1 & -1 \end{bmatrix} = \begin{bmatrix} \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & -\frac{1}{\sqrt{2}} \end{bmatrix}$$



$$\begin{array}{l} |1\rangle \\ |0\rangle \end{array} \rightarrow \frac{|0\rangle + |1\rangle}{\sqrt{2}} \quad \frac{1}{\sqrt{2}} |0\rangle + \frac{1}{\sqrt{2}} |1\rangle$$