

Arithmetic Circuits 3

COE 202

Digital Logic Design

Dr. Muhamed Mudawar


King Fahd University of Petroleum and Minerals

Presentation Outline

- ❖ Carry Lookahead Adder
- ❖ BCD Adder
- ❖ Binary Multiplier
- ❖ Carry-Save Adders in Multipliers

Carry Lookahead Adder

- ❖ Is it possible to eliminate carry propagation?
- ❖ Observation: $c_{i+1} = a_i b_i + (a_i \oplus b_i) c_i$
- ❖ If both inputs a_i and b_i are 1s then c_{i+1} will be 1 regardless of input c_i
- ❖ Therefore, define $g_i = a_i b_i$
- ❖ g_i is called **carry generate**: generates c_{i+1} regardless of c_i
- ❖ In addition, define $p_i = (a_i \oplus b_i)$ a_i or b_i is 1, not both
- ❖ p_i is called **carry propagate**: propagates value of c_i to c_{i+1}
- ❖ Equation of output carry becomes: $c_{i+1} = g_i + p_i c_i$
- ❖ If both inputs a_i and b_i are 0s then $g_i = p_i = 0$ and $c_{i+1} = 0$

 

Carry Bits

Carry bits are generated by a **Lookahead Carry Unit** as follows:

$$c_0 = \text{input carry}$$

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 c_1 = g_1 + p_1 (g_0 + p_0 c_0) = g_1 + p_1 g_0 + p_1 p_0 c_0$$

$$c_3 = g_2 + p_2 c_2 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 c_0$$

$$c_4 = g_3 + p_3 c_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 c_0$$

Define **Group Generate**: $GG = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0$

Define **Group Propagate**: $GP = p_3 p_2 p_1 p_0$

$$c_4 = GG + GP c_0$$

Carry does not ripple anymore


Reduced delay when generating c_1 to c_4 in parallel

4-Bit Carry Lookahead Adder



All **generate** and **propagate** signals (g_i, p_i) are generated in parallel

All carry bits (c_1 to c_4) are generated in parallel

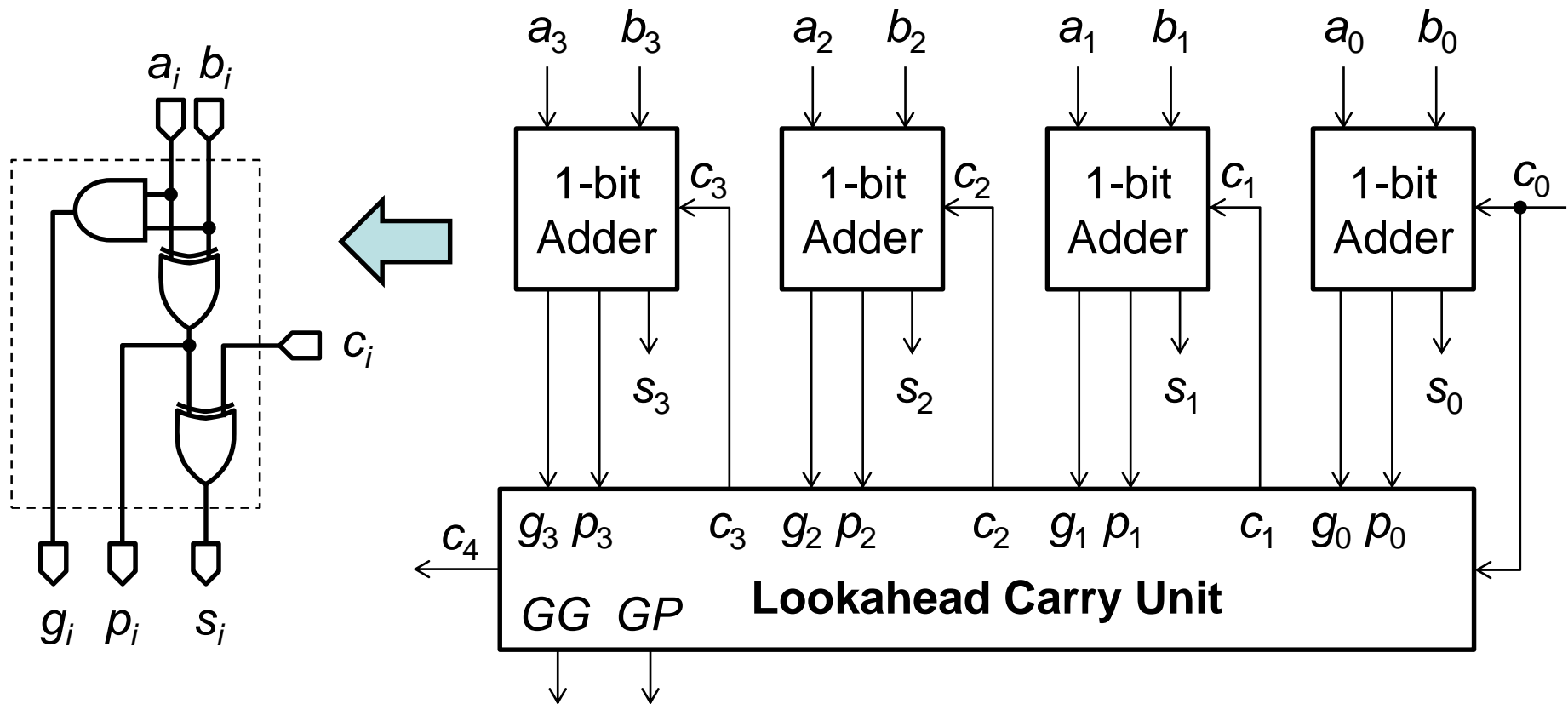The sum bits are generated faster than ripple-carry adder




Lookahead Carry Unit

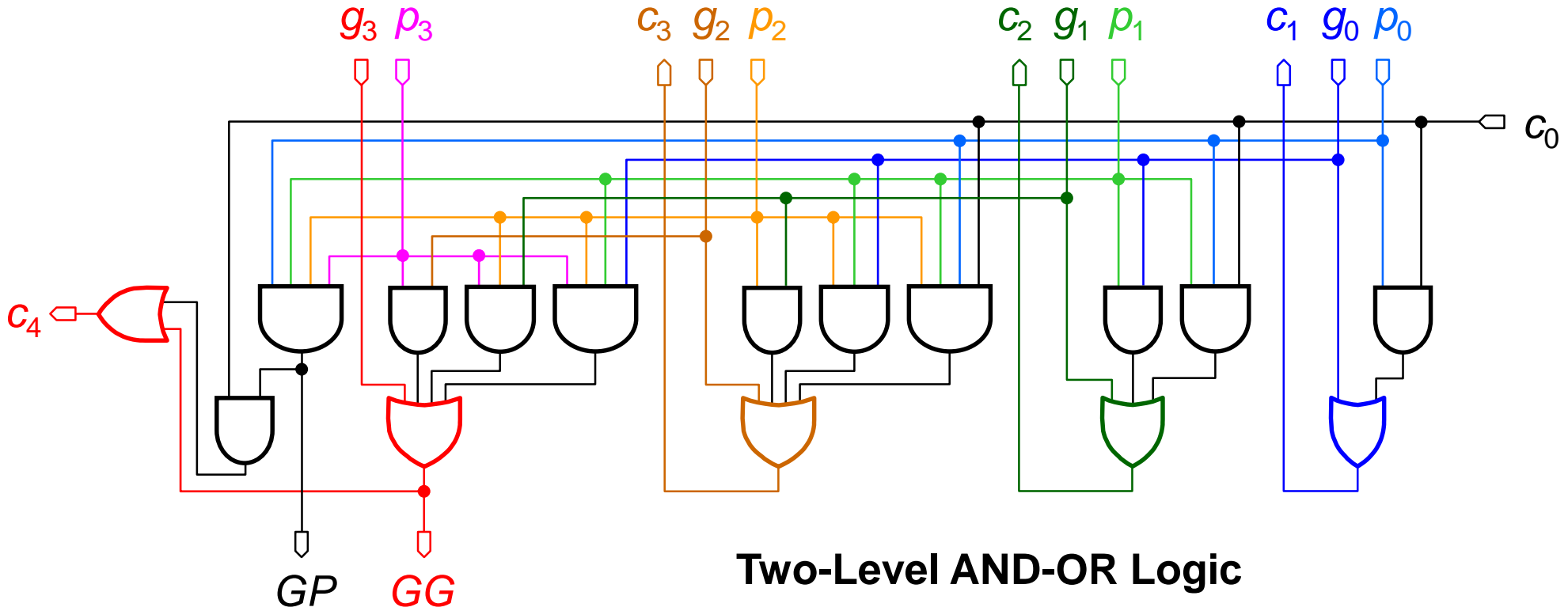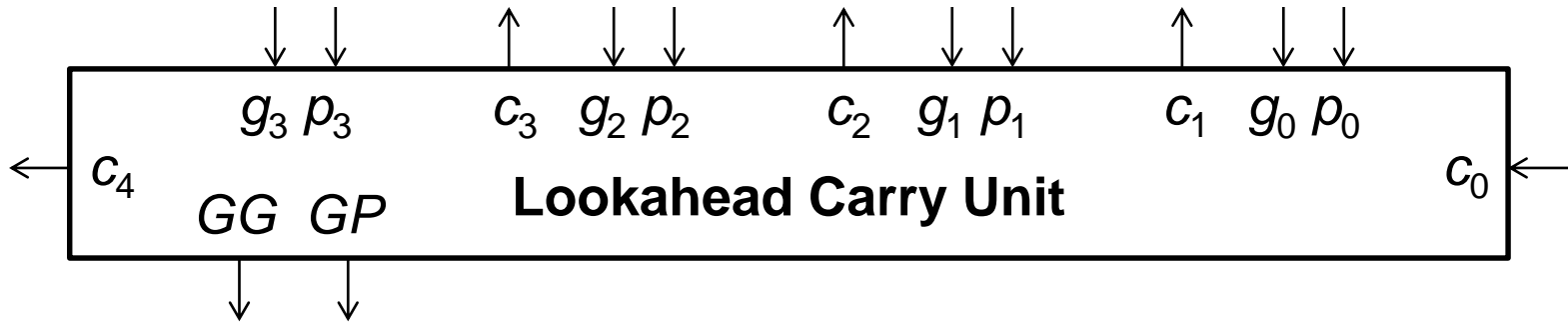


Longest Delay of the 4-bit CLA

- ❖ All generate and propagate signals are produced in parallel
- ❖ Delay of all g_i and $p_i = \Delta_1$ (Delay of XOR > Delay of AND)
- ❖ Carry bits $c_1, c_2,$ and c_3 are generated in parallel (Delay = Δ_2)
 - ✧ Carry-out bit c_4 is not needed to compute the sum bits
- ❖ Longest Delay of the 4-bit CLA = $\Delta_1 + \Delta_2 + \Delta_1 = 2 \Delta_1 + \Delta_2$

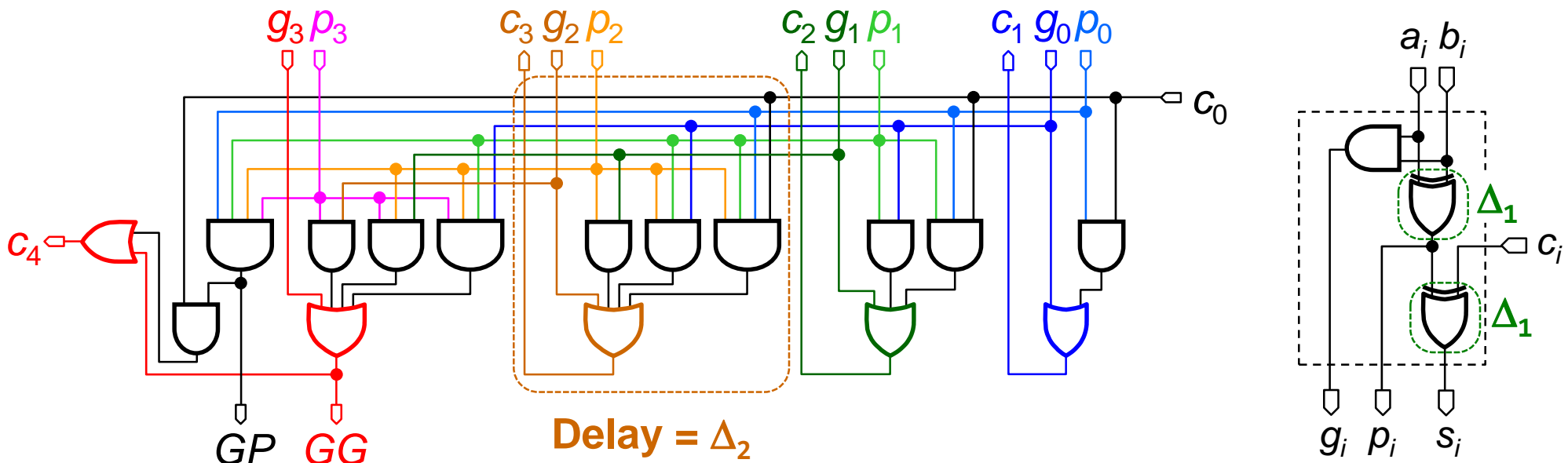


Hierarchical 16-Bit Carry Lookahead Adder

- ❖ Designed with Four 4-bit Carry Lookahead Adders (CLA)
- ❖ A **Second-Level Lookahead Carry Unit** is required
- ❖ Uses **Group Generate** (GG) and **Group Propagate** (GP) signals

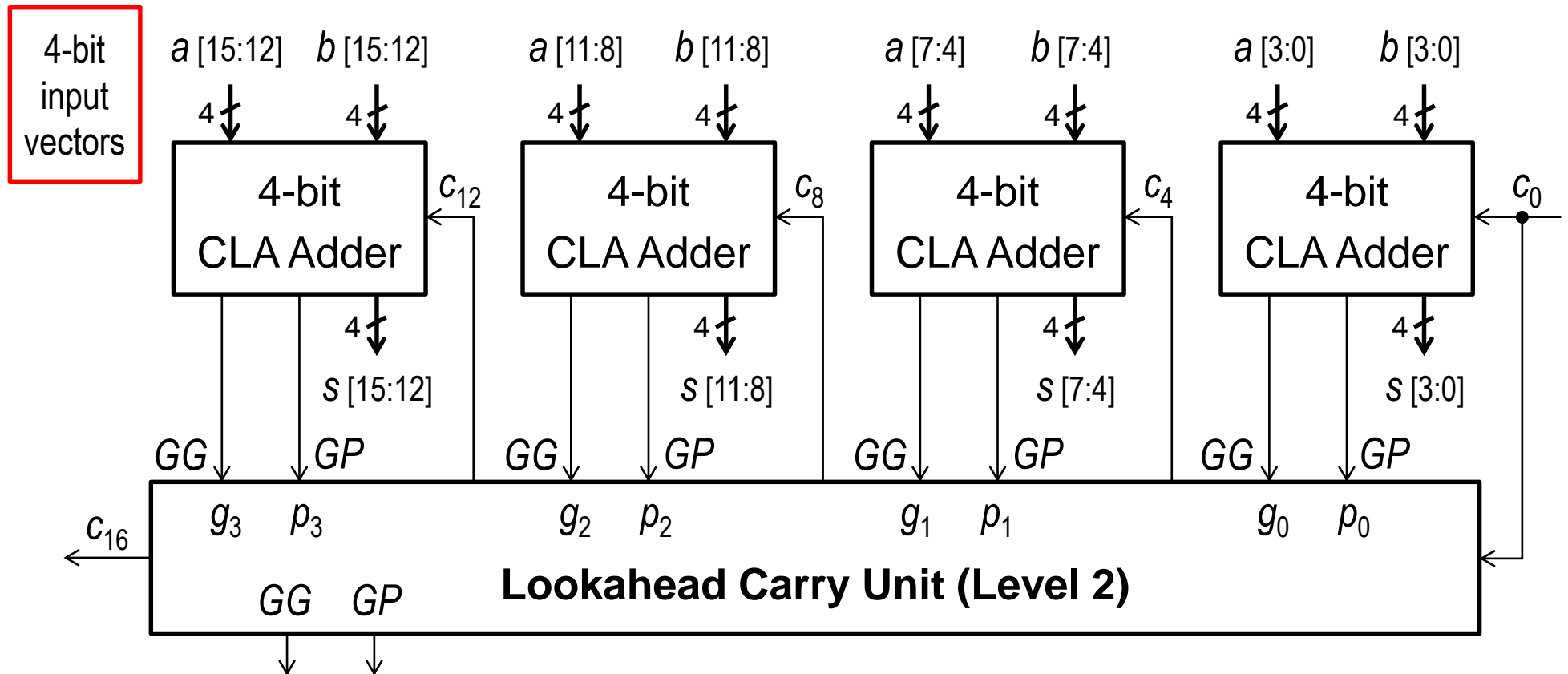

Hierarchical 64-Bit Carry Lookahead Adder

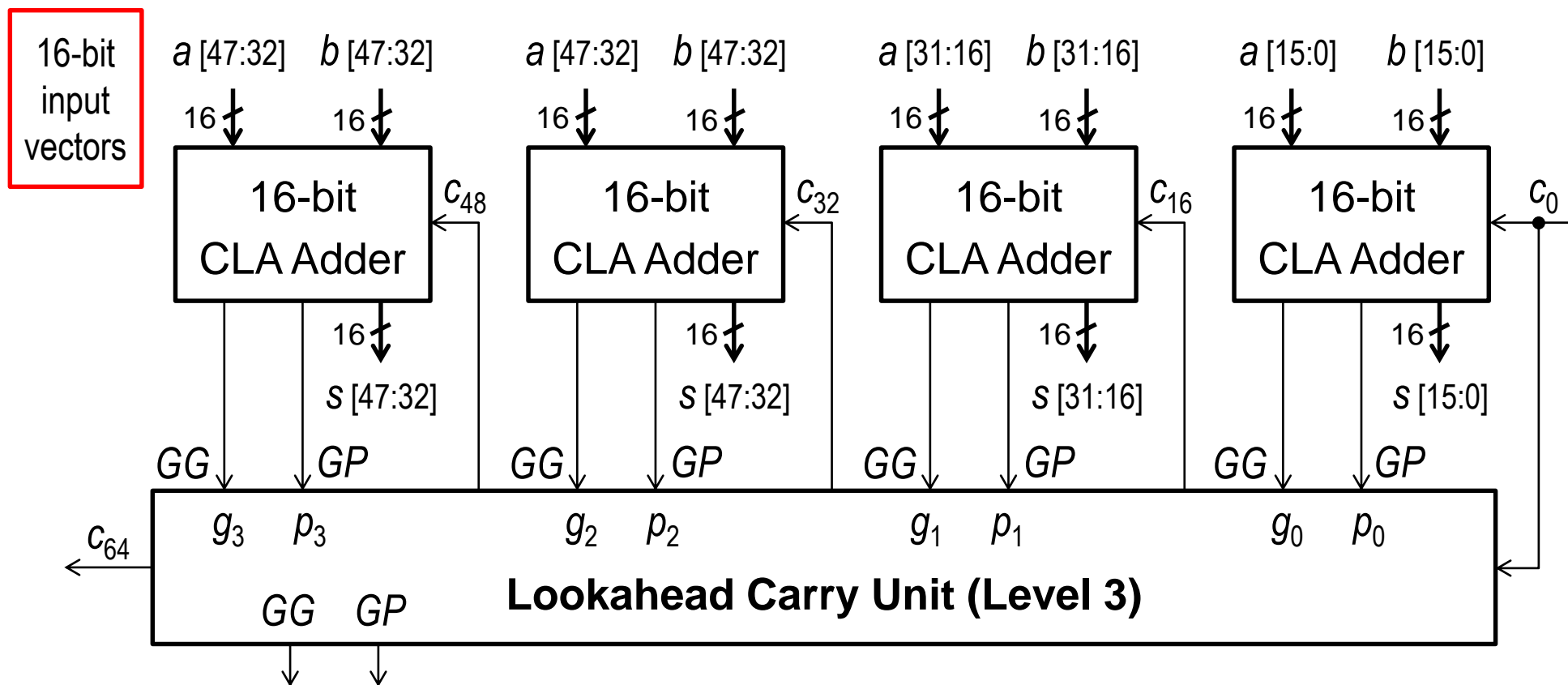- ❖ Designed with Four 16-bit Carry Lookahead Adders (CLA)
- ❖ A **Third-Level Lookahead Carry Unit** is required
- ❖ Uses **Group Generate** (GG) and **Group Propagate** (GP) signals



Next . . .

- ❖ Carry Lookahead Adder
- ❖ BCD Adder
- ❖ Binary Multiplier
- ❖ Carry-Save Adders in Multipliers

BCD Addition

- ❖ We use binary arithmetic to add the BCD digits

$$\begin{array}{r} 1000 \\ + 0101 \\ \hline 1101 \end{array} \qquad \begin{array}{r} 8 \\ + 5 \\ \hline 13 (>9) \end{array}$$

- ❖ If the result is more than 9, it must be corrected to use 2 digits
- ❖ To correct the digit, add 6 to the digit sum

$$\begin{array}{r} 1000 \\ + 0101 \\ \hline 1101 \\ + 0110 \\ \hline 1\ 0011 \end{array} \leftarrow \begin{array}{l} \text{Final answer} \\ \text{in BCD} \end{array} \qquad \begin{array}{r} 8 \\ + 5 \\ \hline 13 (>9) \\ + 6 \text{ (add 6)} \\ \hline 19 \text{ (carry + 3)} \end{array}$$

Multiple Digit BCD Addition



Add: 2905 + 1897 in BCD

Showing carries and digit corrections


| | | | | |
|------------------|-------|------|------|--|
| carry | +1 | +1 | +1 | |
| + 0010 | 1001 | 0000 | 0101 | |
| 0001 | 1000 | 1001 | 0111 | |
| <hr/> | | | | |
| 0100 | 10010 | 1010 | 1100 | |
| digit correction | 0110 | 0110 | 0110 | |
| <hr/> | | | | |
| 0100 | 1000 | 0000 | 0010 | |

Final answer: 2905 + 1897 = 4802

BCD Adder

 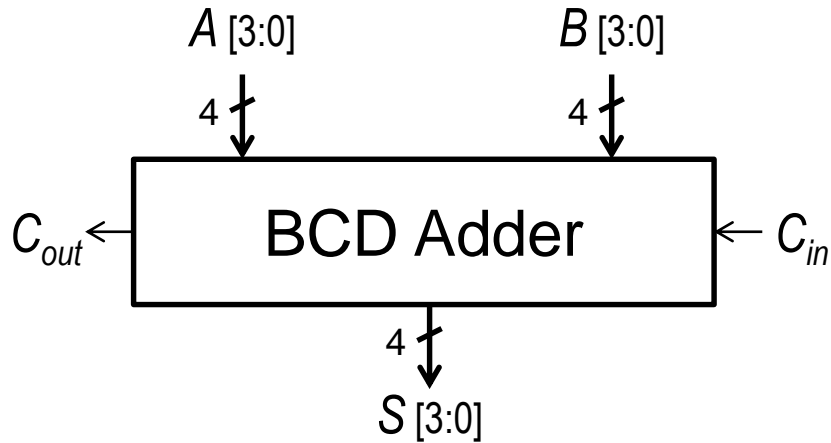


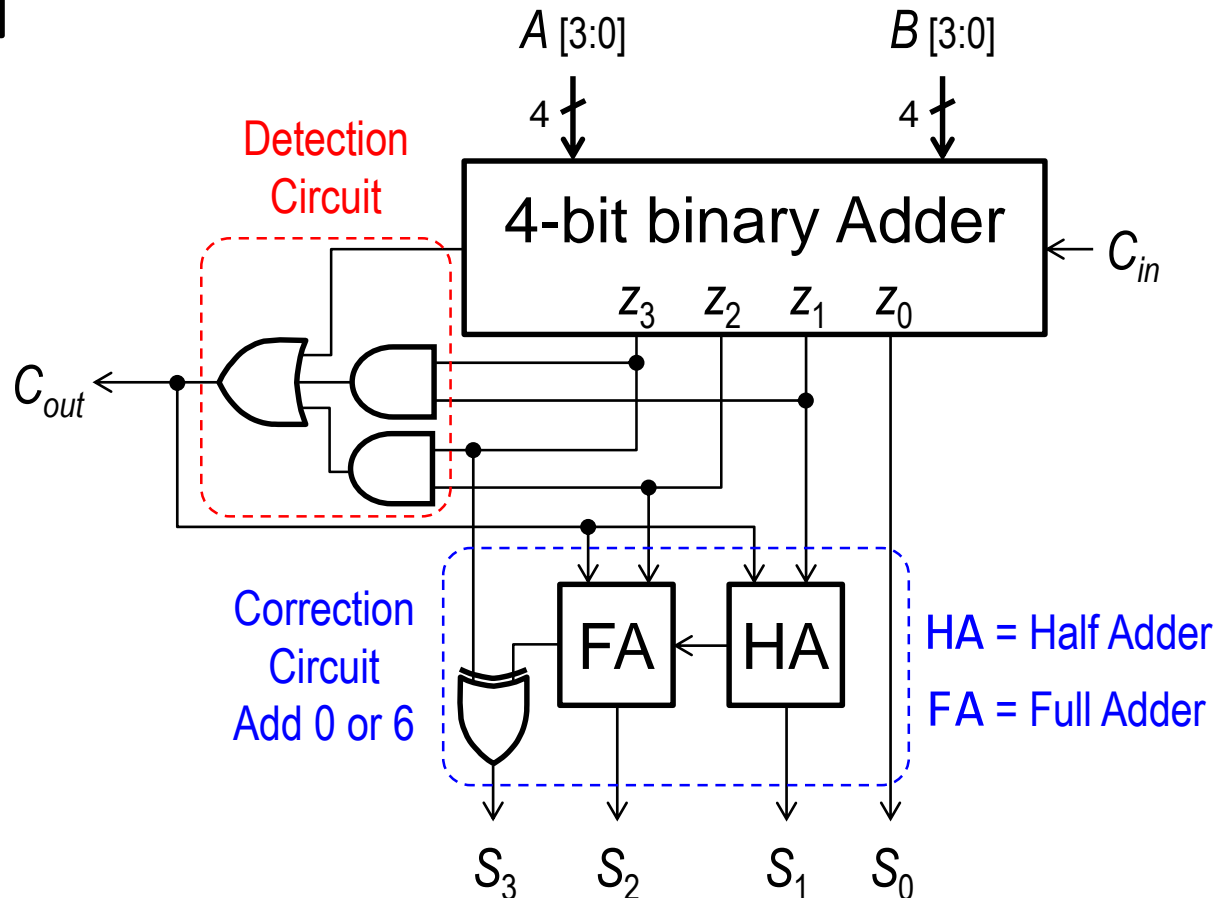Correction is required if: $A+B > 9$
 Correction circuit adds 0 or 6



Ripple-Carry BCD Adder

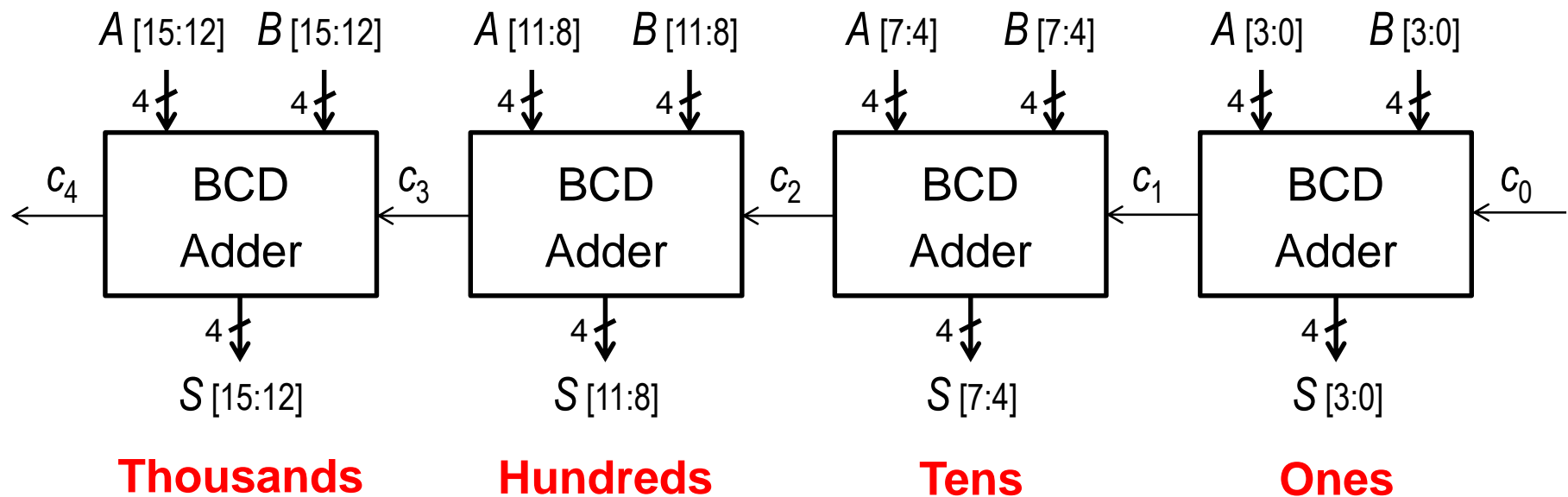- ❖ Inputs are BCD digits: 0 to 9
- ❖ Sum are BCD digits: **ones, tens, hundreds, thousands**, etc.
- ❖ Can be extended to any number of BCD digits
- ❖ BCD adders are larger in size than binary adders



Next . . .

- ❖ Carry Lookahead Adder
- ❖ BCD Adder
- ❖ Binary Multiplier
- ❖ Carry-Save Adders in Multipliers

Binary Multiplication

❖ Binary Multiplication is simple:

$$0 \times 0 = 0, \quad 0 \times 1 = 0, \quad 1 \times 0 = 0, \quad 1 \times 1 = 1$$

Multiplicand $1100_2 = 12$

Multiplier $\times 1101_2 = 13$

$$\begin{array}{r} 1100 \\ 0000 \\ 1100 \\ 1100 \\ \hline \end{array}$$

Binary multiplication
 $0 \times \text{multiplicand} = 0$
 $1 \times \text{multiplicand} = \text{multiplicand}$


Product $10011100_2 = 156$

❖ n -bit multiplicand \times n -bit multiplier = $2n$ -bit product

❖ Accomplished via **shifting** and **addition**


4-bit × 4-bit Binary Multiplier

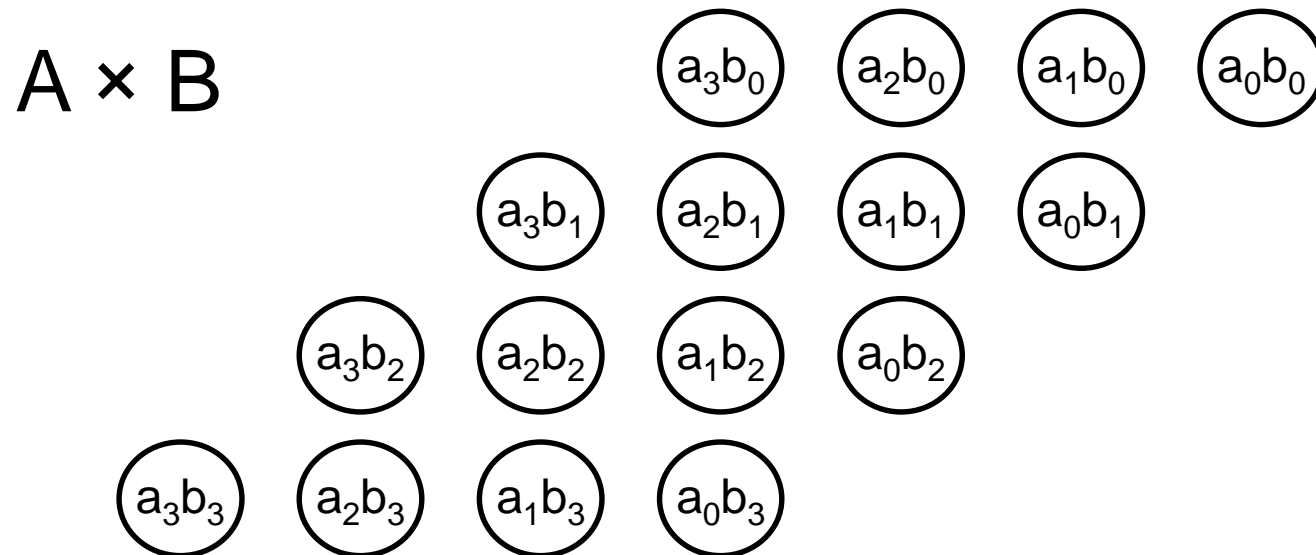- ❖ Suppose we want to multiply two numbers A and B
 - ✧ Example on 4-bit numbers: $A = a_3 a_2 a_1 a_0$ and $B = b_3 b_2 b_1 b_0$
- ❖ Step 1: AND (multiply) each bit of A with each bit of B
 - ✧ Requires n^2 AND gates and produces n^2 product bits
 - ✧ Position of $a_i b_j = (i+j)$. For example, Position of $a_2 b_3 = 2+3 = 5$




Adding the Bits Vertically

 - ❖ ADD the product bits vertically using **Carry-Save adders**
 - ✧ Full Adder adds three vertical bits
 - ✧ Half Adder adds two vertical bits
 - ✧ Each adder produces a partial sum and a carry
- ❖ Use **Carry-propagate adder** for final addition




Carry Save Adder

 - ❖ A n -bit carry-save adder produces two n -bit outputs
 - ✧ n -bit partial sum bits and n -bit carry bits
- ❖ All the n bits of a carry-save adder work in parallel
 - ✧ The carry does not propagate as in a carry-propagate adder
 - ✧ This is why a carry-save is faster than a carry-propagate adder
- ❖ Useful when adding multiple numbers (as in a multiplier)



Carry-Propagate Adder

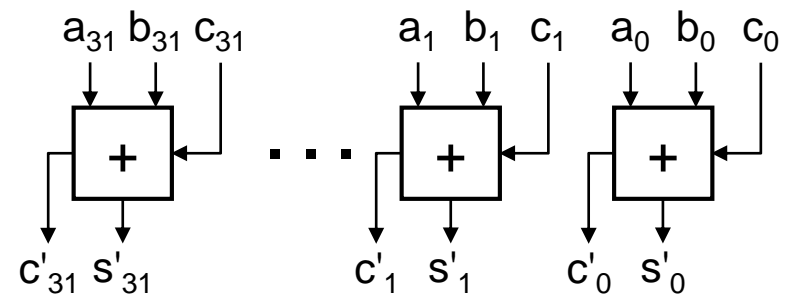

Carry-Save Adder

Carry-Save Adders in a Multiplier

Step 1: Use **carry save adders** to add the partial products

✧ Reduce the partial products to just two numbers

Step 2: Use **carry-propagate adder** to add last two numbers

