

**KING FAHD UNIVERSITY OF PETROLEUM & MINERALS**

**ELECTRICAL ENGINEERING DEPARTMENT**

**EE 201\_102**

**EXAM I**


**DATE: Wednesday 16/3/2011**

**TIME: 6:30 PM-8:00 PM**

<b>SER#</b>	
<b>ID#</b>	
<b>Name</b>	<b>KEY</b>
<b>Section#</b>	

	<b>Maximum Score</b>	<b>Score</b>
<b>Q1</b>	<b>20</b>	
<b>Q2</b>	<b>20</b>	
<b>Q3</b>	<b>25</b>	
<b>Q4</b>	<b>35</b>	
<b>TOTAL</b>	<b>100</b>	

Q1 (20)

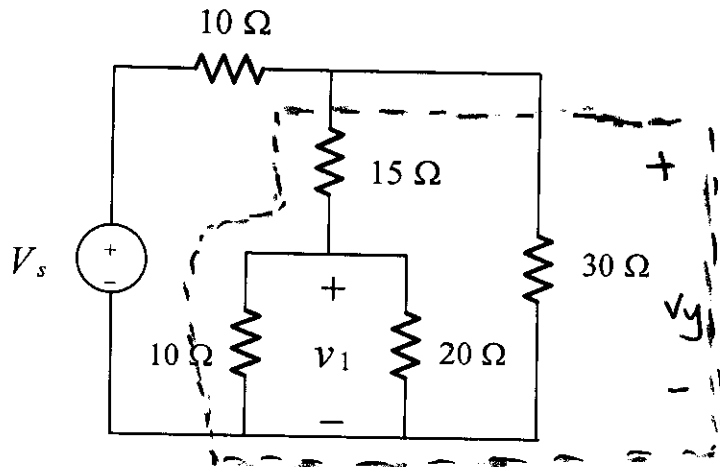

$$\begin{aligned}
 R_{eq} &= 30 \parallel [15 + (20 \parallel 10)] \\
 &= 30 \parallel [15 + 6.67] \\
 &= 30 \parallel 21.67 \\
 &= 12.58 \Omega
 \end{aligned}$$

For the circuit shown above find the voltage  $v_1$  in terms or as a function of the voltage source  $V_s$  ?

$$v_y = \frac{R_{eq}}{R_{eq} + 10} V_s = \frac{12.58}{10 + 12.58} V_s = 0.5572 V_s$$


$$v_1 = \frac{(10 \parallel 20)}{15 + (10 \parallel 20)} v_y$$

$$= \frac{6.67}{21.667} v_y$$

$$= \frac{6.67}{21.667} (0.5572 V_s)$$

$$= 0.17145 V_s$$

Q2 (20)

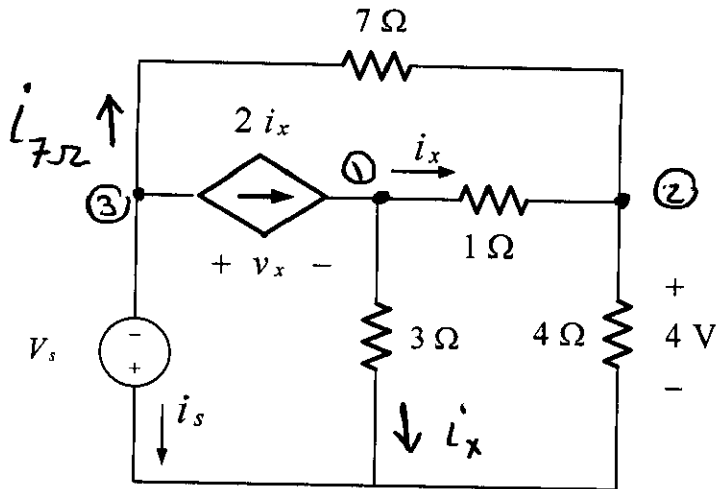

For the circuit shown above, without using nodal analysis (use KCL, KVL and Ohms Law) find the followings:

- (a)  $i_x$  ?
- (b)  $v_x$  ?
- (c)  $i_s$  ?
- (d)  $V_s$  ?

(a) KCL at ①  $i_{3\Omega} = i_x$

$\Rightarrow$  KVL:  $1i_x + 4 - 3i_x = 0 \Rightarrow i_x = 2A$


(b) KCL at ②  $i_{7\Omega} + i_x - \frac{4}{4} = 0 \Rightarrow i_{7\Omega} = -1A$

KVL  $\Rightarrow -v_x + 7i_{7\Omega} - 1i_x = 0$   
 $\Rightarrow v_x = -9V$

(c) KCL at ③  $i_{7\Omega} + 2i_x + i_s = 0$   
 $\Rightarrow i_s = -3A$

(d) KVL  $\Rightarrow V_s + v_x + 3i_x = 0 \Rightarrow V_s = 3V$

Q3 (25)

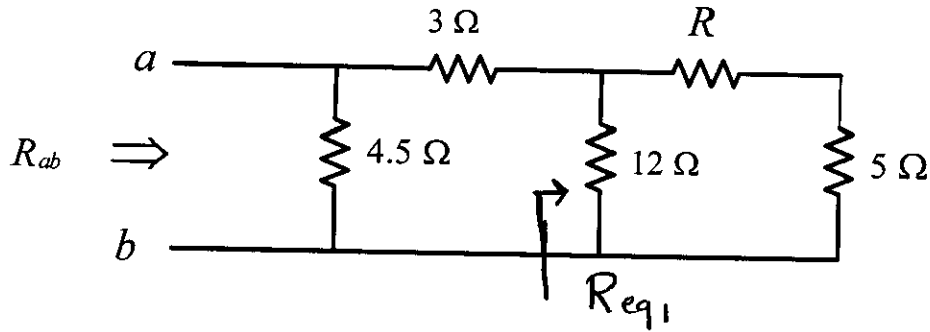

Find the resistant  $R$  such that the equivalent resistor  $R_{ab}$  equal  $3 \Omega$ ?

$$\begin{aligned} R_{eq1} &= 12 \parallel (R + 5) \\ &= \frac{12(R + 5)}{12 + R + 5} = \frac{12R + 60}{17 + R} \end{aligned}$$

$$\frac{1}{R_{ab}} = \frac{1}{4.5} + \frac{1}{3 + R_{eq1}}$$

$$\frac{1}{3} = \frac{1}{4.5} + \frac{1}{3 + \frac{12R + 60}{R + 17}}$$

$$\frac{1}{3} - \frac{1}{4.5} = \frac{R + 17}{3R + 51 + 12R + 60}$$


$$0.1111 = \frac{R + 17}{15R + 111}$$

$$\Rightarrow 1.666R + 12.333 = R + 17$$

$$0.666R = 4.6667$$

$$\Rightarrow R = 7 \Omega$$

Q4 (35)

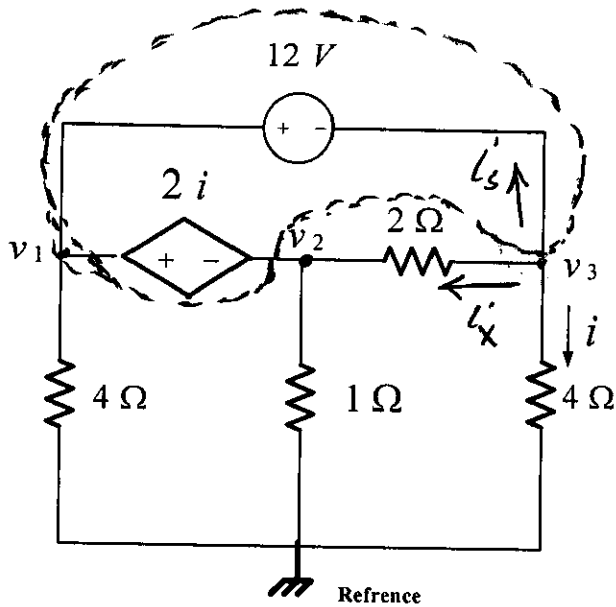

Using **nodal analysis** and **supper node principle** find the followings :

(a) The nodes voltages  $v_1, v_2, v_3$  ?

(b) The power absorbed or delivered by the independent voltage source ?

(a) Kcl on super node :

$$\frac{v_1}{4} + \frac{v_2}{1} + \frac{v_2 - v_3}{2} + \frac{v_3 - v_2}{2} + \frac{v_3}{4} = 0$$

$$\Rightarrow v_1 + 4v_2 + v_3 = 0 \quad \text{--- (1)}$$

$$v_1 - v_3 = 12 \quad \text{--- (2)}$$

$$v_1 - v_2 = 2i = 2 \frac{v_3}{4} = \frac{v_3}{2}$$

$$\Rightarrow v_1 - 2v_2 - \frac{v_3}{2} = 0 \Rightarrow 2v_1 - 2v_2 - v_3 = 0 \quad \text{--- (3)}$$

$$\Rightarrow \begin{bmatrix} 1 & 4 & 1 \\ 1 & 0 & -1 \\ 2 & -2 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 12 \\ 0 \end{bmatrix}$$

Solving  $v_1 = -3 \text{ V} \quad v_2 = 4.5 \text{ V} \quad v_3 = -15 \text{ V}$

OR  $V_1 - V_2 = 2i = 2 \frac{V_3}{4} = \frac{V_3}{2} = \frac{-12 + V_1}{2}$

$$\Rightarrow V_1 - 2V_2 = -12$$

$$\begin{bmatrix} 1 & 4 & 1 \\ 1 & 0 & -1 \\ 1 & -2 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 12 \\ -12 \end{bmatrix}$$

Solving  $V_1 = -3V$   $V_2 = 4.5V$   $V_3 = -15V$

(b)  $i_x = \frac{V_3 - V_2}{2} = \frac{-15 - 4.5}{2} = -9.75 A$

$$i_s + i_x + i = 0$$

$$i_s = -(i_x + i) = -(9.75 + -\frac{15}{4}) = 13.5 A$$

$$P_{12V} = -(12)(13.5) = -162 W$$

$\Rightarrow$  delivering power