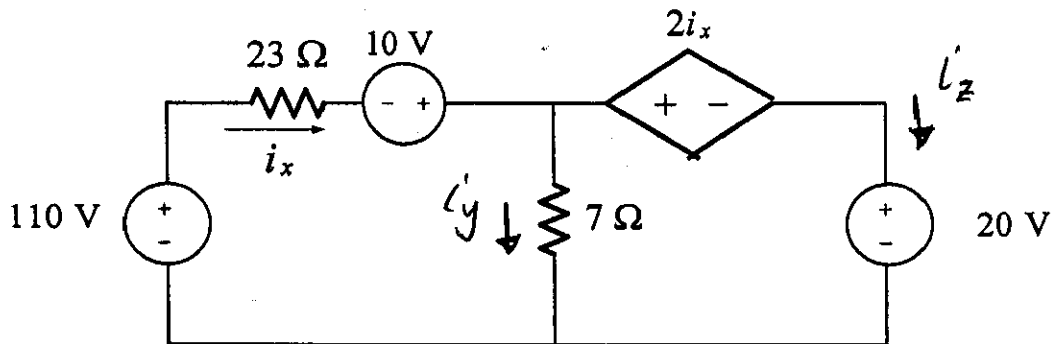


EE 201-02-Winter 2011(102)  
QZ1

Sec	Ser	ID	Name
			KEY



For the circuit shown above, Find the power associated with the 20 V source and indicate if the power is absorbed or delivered by the source

$$P_{20V} = 20 i_z \Rightarrow \text{find } i_z$$

$$\underline{\text{KCL}} \quad i_z = i_x - i_y \Rightarrow \text{find } i_x, i_y$$

$$\underline{\text{KVL}}: \quad -110 + 23i_x - 10 + 2i_x + 20 = 0$$

$$\Rightarrow i_x = 4 \text{ A}$$

$$\underline{\text{KVL}}: \quad -7i_y + 2i_x + 20 = 0$$

$$-7i_y + 2(4) + 20 = 0$$

$$\Rightarrow i_y = 4$$


$$\Rightarrow i_z = 4 - 4 = 0$$

$$\Rightarrow P_{20V} = 20(0) = 0 \text{ W}$$

neither absorbed  
or delivered.

EE 201-01-Winter 2011(102)  
QZ1

Sec	Ser	ID	Name
			KEY

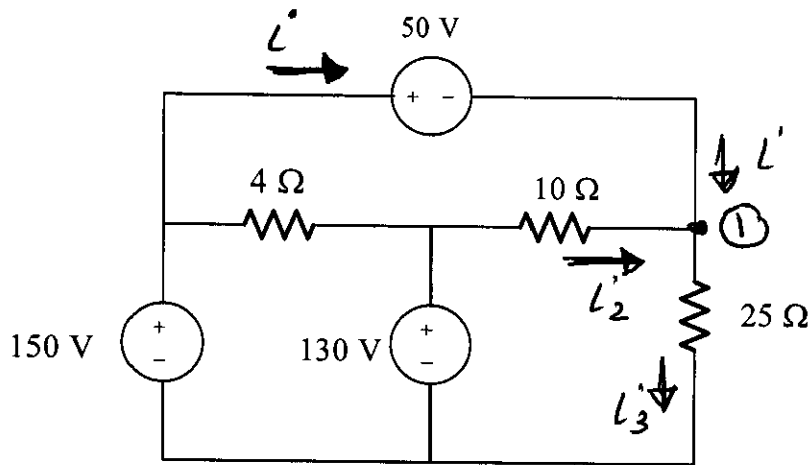

For the circuit shown above, Find the power associated with the 50 V source and indicate if the power is absorb or deliver by the source

$$P_{50V} = 50 i' \Rightarrow \text{find } i'$$

$$\underline{\text{KCL at (1)}} \quad i' = l'_3 - l'_2 \Rightarrow \text{find } l'_3, l'_2$$

$$\underline{\text{KVL:}} \quad -150 + 50 + 25l'_3 = 0 \Rightarrow l'_3 = 4 \text{ A}$$

$$\underline{\text{KVL:}} \quad -130 + 10l'_2 + 25l'_3 = 0 \Rightarrow l'_2 = 3 \text{ A}$$

$$\Rightarrow i' = 4 - 3 = 1 \text{ A}$$

$$\Rightarrow P_{50V} = (50)(1) = 50 \text{ W absorbed}$$