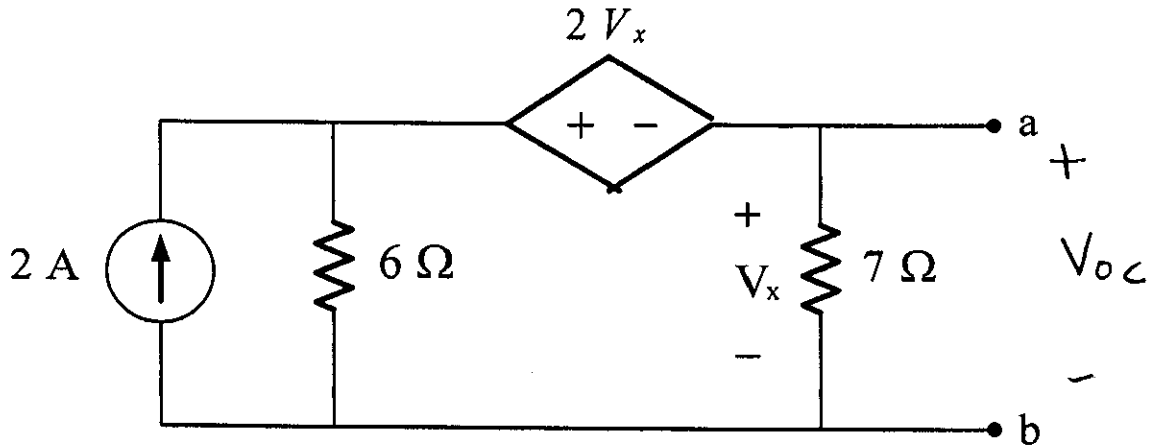


EE 201-01-Winter 2011(102)  
QZ1


Sec	Ser	ID	Name
-----	-----	----	------



For the circuit shown above, find Thevenin equivalent between terminals **a** and **b**?

Finding  $V_{oc}$

method ① source transformation

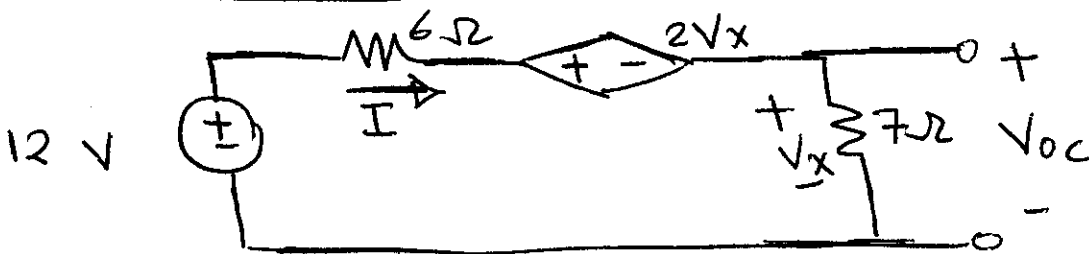

KVL  $-12 + 6I + 2V_x + V_x = 0$


$$I = \frac{V_x}{7}$$

$$\Rightarrow -12 + 6\left(\frac{V_x}{7}\right) + 3V_x = 0$$

$$\Rightarrow V_x = \frac{28}{9} = V_{oc}$$

continue  $\Rightarrow$

method (2) Nodal Method

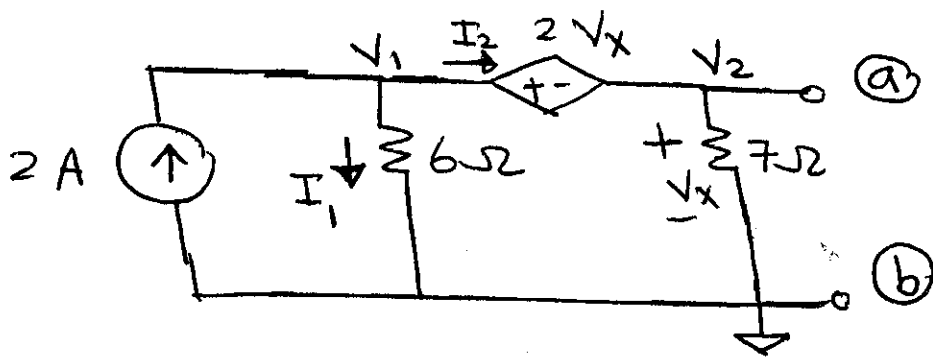



$$V_2 = V_x \quad V_1 - V_2 = 2V_x \Rightarrow V_1 = 3V_x$$

KCL  $2 = I_1 + I_2 = \frac{V_1}{6} + \frac{V_2}{7} = \frac{3V_x}{6} + \frac{V_x}{7}$


$$\Rightarrow V_x = \frac{28}{9} \text{ V} = V_{oc}$$

Finding Rth

method 1 Find  $I_{sc} \Rightarrow R_{th} = \frac{V_{oc}}{I_{sc}}$

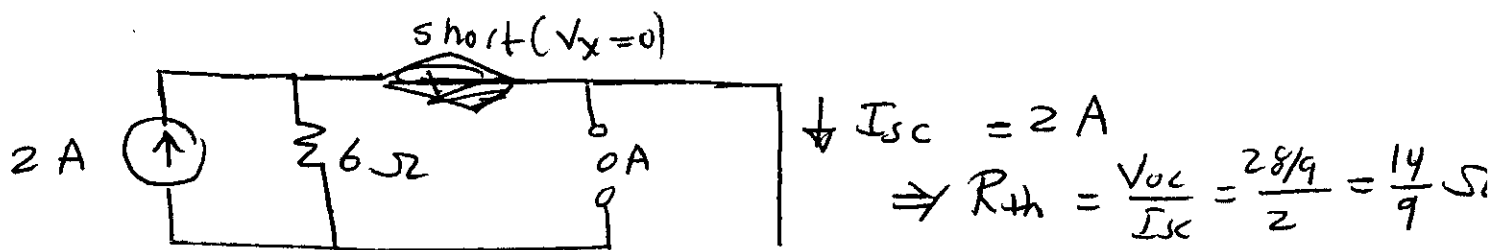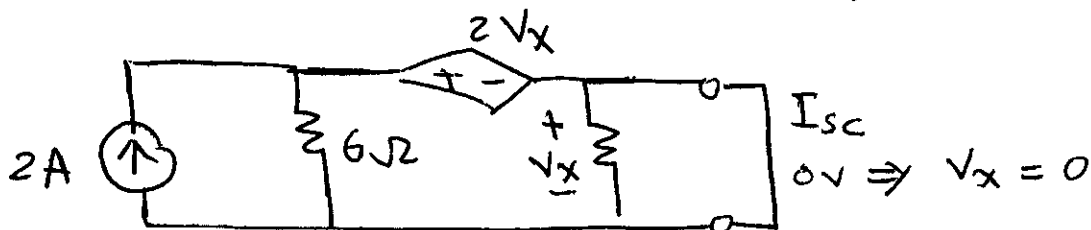

method 2

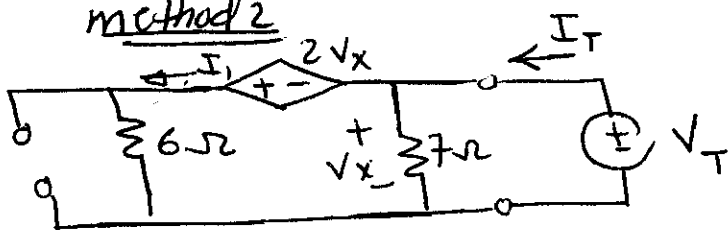

KVL  $-2V_x + 6I_1 - V_x = 0$

$$V_x = V_T$$


$$\Rightarrow I_1 = \frac{V_T}{2}$$

KCL  $I_T = \frac{V_x (= V_T)}{7} + I_1 = \frac{V_T}{7} + \frac{V_T}{2} = \frac{9}{14} V_T$

$$\Rightarrow R_{th} = \frac{V_T}{I_T} = \frac{14}{9} \Omega$$

EE 201-02-Winter 2011(102)  
QZ1

Sec	Ser	ID	Name	KEY
-----	-----	----	------	-----

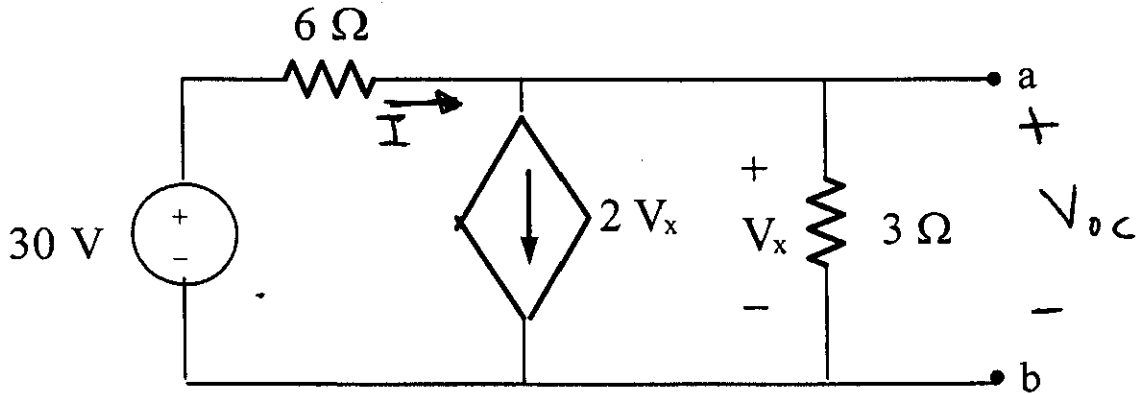

For the circuit shown above, find Thevenin equivalent between terminals **a** and **b** ?

$$V_{oc} = V_x$$

KCL  $I = 2V_x + \frac{V_x}{3}$



KVL  $-30 + 6I + V_x = 0$

$$-30 + 6 \left[ 2V_x + \frac{V_x}{3} \right] + V_x = 0$$

$$\Rightarrow V_x = 2V = V_{oc}$$

another solution

source transformation

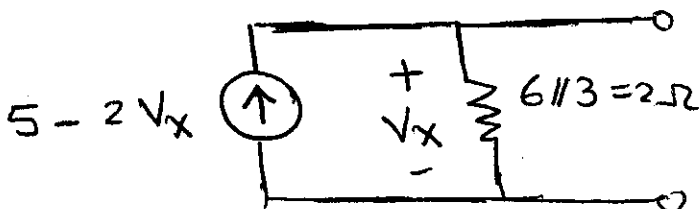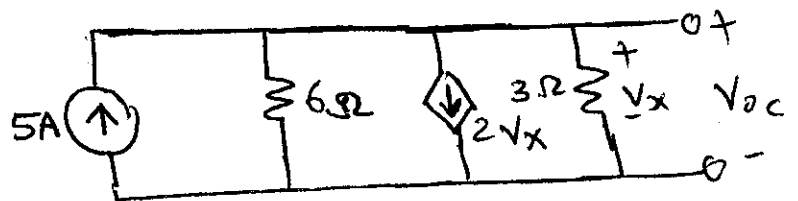


$$V_x = 2(5 - 2V_x)$$


$$\Rightarrow V_x = 2V = V_{oc}$$
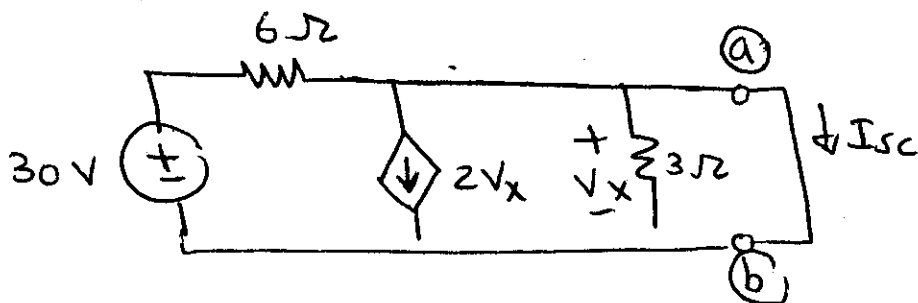
# Finding $R_{th}$

method 1 Find  $I_{sc} \Rightarrow R_{th} = \frac{V_{oc}}{I_{sc}}$



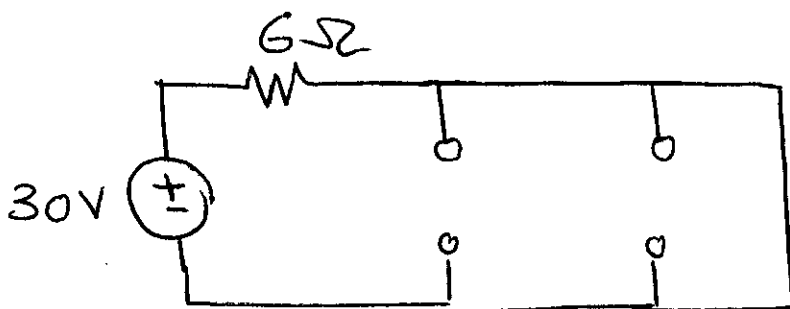
short a, b  $\Rightarrow V_x = 0$   
 $\Rightarrow I_{3\Omega} = \frac{V_x}{3} = 0A$  (open)  
 $2V_x = 0 \Rightarrow$  open




$I_{sc} = \frac{30}{6} = 5A$

$\Rightarrow R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{2}{5} \Omega$

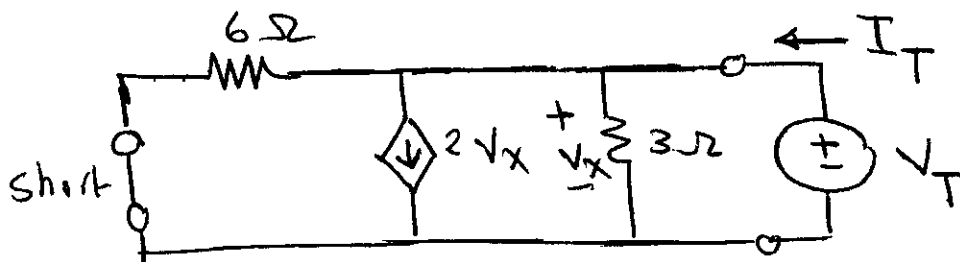method 2 deactivate independent sources  
 apply test voltage.



$R_{th} = \frac{V_T}{I_T}$

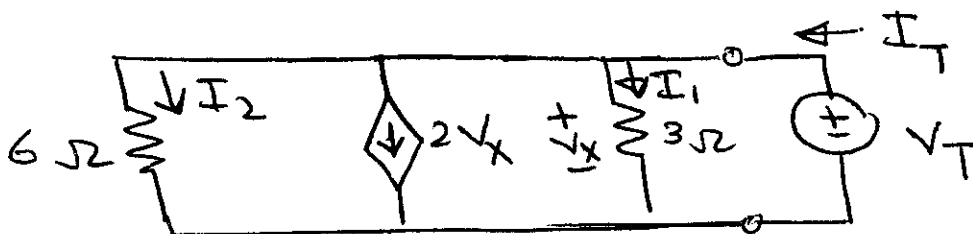

$V_x = V_T$

$$I_T = I_1 + 2V_x + I_2 = \frac{V_x}{3} + 2V_x + \frac{V_x}{6}$$

$$= \frac{V_T}{3} + 2V_T + \frac{V_T}{6}$$

Solve for  $\frac{V_T}{I_T} = R_{th} = \frac{2}{5} \Omega$