

$$6.6-1 \quad (a) P_{AV} = \frac{1}{2} \times 10 \times 2 \cos(30 + 60) = 0 \text{ W}$$

$$(b) P_{AV} = \frac{1}{2} \times 20 \times 5 \cos(30 - 45) = 48.3 \text{ W}$$

$$(c) P_{AV} = \frac{1}{2} \times 8 \times 5 \cos(-35 + 80) = 14.14 \text{ W}$$

$$(d) P_{AV} = \frac{1}{2} \times 25 \times 10 \cos(45 - 60) = 120.74 \text{ W}$$

6.6-2

$$\hat{I} = \frac{10 \angle 30^\circ}{3 + j6 - j3} = \frac{10}{3\sqrt{2}} \angle -15^\circ$$

$$P_{AV} = \frac{1}{2} |I|^2 3 = 8.33 \text{ W}$$

$$P_{AV} = \frac{1}{2} \times 10 \times \frac{10}{3\sqrt{2}} \cos(30 + 15) = 8.33 \text{ W}$$

6.6-3

$$\hat{V} = \frac{5 \angle -45^\circ}{\frac{1}{2} + j8 + j3 - j2} = \frac{5 \angle -45^\circ}{\frac{5}{6} + j \frac{3}{8}} = 5.47 \angle -69.23^\circ$$


$$P_{AV} = \frac{1}{2} \times 5 \times 5.47 \cos(-45 + 69.23) = 12.47 \text{ W}$$

$$P_{AV_{2\Omega}} = \frac{1}{2} \frac{101^2}{2} = 7.48 \text{ W} \quad P_{AV_{3\Omega}} = \frac{1}{2} \frac{101^2}{3} = 4.99 \text{ W}$$

$$P_{AV} = P_{AV_{2\Omega}} + P_{AV_{3\Omega}}$$

6.6-13

$5 \angle 30^\circ$

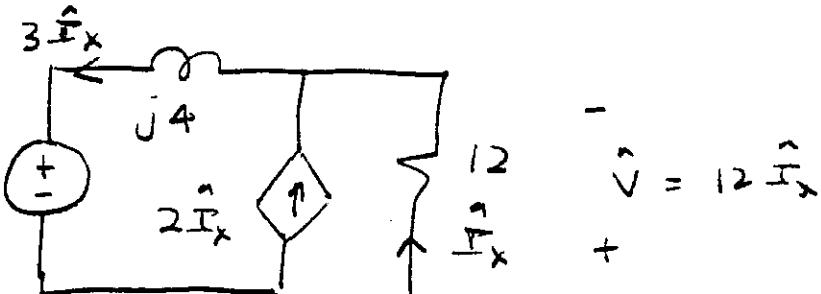

$$\hat{V} = 12 \hat{I}_x$$

$$5 \angle 30^\circ = -j4(3\hat{I}_x) - 12\hat{I}_x \quad \therefore \hat{I}_x = -\frac{5 \angle 30^\circ}{12 + j4}$$

$$P_{AV} = \frac{1}{2} \times 5 \times 3 (-0.29) \cos(30 + 15) = -0.29 \angle -15^\circ$$

$$= \boxed{1.56 \text{ W}} \quad = P_{AV_{12\Omega}} = \frac{1}{2} |1\hat{I}_x|^2 12 = 0.5 \text{ W}$$

$$+ P_{AV} = \frac{1}{2} \times |2\hat{I}_x| |\hat{V}| \cos(-15 + 15) \\ \text{cont source} = 1.01 \text{ W} \quad \checkmark$$

6.6-14

$$V_{rms} = \sqrt{\frac{1}{2} \left[\int_0^1 (5t)^2 dt + \int_1^2 (5)^2 dt \right]}$$

$$= \sqrt{\frac{1}{2} \left[\frac{25}{3} + 25 \right]} = \boxed{4.08 \text{ V}}$$

$$P_{AV} = \frac{V_{rms}^2}{Z} = \boxed{8.33 \text{ W}}$$

6.6-15


$$V_{rms} = \sqrt{\frac{1}{4} \left[\int_0^2 (2t)^2 dt + \int_2^4 (-2(t+8))^2 dt \right]}$$

$$P_{AV} = \frac{V_{rms}^2}{Z} = \sqrt{\frac{1}{4} \left[\left. \frac{4t^3}{3} \right|_0^2 + \left(\frac{4t^3}{3} - \frac{32t^2}{2} + 64t \right)_2^4 \right]}$$

$$= \sqrt{\frac{1}{4} \left[\frac{32}{3} + (85.33 - 74.67) \right]}$$


$$= \boxed{2.31 \text{ V}}$$

6.6-21

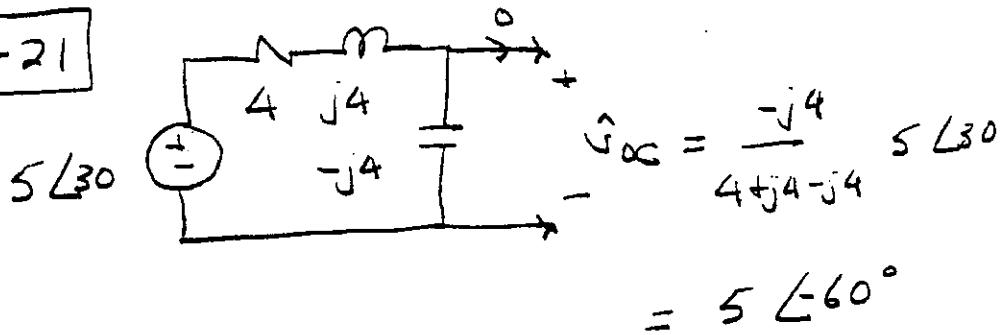


$$\hat{Z}_{TH} = \frac{(4+j4)(-j4)}{4+j4-j4} = 4-j4$$
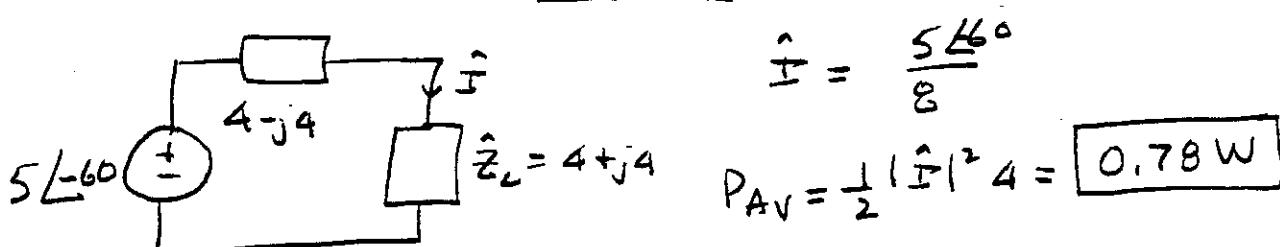
$$\therefore \hat{Z}_L = \hat{Z}_{TH}^* = 4+j4 \Omega$$




6.6-22

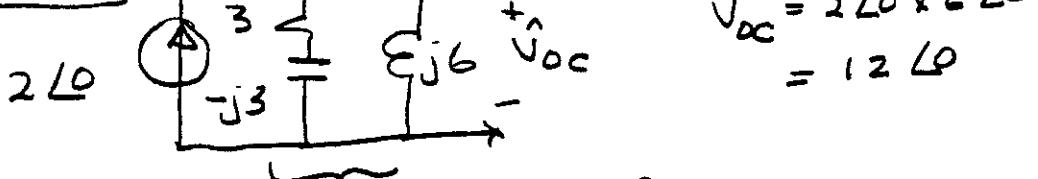


$$\frac{(3-j3)(j6)}{3-j3+j6} = \frac{18+j18}{3+j3} = 6\angle 0^\circ$$
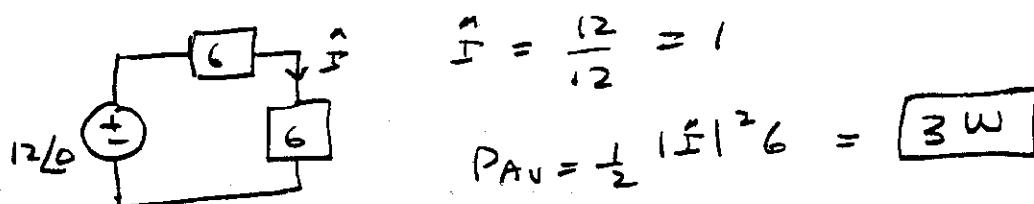
$$\hat{Z}_{TH} = 6\angle 0^\circ \quad \therefore \hat{Z}_L = \hat{Z}_{TH}^* = 6\angle 0^\circ$$



6.9-3

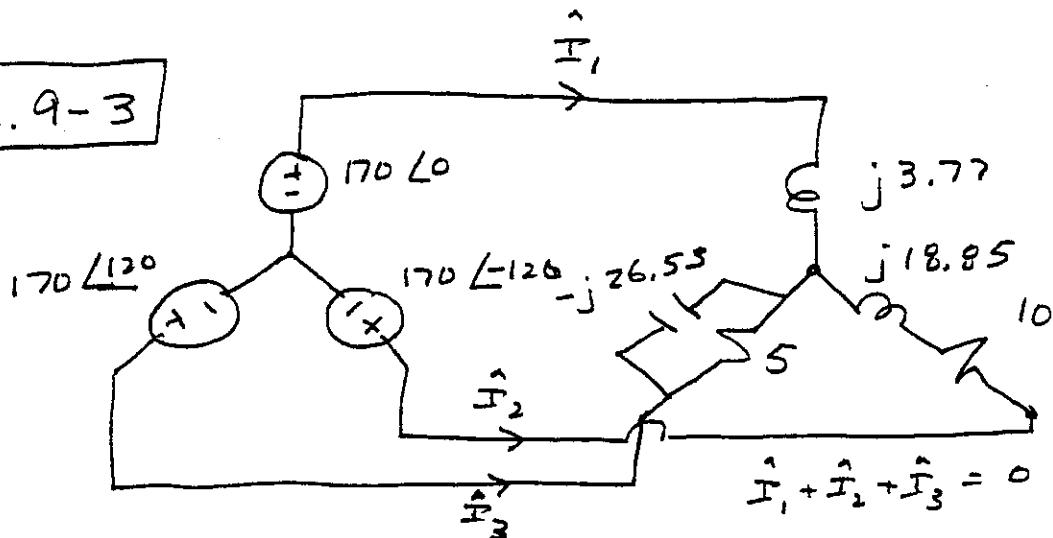

$$170 L 0 - 170 L 120 = j 3.77 \hat{I}_1 - (10 + j 18.85) \hat{I}_2 - \hat{I}_1 - \hat{I}_2$$

$$170 L 0 - 170 L 120 = j 3.77 \hat{I}_1 - \underbrace{51(-j 26.53)}_{4.91 L -10.67} \hat{I}_3 \\ = 4.83 - j 0.91$$

$$\therefore j 3.77 \hat{I}_1 - 21.34 L 62.05 \hat{I}_2 = 294.45 L 30 \\ = 294.45 L -30$$

$$\begin{vmatrix} (4.83 + j 2.86) \hat{I}_1 + (4.83 - j 0.91) \hat{I}_2 \\ 294.45 L 30 - 21.34 L 62.05 \\ 294.45 L -30 (4.83 - j 0.91) \end{vmatrix} \\ \hat{I}_1 = \frac{\begin{vmatrix} j 3.77 - 21.34 L 62.05 \\ (4.83 + j 2.86) (4.83 - j 0.91) \end{vmatrix}}{\begin{vmatrix} j 3.77 - 21.34 L 62.05 \\ (4.83 + j 2.86) (4.83 - j 0.91) \end{vmatrix}} \\ = 3.94 L 151.03$$

$$= 26.89 - j 48.96 \\ = 55.86 L -61.22^{\circ}$$

$$\hat{I}_2 = -3.45 + j 1.91, \quad \hat{I}_3 = -\hat{I}_1 - \hat{I}_2 = -23.44 + j 47.05 = 52.57 L 116.48$$

$$i_1(t) = 55.86 \sin(120\pi t - 61.22^{\circ}) A$$

$$i_2(t) = 3.94 \sin(120\pi t + 151.03^{\circ}) A$$

$$i_3(t) = 52.57 \sin(120\pi t + 116.48) A$$


$$P_{AV_1} = \frac{1}{2} 170 \times 55.86 \cos(0 + 61.22^{\circ}) \\ = 2285.96 W$$

$$P_{AV_2} = \frac{1}{2} 170 \times 3.94 \cos(-120 - 151.03) \\ = 6.02 W$$

$$P_{AV_3} = \frac{1}{2} 170 \times 52.57 \cos(120 - 116.48) \\ = 4460.02 W$$

$$P_{AV} = 6752 W$$

6.9-4

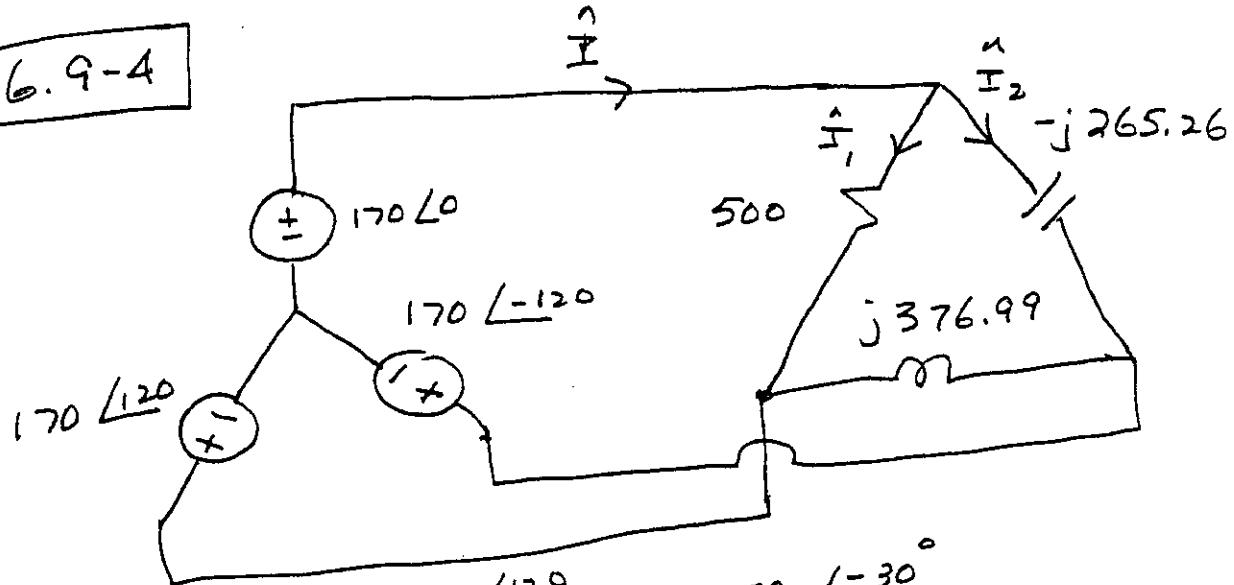

$$\hat{I}_1 = \frac{170\angle 0^\circ - 170\angle -120^\circ}{500} = 0.59\angle -30^\circ$$


$$\begin{aligned}\hat{I}_2 &= \frac{170\angle 0^\circ - 170\angle -120^\circ}{-j265.26} = \frac{294.45\angle 30^\circ}{265.26\angle -90^\circ} \\ &= 1.11\angle 120^\circ\end{aligned}$$

$$\begin{aligned}\hat{I} &= \hat{I}_1 + \hat{I}_2 \\ &= 0.67\angle 93.78^\circ\end{aligned}$$

$$\therefore i(t) = 0.67 \cos(120\pi t + 93.78^\circ) A$$

$$\begin{aligned}P_{AV} &= \frac{1}{2} |\hat{I}|^2 R \\ &= 87.03 W\end{aligned}$$

Extra Problem

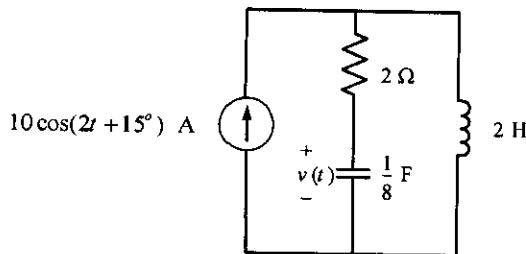


Using the complex power concept find the followings:

- The complex power absorb by the load ?
- The Average power absorb by the load ?
- Power factor of the load ?
- Verify $\theta_{\text{Complex Power}} = \theta_{\text{power factor}} = \theta_{\text{Impedance}}$

Solution

(a)
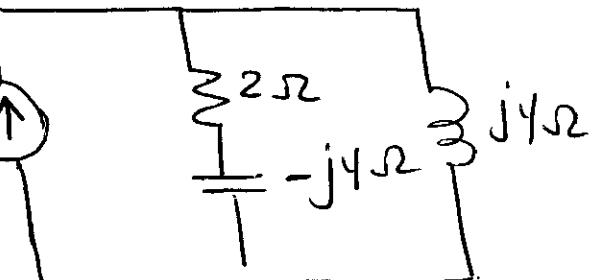
$$\begin{aligned} Z_L &= (j4)(2-j4) \quad 10 \angle 15^\circ A \\ &= \frac{j4(2-j4)}{j4+2-j4} \\ &= 8 + j4 \Omega \end{aligned}$$



$$\begin{aligned} S_{\text{load}} &= \frac{1}{2} Z_{\text{load}} |10 \angle 15^\circ|^2 = \frac{1}{2}(8+j4)(10)^2 \\ &= 400 + j200 \text{ VA} \end{aligned}$$

$$(b) P_{\text{load}} = \text{Re}[S_{\text{load}}] = 400 \text{ W}$$

$$(c) \theta_{S_{\text{load}}} = \tan^{-1}\left(\frac{200}{400}\right) = 26.56^\circ$$

$$\text{pf} = \cos(26.56) = 0.89 \text{ lagging}$$

$$(d) \theta_Z = \tan^{-1}\left(\frac{4}{8}\right) = 26.56^\circ = \theta_{S_{\text{load}}} = \theta_{\text{pf}}$$