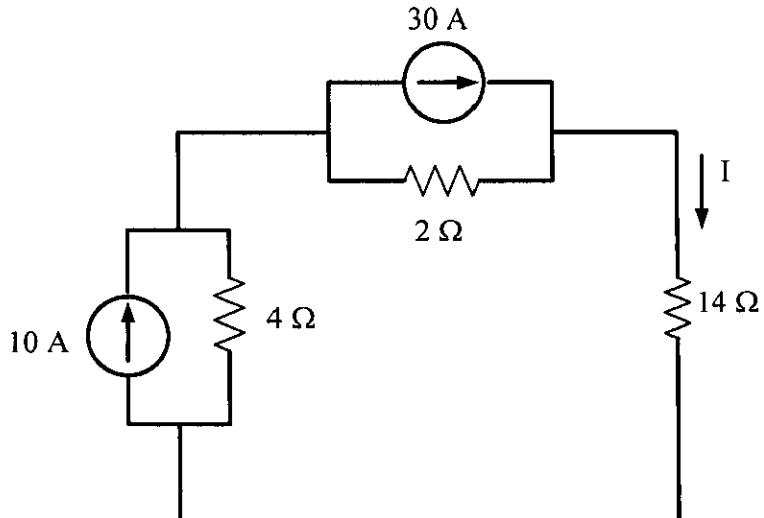


EE 201 Exam II -KEY Solution

Attention:

There are two version for the answer sequence for problems 3,4,5 indicated as version (*) and version (**) which are printed on the cover of the exam

Problem #1 (3)



I = 5A

(3)


OR

I = -5A

(1.5)

Find the current I ?

Source Transformation

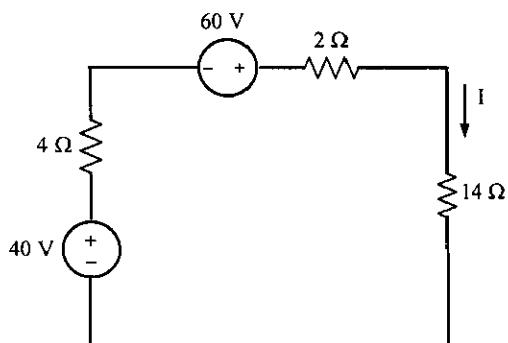

KVL

$$-40 + 4I - 60 + 2I + 14I = 0 \Rightarrow 20I = 100 \Rightarrow I = 5 \text{ A}$$

For each voltage the following
50% for the correct deactivation
100 % for the correct answer

Problem #2 (6)

Vx	Ans.	Marks
+6	2/2	
-6	1/2	
else	0/2	
12V		

Vx	Ans.	Marks
+6	3/3	
+6	1.5/3	
else	0/3	

Vx	Ans.	Marks
0	1/1	
else	0/1	

The voltages are :

②


$$V_x = 6V$$

③

$$V_x = -6V$$

①

$$V_x = 0V$$

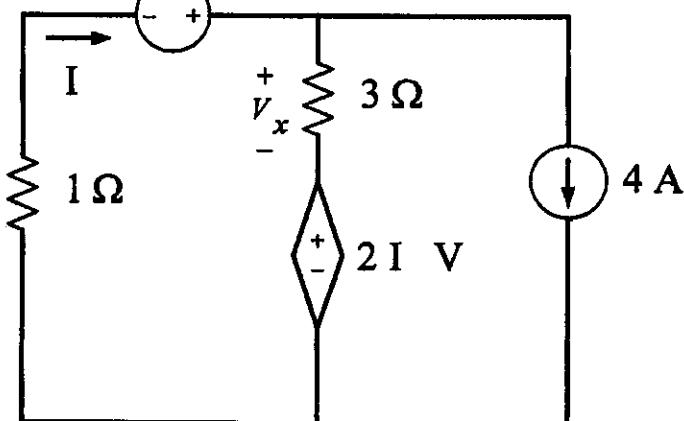


Using the principle of superposition find all voltage components

of V_x and find the total V_x and put all the values on the box

First, turn the current source off:

(2 pts)

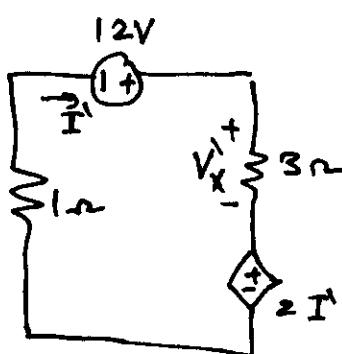

Apply KVL:


$$+1 \cdot I' - 12 + 3 \cdot I' + 2 \cdot I' = 0$$

$$\therefore I' = 2A$$

$$V_x' = 3 \cdot I' = 3 \cdot 2 = 6V$$

Then, turn the independent voltage source off:

(3 pts)

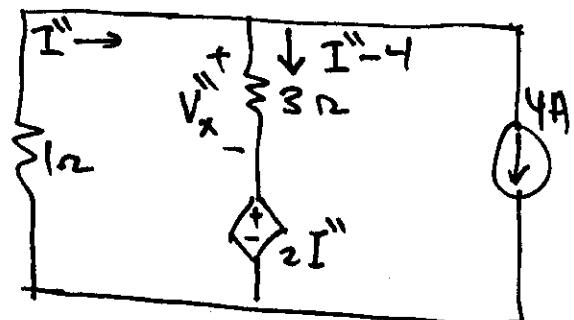

Apply KVL on the left loop:

$$I'' + 3(I'' - 4) + 2I'' = 0$$

$$6I'' = 12$$

$$I'' = 2A$$


$$V_x'' = 3(I'' - 4) = 3(2 - 4) = -6V$$

$$(1 pt) \rightarrow V_x = V_x' + V_x'' = 6 + (-6) = 0V$$

Summation is 1 point but with right polarity

VERSION (*)

Problem #3 (4)

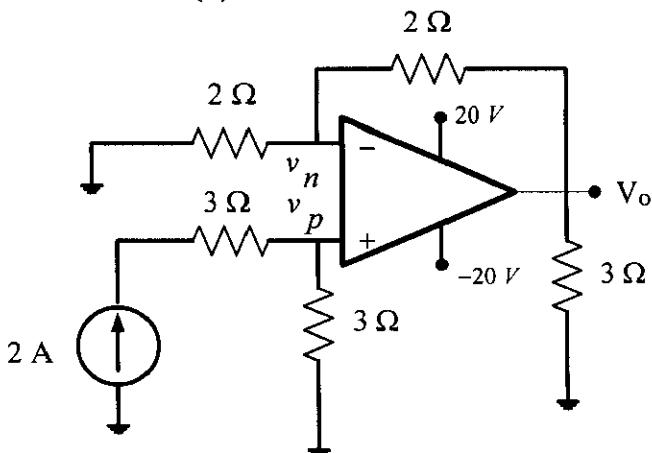

For the ideal Op Amp circuit shown above find the voltage V_o ?
 Version (*)


(a)	6
(b)	-6
(c)	20
(d)	-20
(e)	12
(f)	-12
(g)	8

→ ④
 → ②

$$v_p = 3(2) = 6 \text{ V} = v_n$$

KCL at (-) terminal

$$\frac{v_n - 0}{2} + \frac{v_n - v_o}{2} = 0 \Rightarrow v_o = 2v_n = 2(6) = 12 \text{ V}$$

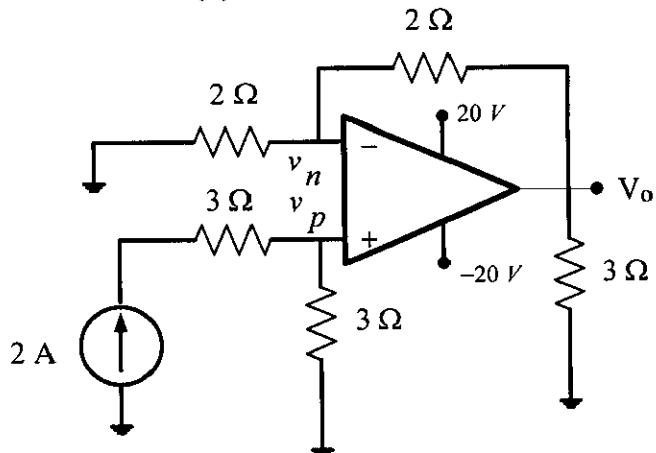
Problem #3 (4)

For the ideal Op Amp circuit shown above find the voltage V_o and circle the correct answer ?

(a)	8
(b)	12
(c)	-12
(d)	-20
(e)	20
(f)	-6
(g)	6

→ ④
OR
→ ②

Problem #4 (3)

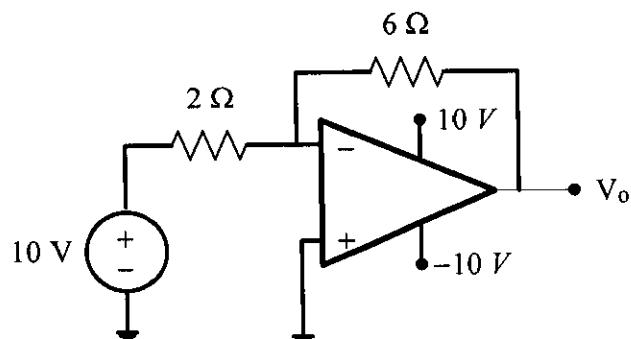

For the ideal Op Amp circuit shown above find the voltage V_o ?

(a)	-10	→ (3)
(b)	+10	
(c)	-30	
(d)	+30	
(e)	18	
(f)	-18	
(g)	20	


$$v_p = 0 = v_n$$

KCL at (-) terminal

$$\frac{0-10}{2} + \frac{0-v_o}{6} = 0 \Rightarrow v_o = -30$$

$$\Rightarrow v_o = -10 \text{ (Saturation) (a)}$$

Problem #4 (3)

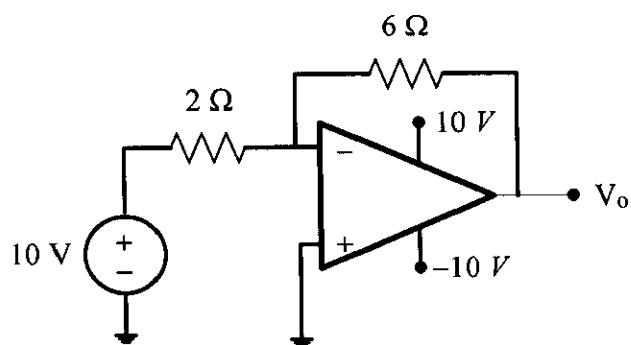

For the ideal Op Amp circuit shown above find the voltage V_o and circle the correct answer ?

(a)	-30
(b)	+30
(c)	7.5
(d)	-7.5
(e)	-10
(f)	10
(g)	2.5

→ ③

Version (*)


Problem #5 (5)

For the circuit shown, circle the correct answer

(1) $i_R(0.5)$ equals

- | |
|-----------------------|
| (a) 0.5A |
| (b) 0.125A |
| (c) 0.25 A |
| (d) 1.75A |
| (e) 1A |
| (f) -1A |
| (g) -0.5A |
| (h) none of the above |


→ ①

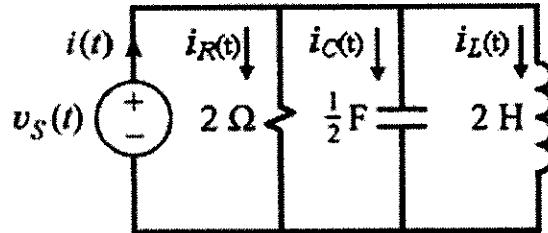

(2) $i_C(0.5)$ equals

- | |
|-----------------------|
| (a) 0.5A |
| (b) 0.125A |
| (c) 0.25 A |
| (d) 1.75A |
| (e) 1A |
| (f) -1A |
| (g) -0.5A |
| (h) none of the above |

→ ②

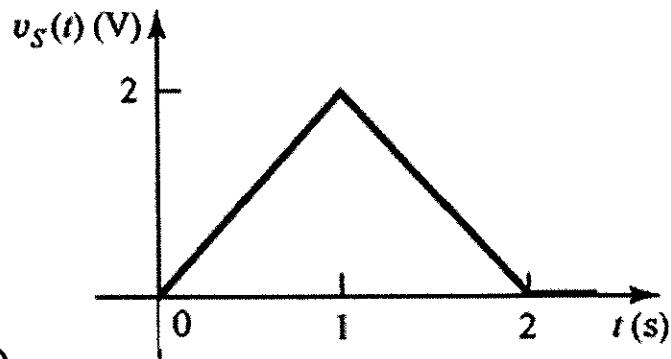

$$i_R(t) = \frac{v_s(t)}{2} \Rightarrow i_R(0.5) = 0.5 \text{ A}$$

$$i_C(t) = \frac{1}{2} \frac{d v_s(t)}{dt} = 1 \quad 0 < t < 1 \\ \Rightarrow i_C(0.5) = 1 \text{ A}$$

$$i_L(t) = \frac{1}{2} \int_{-\omega}^t v_s(\tau) d\tau = \frac{t^2}{2} \quad 0 \leq t \leq 1 \\ \Rightarrow i_L(0.5) = 0.125 \text{ A}$$

(3) $i_L(0.5)$ equals

- | |
|-----------------------|
| (a) 0.5A |
| (b) 0.125A |
| (c) 0.25 A |
| (d) 1.75A |
| (e) 1A |
| (f) -1A |
| (g) -0.5A |
| (h) none of the above |

→ ③

Version (**)


Problem #5 (5)

For the circuit shown, circle the correct answer

(1) $i_C(0.5)$ equals

- | |
|-----------------------|
| (a) 0.5A |
| (b) 0.125 |
| (c) 0.25 A |
| (d) 1.75A |
| (e) 1A |
| (f) -1A |
| (g) -0.5A |
| (h) none of the above |


→ ②

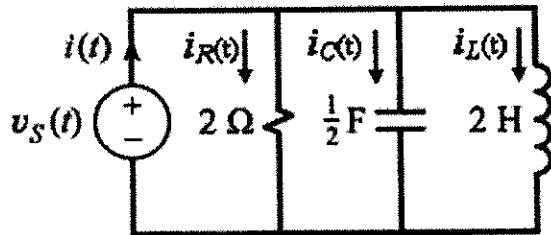

(2) $i_L(0.5)$ equals

- | |
|-----------------------|
| (a) 0.5A |
| (b) 0.125 |
| (c) 0.25 A |
| (d) 1.75A |
| (e) 1A |
| (f) -1A |
| (g) -0.5A |
| (h) none of the above |

→ ②

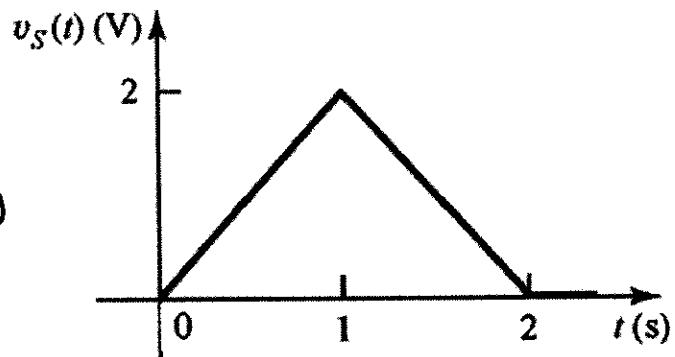


(3) $i_R(0.5)$ equals

- | |
|-----------------------|
| (a) 0.5A |
| (b) 0.125 |
| (c) 0.25 A |
| (d) 1.75A |
| (e) 1A |
| (f) -1A |
| (g) -0.5A |
| (h) none of the above |

→ ①

Problem #6 (9)

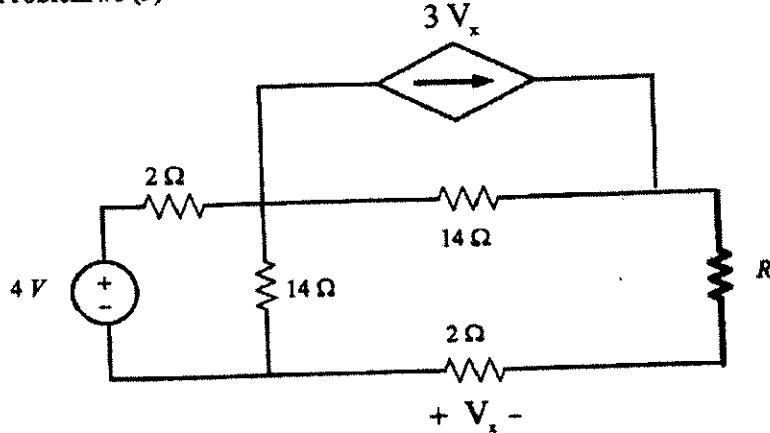

Find the maximum power absorbed by the load resistance R

Solution of Problem 6

The solution is in 3 parts:

Part1: finding V_{th}

In this part we have three options:

- a) 1 mark: If starts in the right direction by (Removing the load resistor) and (Calculating the open-voltage V_{oc} between the terminals) as shown in figure 1, Look at [Figure 1](#).
- b) 2 marks: if followed part (a) and found that $V_{th} = 3.5 \text{ V}$.
- c) Zero: if he did not start in the right direction

Part2: finding R_{th}

In this part we have three options:

- a) 2.5 marks: if starts in the right directions by one of the following options
 - i. [Figure 2a](#): Finding the Short circuit current I_{sc} then $R_{th} = V_{oc}/I_{sc}$.
 - ii. [Figure 2b](#): By deactivating the independent voltage source (4V) by short circuit then applying a test voltage source and calculate I_{ex} , then $R_{th} = V_{ex}/I_{ex}$.
 - iii. [Figure 2c](#): By deactivating the independent voltage source (4V) by short circuit then applying a test current source and calculate V_{ex} , then $R_{th} = V_{ex}/I_{ex}$.
 - iv. [Figure 2d](#): Some students might use source transformation.
- b) 5 marks: if he followed part (a) and found that $R_{th} = 101.75 \Omega$.
- c) Zero: if he did not start in the right direction.

Part3: finding maximum power

There are two options:

- a) 2 marks: if he wrote $P_{max} = \frac{V_{th}^2}{4R_{th}} = \frac{(3.5)^2}{4(101.75)} = 30.1 \text{ mW}$
- b) Zero: if he made a mistake in the maximum power expression.

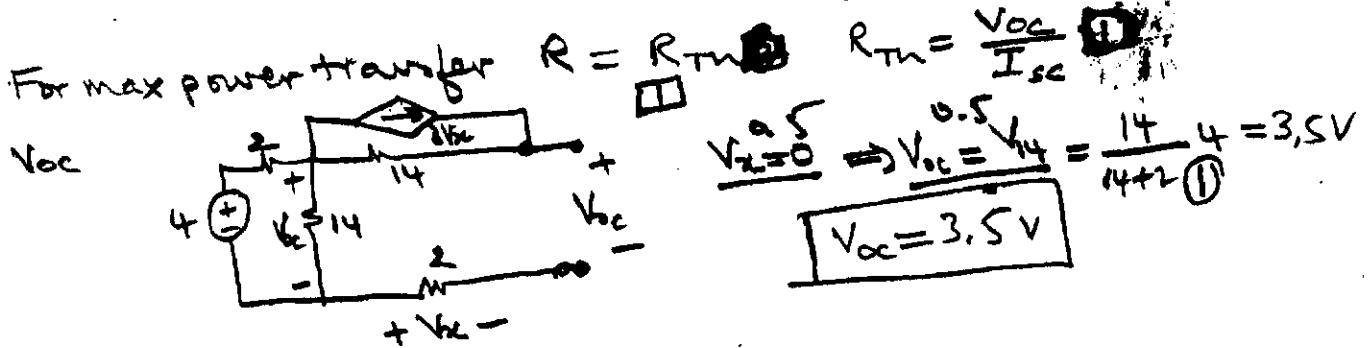


Figure 1: finding V_{oc}

I_{sc}

same pattern if mesh analysis is used here

$$\frac{V_2-4}{2} + \frac{V_2}{14} + \frac{V_2-V_1}{14} + 3(-V_1) = 0 \quad (1)$$

$$\frac{V_1}{2} + \frac{V_1-V_2}{14} + 3V_1 = 0 \quad (1)$$

$$7V_2 - 28 + V_2 + V_2 - V_1 - 42V_1 = 0$$

$$-43V_1 + 9V_2 = 28 \quad (1) \quad (3)$$

$$7V_1 + V_1 - V_2 + 42V_1 = 0$$

$$50V_1 - V_2 = 0 \quad V_2 = 50V_1 \quad (2)$$


$$(2) \text{ in } (1) \Rightarrow -43V_1 + 9(50V_1) = 28 \Rightarrow 407V_1 = 28 \quad V_1 = 0.0688$$

$$\therefore I_{sc} = \frac{V_1}{2} = 0.0344 \quad I_{sc} = 34.4 \text{ mA} \quad (4)$$

$$\therefore R_{TH} = \frac{3.5}{0.0344} = 101.75 \Omega \quad R = 101.75 \Omega$$

Figure 2a: finding R_{TH} using I_{sc} and previous V_{oc}

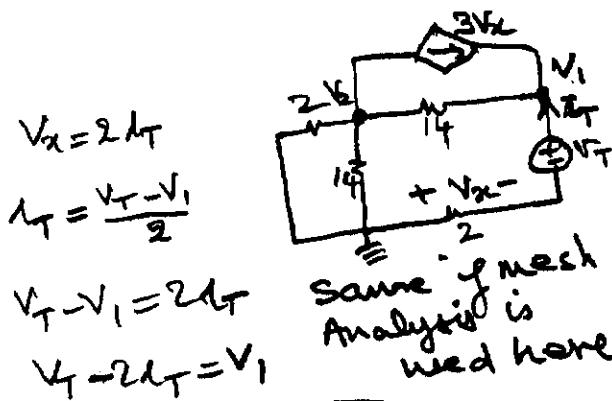For max power transfer $R = R_{TH}$ $R_m = \frac{V_T}{I_T}$ $V_{oc} = 3.5V$ 2
 $3Vx = 6I_T$



Or choose $V_T = 1V$
or put current
source $I_T = 1A$ and
find V_1
 $R_m = \frac{V_1}{I_T}$

$$\frac{V_2 + V_x}{2} + \frac{V_2 - V_1}{14} + 6I_T = 0 \quad (1)$$

$$\frac{V_1 - V_2}{14} - 6I_T - I_T = 0 \quad (1)$$

$$7V_2 + V_x + V_2 - V_1 + 84I_T = 0$$

$$9V_2 - V_1 = -84I_T$$

$$V_1 - V_2 = 7 \times 14 I_T$$

$$8V_2 = 14I_T$$

4

$$V_2 = V_1 - 98I_T$$

$$8(V_1 - 98I_T) = 14I_T \quad (1.5)$$

$$8(V_T - 2I_T - 98I_T) = 14I_T$$

$$8V_T - 800I_T = 14I_T$$


$$8V_T = 814I_T$$

$$\frac{V_T}{I_T} = \frac{814}{8} = \underline{\underline{101.75 \Omega}}$$

Figure 2b: finding R_{TH} using external voltage source

$R = R_m$ for max power transfer. $V_{oc} = 3.5V$ as before [2]

Rm: Apply current test

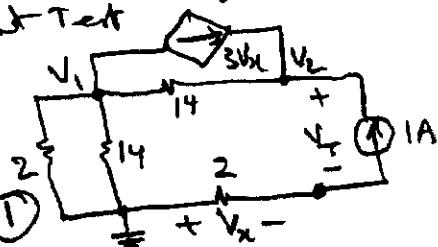

$$R_m = \sqrt{t}/\lambda \quad [1]$$

same if mesh Analysis
is used here.

$$\textcircled{1} \quad \text{node} \quad \frac{V_1}{2} + \frac{V_1}{14} + \frac{V_1 - V_2}{14} + 3V_3 = 0 \quad \textcircled{1}$$

$$\text{node } 2 \quad 3V_2 + 1 + \frac{V_1 - V_2}{14} = 0 \quad (1) \quad V_2 = 2 \times 1 = 2 \text{ V}$$

$$\text{ode } \begin{aligned} ① \quad 7V_1 + V_1 + V_1 - V_2 + 6 \times 14 &= 0 \Rightarrow 9V_1 - V_2 = -98 \quad \Rightarrow 8V_1 = 112 \\ V_1 - V_2 &= -7 \times 14 = -98 \\ V_2 &= V_1 + 98 = \frac{14}{8} + 98 \\ -V_2 + V_T - V_2 &= 0 \quad V_T = V_2 + V_X = \frac{14}{8} + 98 + 2 \\ \therefore R_{TH} &= \frac{14}{8} + 100 = \underline{\underline{101.75\Omega}} \end{aligned}$$

Figure 2c: finding R_{th} using external current source

For Smart Students

$$T = T \quad \square$$

$$R = \frac{V_T}{I} + V_x -$$

$$V_{\infty} = 3.5$$

Apply test current

Apply test current

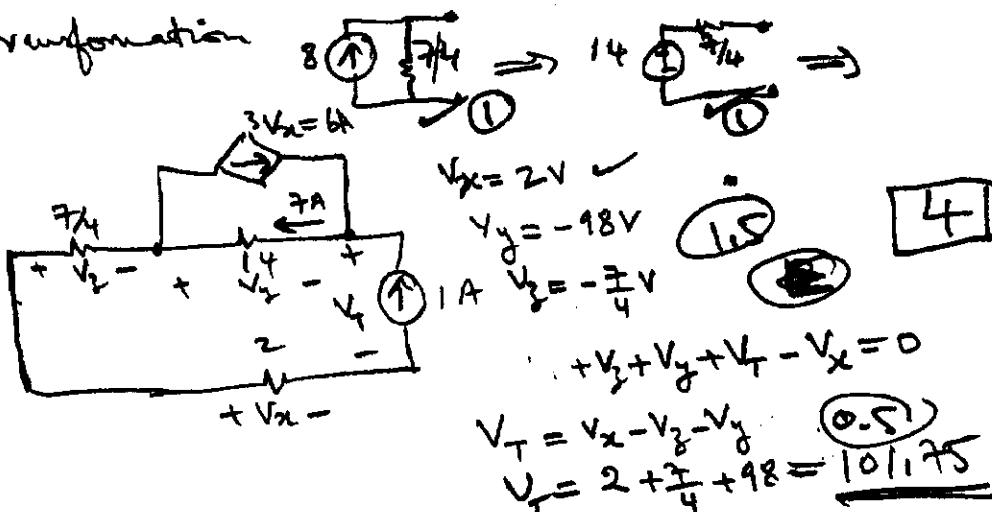


Figure 2d: finding R_{th} using source transformation