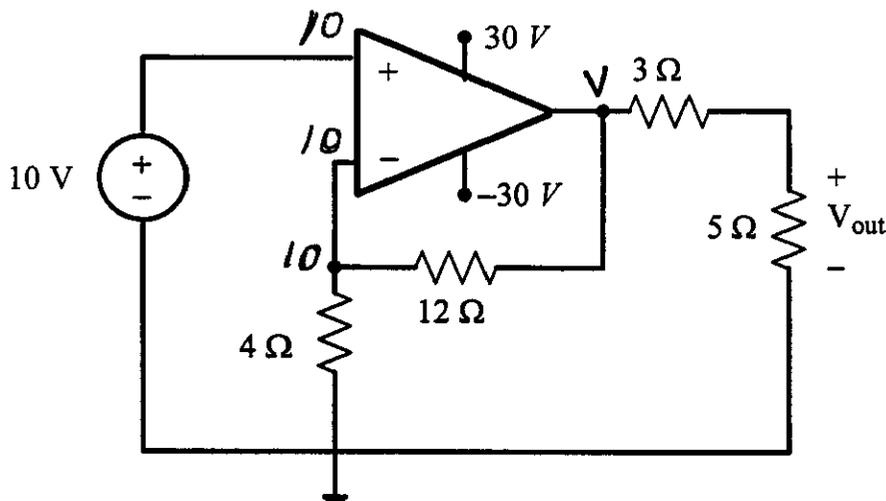


SER	ID	NAME	KEY
-----	----	------	-----



For the OP AMP circuit shown above find the followings :

(a)  $V_{out}$  ?

(b) If the power supply is changed from  $\pm 30$  to  $\pm 20$  what is  $V_{out}$  ?  
between a and b ?

(a) kd  $\frac{10}{4} + \frac{10 - v}{12} = 0 \Rightarrow 3(10) + 10 - v = 0$   
 $\Rightarrow v = 40 \Rightarrow$  saturation  $v = 30V$   
 $V_{out} = \frac{5}{3+5} 30 = \frac{150}{8} = 18.75 V$

(b) power supply  $\pm 20 \Rightarrow v = 20$   
 $V_{out} = \frac{5}{3+5} 20 = \frac{100}{8} = 12.5 V$