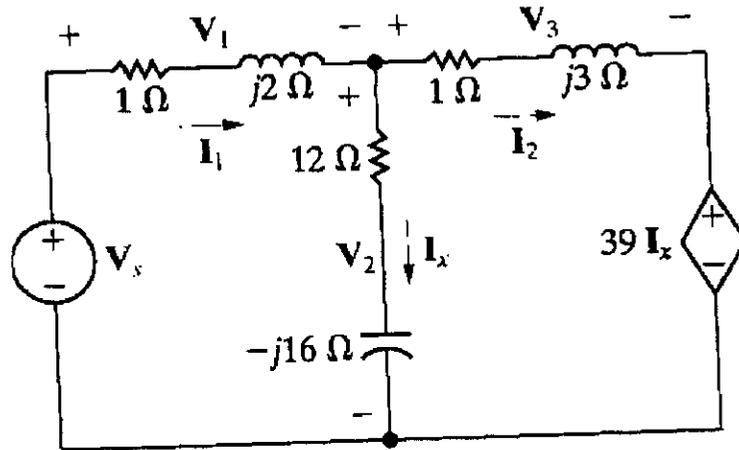


EE 201-01 – Fall 2011(111)
Quiz 7

SER	ID	NAME KEY
-----	----	----------



Example
10.7
P 398

$$V_s = 150 \angle 0^\circ \text{ V}$$

$$V_1 = (78 - j104) \text{ V} \quad I_1 = (-26 - j52) \text{ A}$$

$$V_2 = (72 + j104) \text{ V} \quad I_x = (-2 + j6) \text{ A}$$

$$V_3 = (150 - j130) \text{ V} \quad I_2 = (-24 - j58) \text{ A}$$

For the circuit shown above :

(a) Calculate the Complex power absorb by each impedance in the circuit?

(b) Calculate the Complex power deliver by each source in the circuit ?

(c) The power factor of the total impedance in the circuit and indicate if it is leading or lagging?

$$(a) \bar{S}_1 = \frac{1}{2} \bar{V}_1 \bar{I}_1^* = \frac{1}{2} (78 - j104) (-26 + j52) = 1690 + j3380 \text{ VA}$$

$$\bar{S}_2 = \frac{1}{2} \bar{V}_2 \bar{I}_x^* = \frac{1}{2} (72 + j104) (-2 - j6) = 240 - j320 \text{ VA}$$

$$\bar{S}_3 = \frac{1}{2} \bar{V}_3 \bar{I}_2^* = \frac{1}{2} (150 - j130) (-24 + j58) = 1970 + j5910 \text{ VA}$$

$$(b) \bar{S}_s = -\frac{1}{2} \bar{V}_s \bar{I}_1^* = -\frac{1}{2} (150) (-26 + j52) = 1950 - j3900 \text{ VA}$$

$$\bar{S}_x = \frac{1}{2} (39 \bar{I}_x) (\bar{I}_2^*) = \frac{1}{2} (-78 + j234) (-24 + j58) = -5850 - j5070 \text{ VA}$$

$$(c) \bar{S}_{\text{Total}} = \bar{S}_1 + \bar{S}_2 + \bar{S}_3 = 3900 + j8970 \text{ VA} = 390 \sqrt{629} \angle 66.50^\circ$$

$$PF = \cos(66.50^\circ) = 0.4 \text{ lagging}$$