

$$i_2 = 2A \quad (\text{by inspection})$$

$$i_1 = -\frac{V_1}{4} = -\frac{1}{4} [2(i_2 - i_1)]$$

$$i_1 = -\frac{1}{4} [2(2 - i_1)]$$

$$= -\frac{1}{2} [2 - i_1] = \frac{1}{2} [i_1 - 2]$$

$$2i_1 = i_1 - 2 \quad \Rightarrow \quad \boxed{i_1 = -2A}$$

KVL



$$V_{out} - V_1 + 2i_1 = 0$$

$$V_{out} = V_1 - 2i_1 = 2(2+2) - 2(-2)$$

$$= 8 + 4 = \boxed{12V}$$


Finding R_{th}

(2)

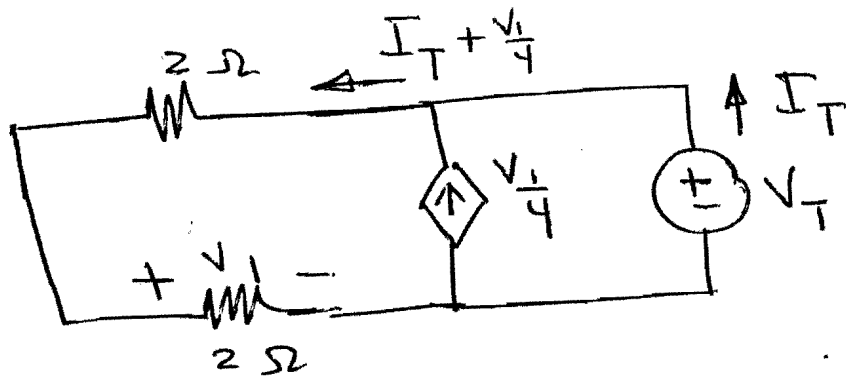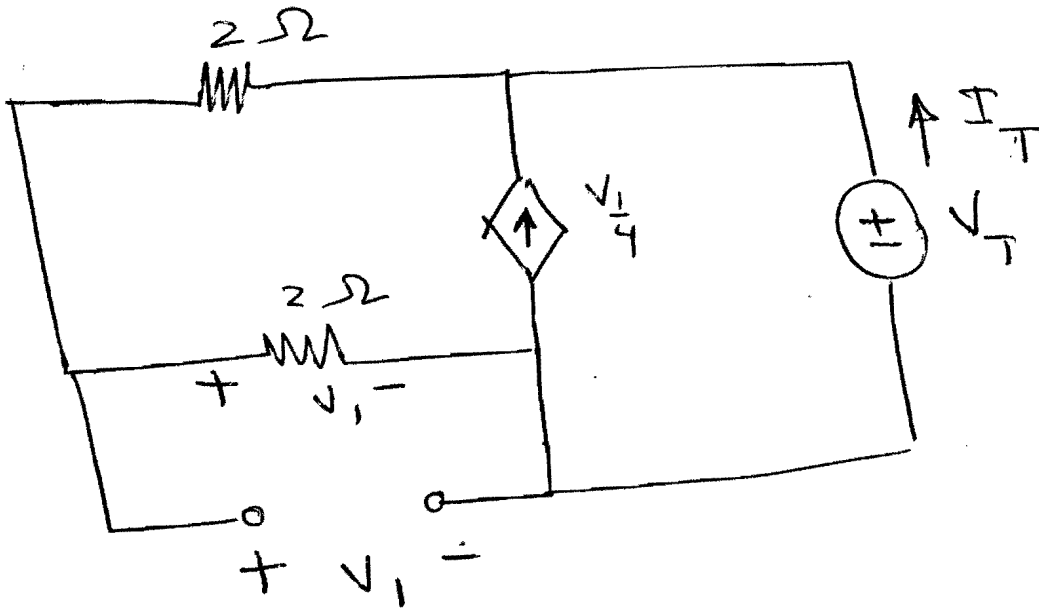

$$v_1 = 2 \left(I_T + \frac{v_1}{4} \right) \Rightarrow v_1 = 4 I_T$$

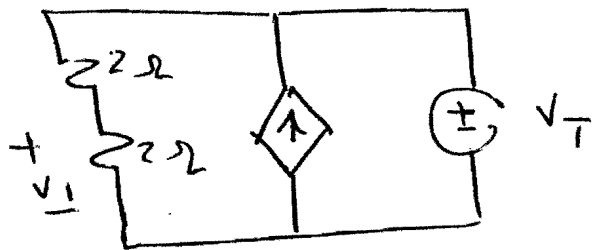however since $v_1 = \frac{v_T}{2}$ (voltage division)



$$\Rightarrow \frac{v_T}{2} = 4 I_T \Rightarrow \frac{v_T}{I_T} = (4)(2) = 8\ \Omega$$