
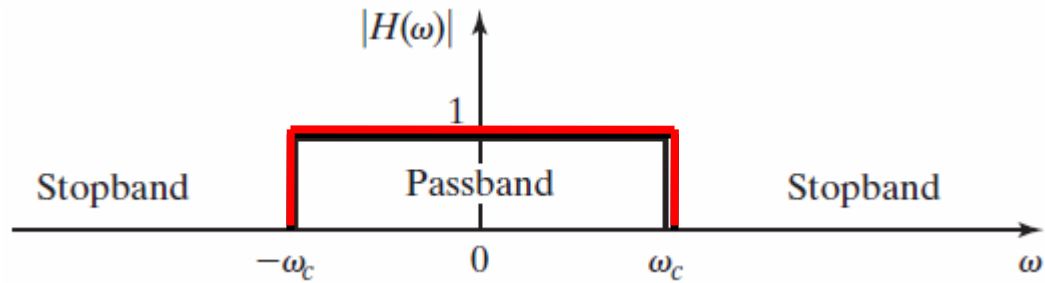



## 6.1 IDEAL FILTERS

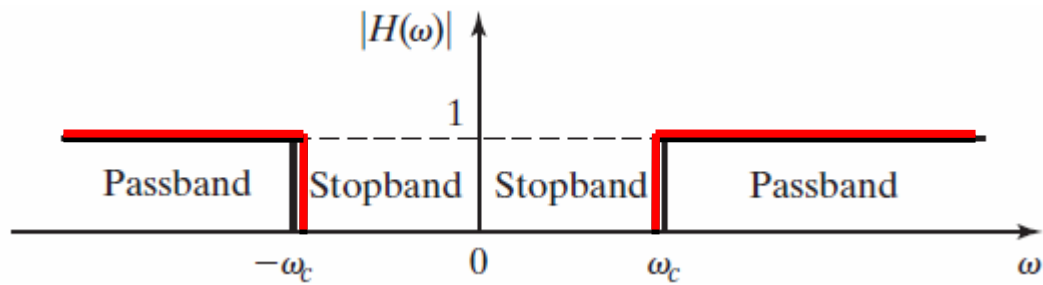

**ideal low-pass filter**




**high-pass filter**

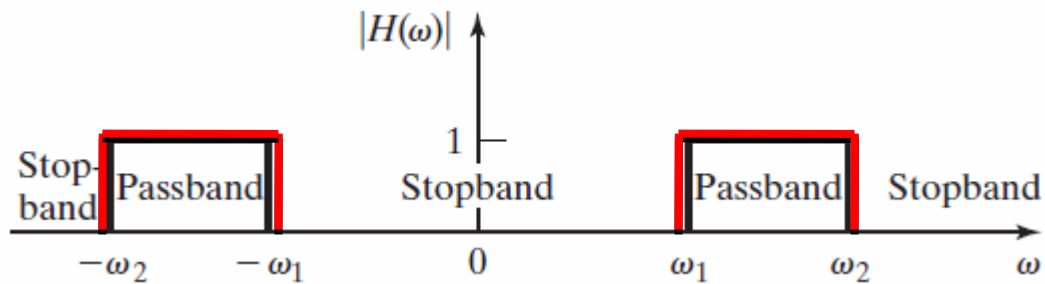

**bandpass filter**

## RC Low-Pass Filter

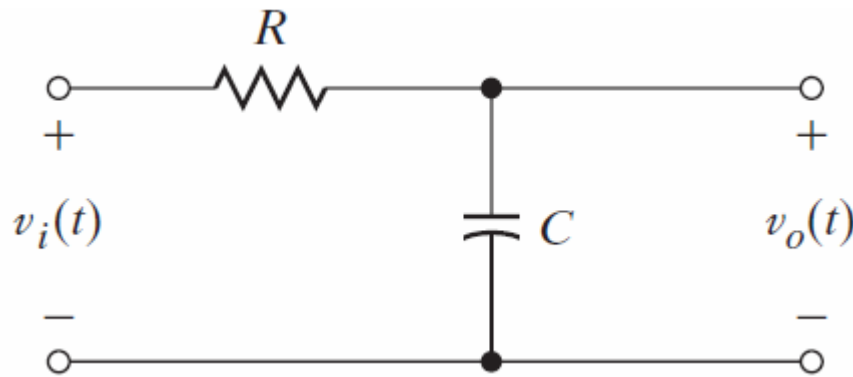

$$v_o(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

$$v_i(t) = Ri(t) + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

$$V_i(\omega) = RI(\omega) + \frac{1}{j\omega C} I(\omega)$$

$$V_o(\omega) = \frac{1}{j\omega C} I(\omega)$$

$$H(\omega) = \frac{V_o(\omega)}{V_i(\omega)} = \frac{1}{1 + j\omega RC}$$

$$\omega_c = \frac{1}{RC} \quad H(\omega) = \frac{1}{1 + j\omega/\omega_c} = |H(\omega)|e^{j\Phi(\omega)}$$

The magnitude and phase frequency spectra of the filter are described by the equations

$$H(\omega) = \frac{1}{1 + j\omega/\omega_c}$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_c)^2}}$$


$$\Phi(\omega) = -\arctan(\omega/\omega_c)$$

At the frequency  $\omega = \omega_c \Rightarrow \frac{\omega}{\omega_c} = 1$

$$|H(\omega_c)| = \frac{|V_o(\omega_c)|}{|V_i(\omega_c)|} = \frac{1}{\sqrt{2}}$$

The ratio of the normalized power of the **input** and **output** signals is given by

$$|H(\omega_c)|^2 = \frac{|V_o(\omega_c)|^2}{|V_i(\omega_c)|^2} = \frac{1}{2}$$

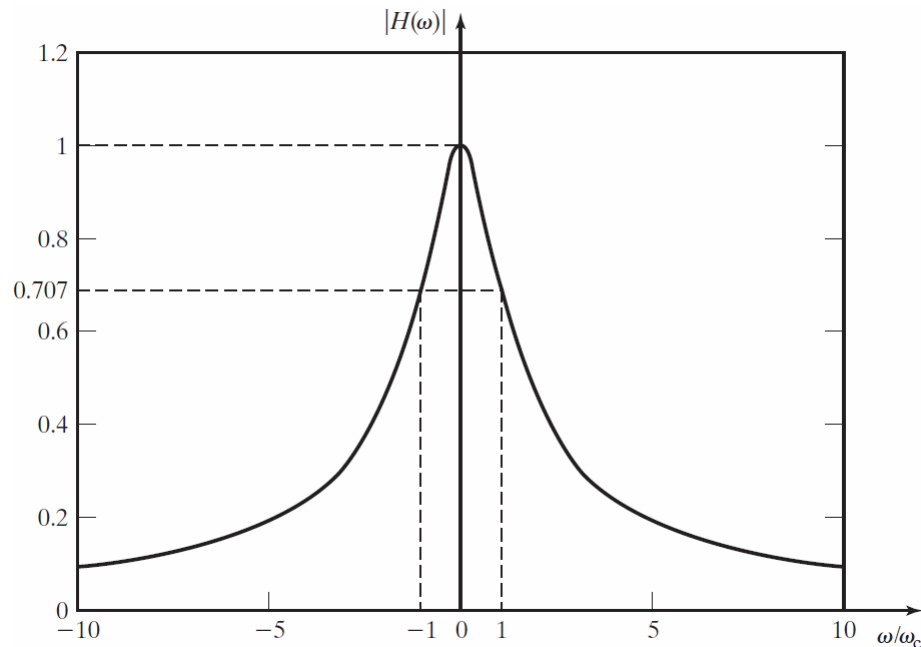

This type of filter is often called the **half-power frequency**