

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

EE 202


Homework #7, Ch.9

DUE DATE: Wednesday 26th, 2012

| | |
|-----------------|--|
| ID# | |
| Name | |
| Section# | |

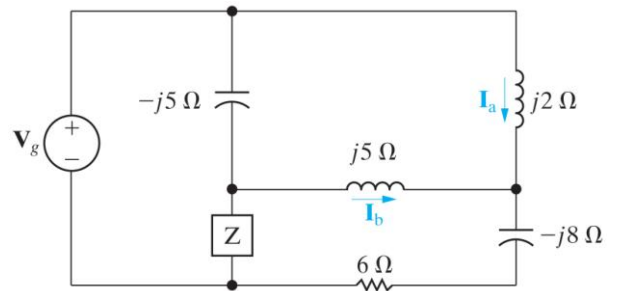Problem #1

Find \mathbf{I}_b and \mathbf{Z} in the circuit shown, $\mathbf{V}_g = 60\angle 0^\circ \text{ V}$ and $\mathbf{I}_a = 5\angle -90^\circ \text{ A}$




Problem #2

The circuit shown is operating in the sinusoidal steady state. Find the value of ω if

$$i_o = 100 \sin(\omega t + 81.87^\circ) \text{ mA}$$


$$v_g = 50 \cos(\omega t - 45^\circ) \text{ V}$$

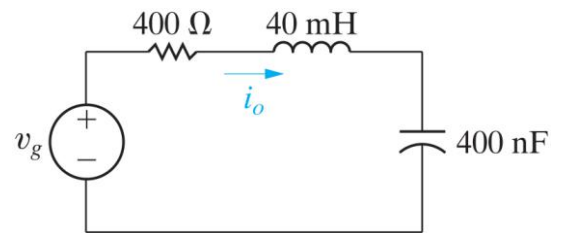What is the phase difference between the voltage and current, take the voltage as reference.



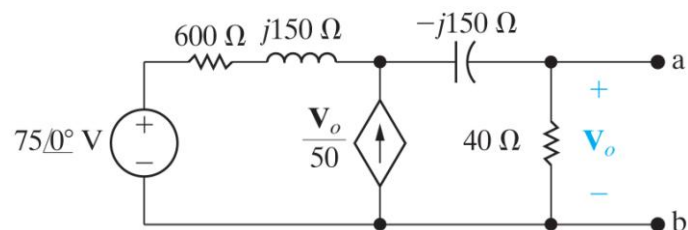
Problem #3

Find the Norton equivalent circuit with respect to the terminals a, b of the circuit shown below:



Problem #4

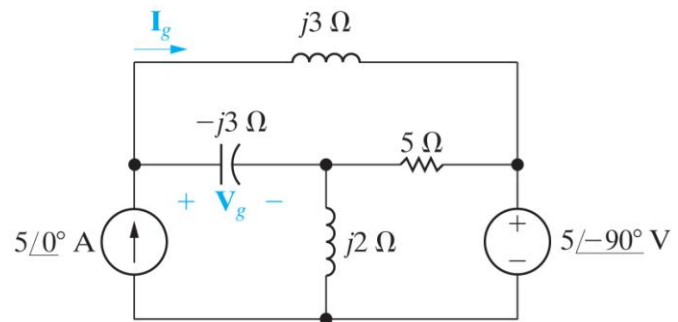- A) Use the node-voltage method to find the phasor voltage \mathbf{V}_g in the circuit shown below:



- B) Use Mesh Analysis method to find the phasor \mathbf{I}_g .