


EE 202-Fall 2012(121)

HW5 Solution




Dr. Alakhdhar

Due 1/12/2012


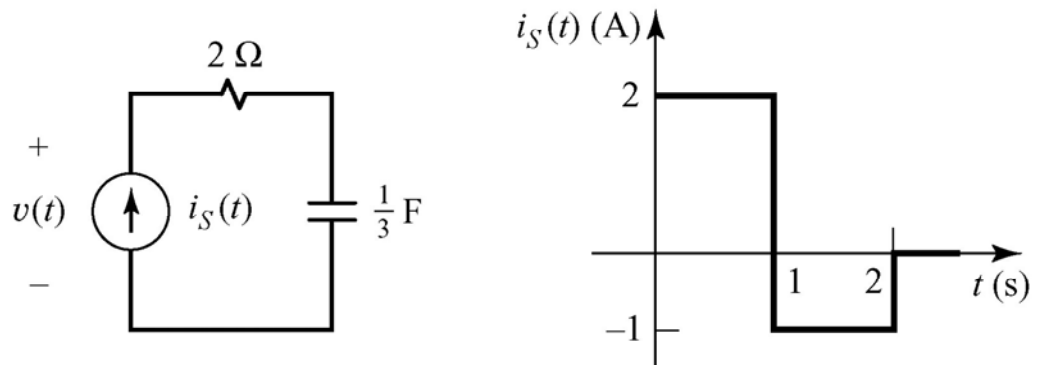
**Q1** Sketch the voltage  $v(t)$  in the circuit shown. Assume  $i_s(t) = 0$  for  $t \leq 0$



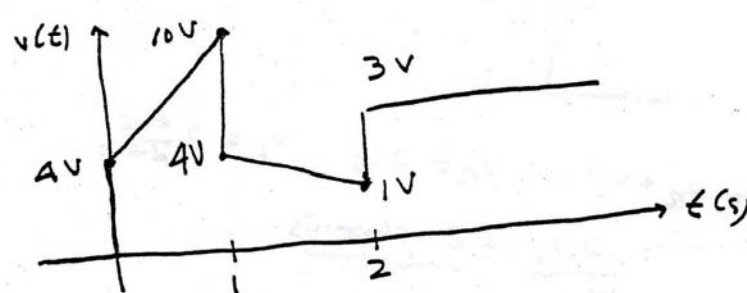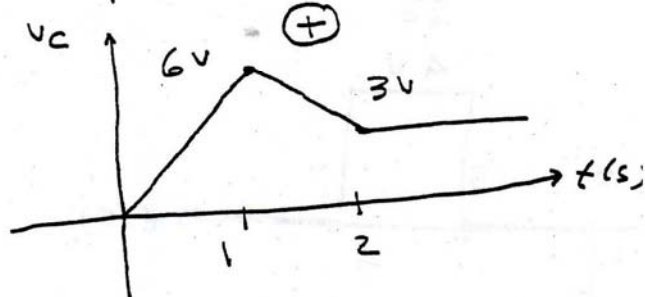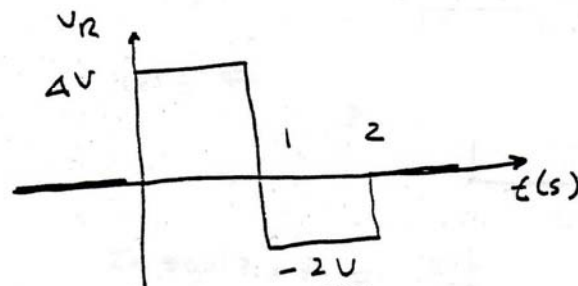
$$v(t) = v_R + v_C, \quad v_C + v_R = \underbrace{2i_s}_{v_R} + \underbrace{3 \int_{-\infty}^t i_s(\tau) d\tau}_{v_C}$$



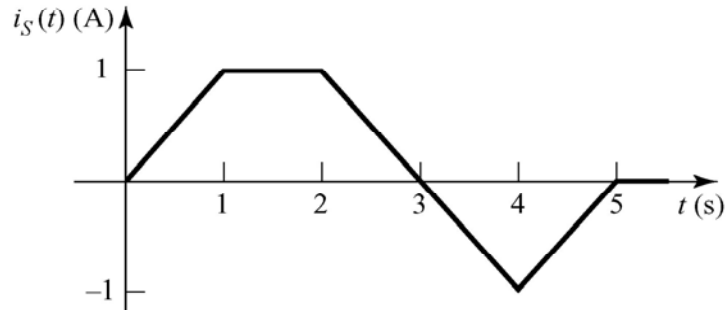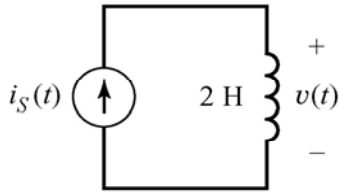
**Q2** Sketch the voltage  $v(t)$  in the circuit shown


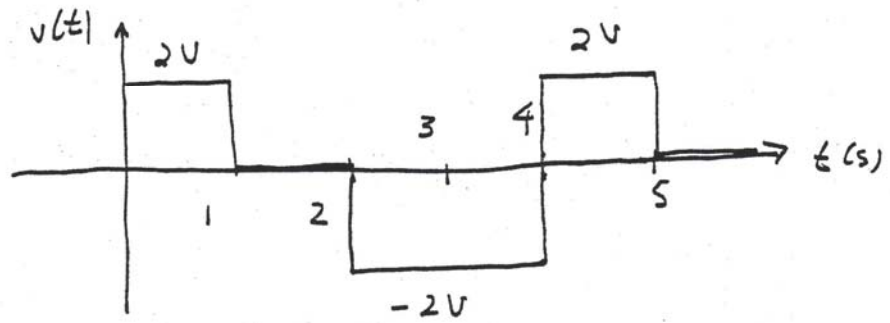
$$v(t) = L \frac{di(t)}{dt} = 2 \frac{di_s}{dt}$$





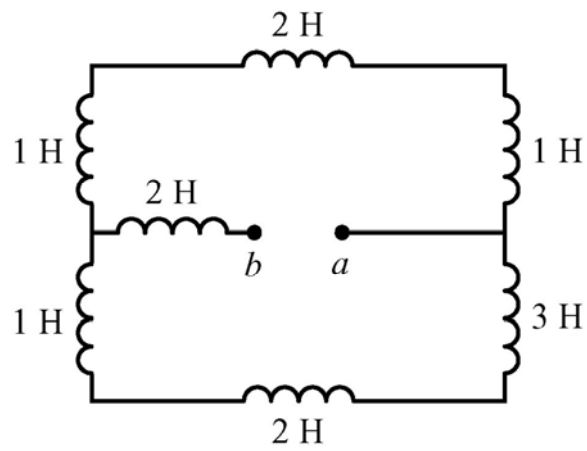**Q3** Determine the equivalent inductance between the terminal



$$\begin{aligned}
 L_{eq} &= 2\text{ H} + \left[ (1\text{ H} + 2\text{ H} + 1\text{ H}) \parallel (1\text{ H} + 2\text{ H} + 3\text{ H}) \right] \\
 &= 2 + [4 \parallel 6] = 2 + \frac{12}{5} = \frac{22}{5}\text{ H}
 \end{aligned}$$

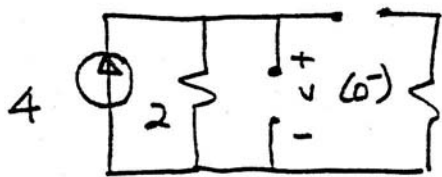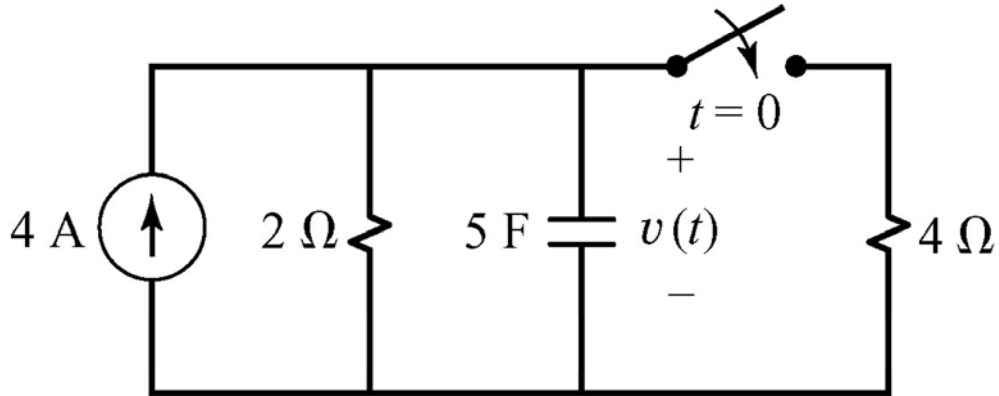
**Q4** Determine and sketch the voltage  $v(t)$  for all  $t$ .





$$v(0^-) = 8 \text{ V} = v(0^+)$$

$$v_{\text{final}} = \frac{16}{3} \quad \tau = RC = \frac{4}{3} \times 5 = \frac{20}{3}$$


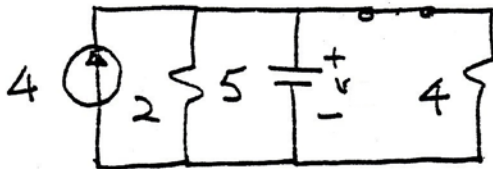
$$\therefore v(t) = \frac{16}{3} + \left[ 8 - \frac{16}{3} \right] e^{-3t/20}$$


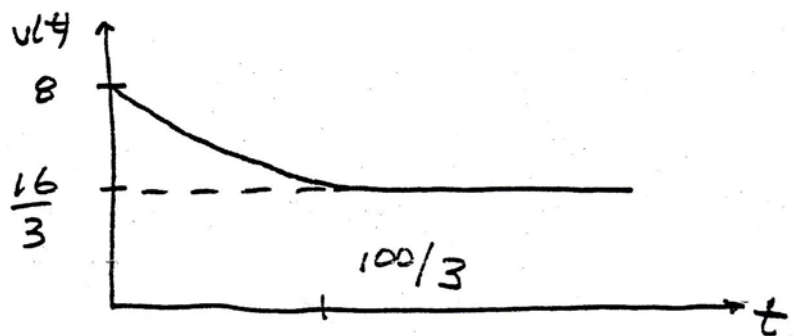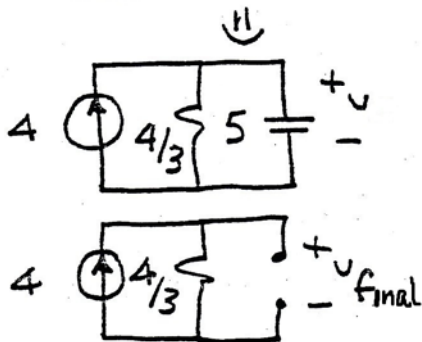
$$\therefore v(t) = \left( \frac{16}{3} + \frac{8}{3} e^{-3t/20} \right) \text{ V} \quad t > 0$$




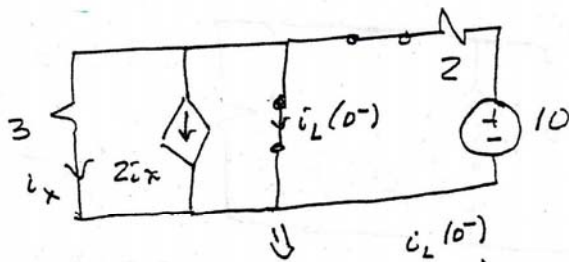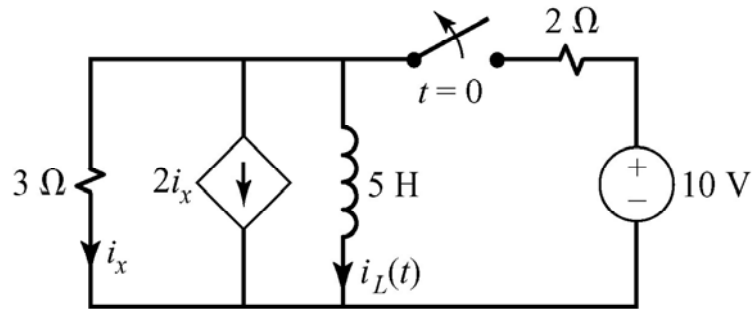**Q5** Determine and sketch the current  $i_L(t)$  for all  $t$ .




$$i_x = 0$$
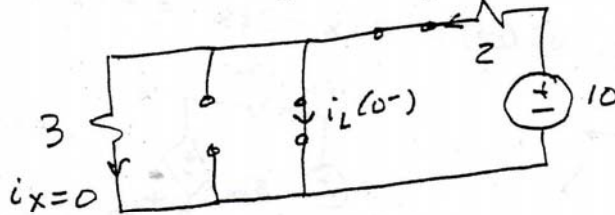
$$i_L(0^-) = i_L(0^+) = \frac{10}{2} = 5 \text{ A}$$



$t > 0$

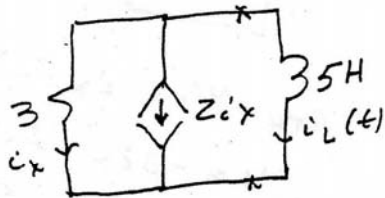


$$3\left(\frac{v_L}{3}\right) + v_L = 0$$

$$5 \frac{di_L}{dt} + v_L = 0$$

$$\frac{di_L}{dt} + \frac{1}{5}i_L = 0$$



$$\tau = 5 \text{ s}$$
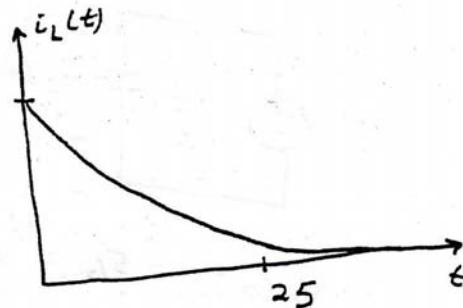
$$\therefore i_L(t) = i_L(0^+) e^{-t/5} = 5 e^{-t/5} \text{ A}$$




**Q6** The switch in the circuit shown has been in position a for a long time. At  $t = 0$ , it moves instantaneously to position b, where it remains for 350 ms before moving instantaneously to position c. Find  $v_o(t)$  for  $t \geq 0$ .

$t < 0$ :

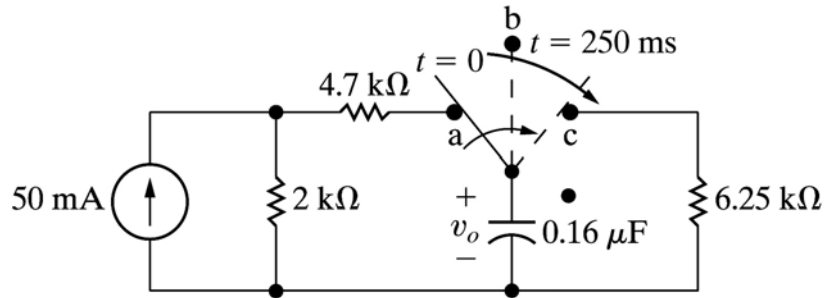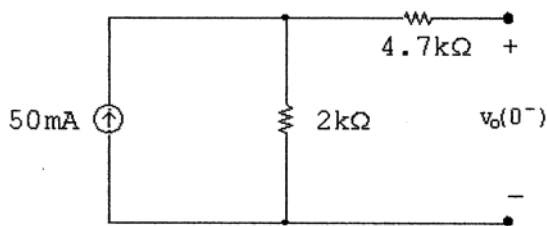


$$v_c(0^-) = (50)(2000) \times 10^{-3} = 100 \text{ V} = v_c(0^+)$$

$0 \leq t \leq 250 \text{ ms}$ :

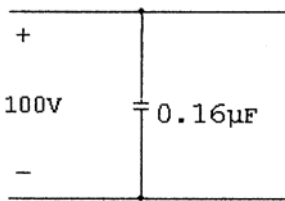

$$\tau = \infty; \quad 1/\tau = 0; \quad v_o = 100e^{-0} = 100 \text{ V}$$

$250 \text{ ms} \leq t < \infty$ :

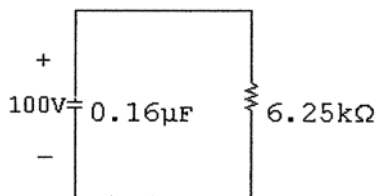

$$\tau = (6.25)(0.16)10^{-3} = 1 \text{ ms}; \quad 1/\tau = 1000; \quad v_o = 100e^{-1000(t-0.25)} \text{ V}$$

Summary:

$$v_o = 100 \text{ V}, \quad 0 \leq t \leq 250 \text{ ms}$$

$$v_o = 100e^{-1000(t-0.25)} \text{ V}, \quad 250 \text{ ms} \leq t < \infty$$