
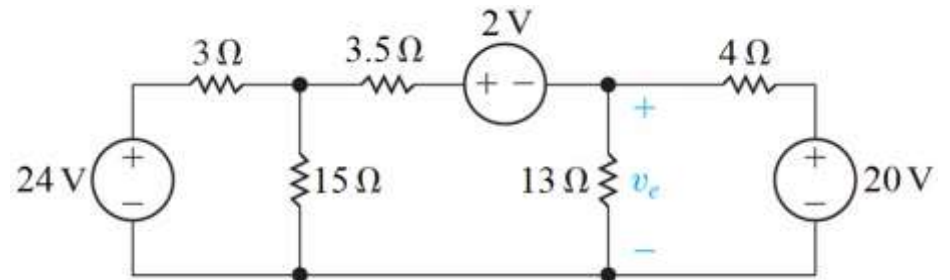


Question 1:


For the circuit below, use a series of source transformations all the way (only **source transformations**) to find the **voltage** v_e .

**Solution:**

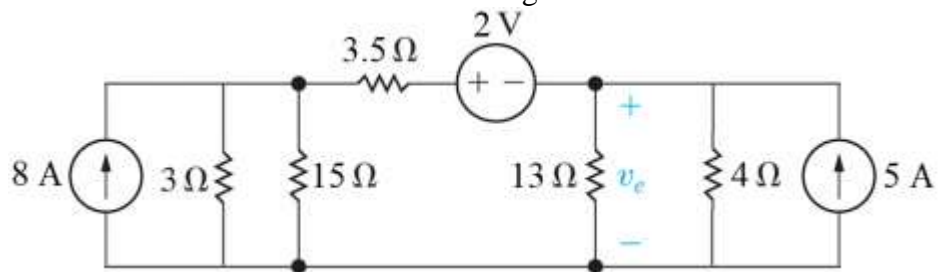
1) [] Two source transformations from the left and write to get:



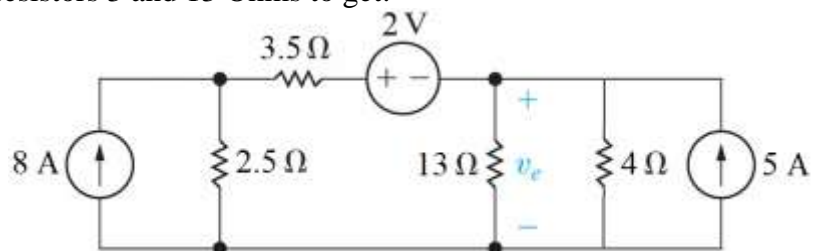
2) []:Combine the two resistors 3 and 13 Ohms to get:



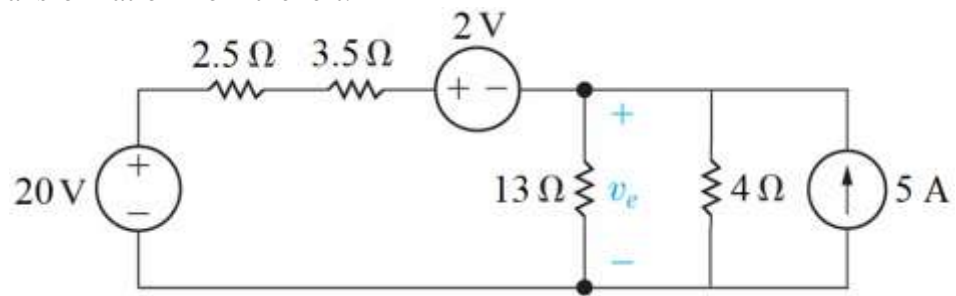
3) [] One source transformation from the left:



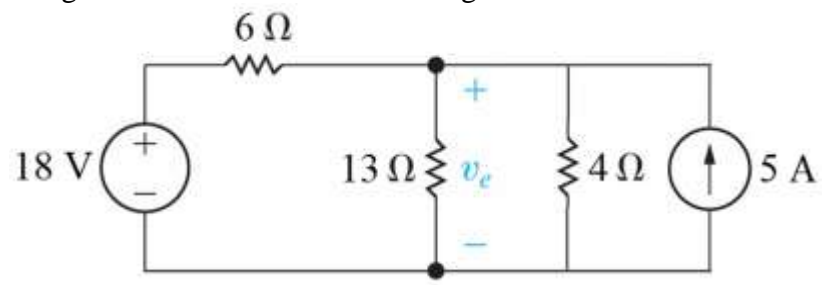4) []:Combine the two voltage sources and two resistors to get:



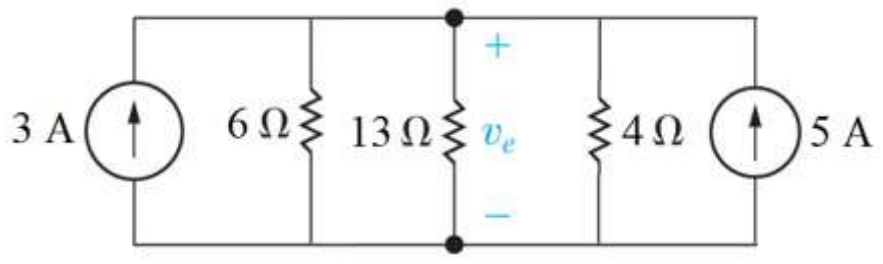5) []:One source transformation from the left to get:



6) []:Apply KCL and the upper node and Ohms Law on the three resistors to get:

$$v_e \left(\frac{1}{6} + \frac{1}{13} + \frac{1}{4} \right) - 3 - 5 = 0$$

$$v_e = 16.21 \text{ V}$$


Question 2:

For the circuit shown, the voltage

$$v_s(t) = \begin{cases} -2t + 2 \text{ V} & , 0 \leq t \leq 1 \\ 2t - 2 \text{ V} & , 1 \leq t \leq 2 \end{cases}$$

and $i_L(0) = -1 \text{ A}$

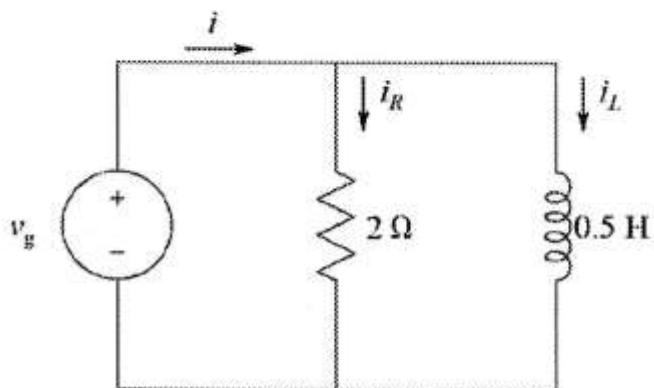- Find the current $i(t)$ for $0 < t < 1 \text{ s}$
- Find $i(1)$
- Find the energy stored in the inductor at $t=1 \text{ s}$
- Find the current $i(t)$ for $1 < t < 2 \text{ s}$



Solution

a)

$$i = i_R + i_L$$

$$i_R = \frac{v_s}{2} = -t + 1 \quad 0 < t < 1$$

$$i_L = \frac{1}{0.5} \int_0^t v_s dt + i_L(0) \quad 0 < t < 1$$

$$= \frac{1}{0.5} \int_0^t (-2t + 2) dt - 1 \quad 0 < t < 1$$

$$= 2[-t^2 + 2t] - 1 \quad 0 < t < 1$$

$$i = -2t^2 + 3t \text{ A} \quad 0 < t < 1$$

b)

$$i(1) = 1 \text{ A}$$

c)

$$W(1) = \frac{1}{2} L i^2(1) = \frac{1}{2} (0.5) (1)^2 = \frac{1}{4} \text{ J}$$

d)

$$i_R = \frac{v_s}{2} = t - 1 \quad 1 < t < 2$$

$$i_L = \frac{1}{0.5} \int_1^t v_s dt + i_L(1) \quad 1 < t < 2$$

$$= \frac{1}{0.5} \int_1^t (2t - 2) dt + 1 \quad 1 < t < 2$$

$$= 2[t^2 - 2t - 1 + 2] + 1 \quad 1 < t < 2$$

$$i = 2t^2 - 3t + 2 \text{ A} \quad 1 < t < 2$$

Question 3:

For the circuit below, the switch has been Closed for long time before opening at $t = 0$. All currents $i(t)$ are in mA, and voltages $v(t)$ in V. Circle the correct answer for the parts a to i.

a) Find $i_o(0^-)$:

- i) -3 ii) -2 iii) -1 iv) 0 **v) 1** vi) 2 vii) 3

b) Find $v_C(0^-)$:

- i) -20 ii) -10 iii) -5 iv) 0 v) 5 **vi) 10** vii) 20

c) Find $i_o(0^+)$:

- i) -3 ii) -2 iii) -1 iv) 0 **v) 1** vi) 2 vii) 3

d) Find $v_C(0^+)$:

- i) -20 ii) -10 iii) -5 iv) 0 v) 5 **vi) 10** vii) 20

e) Find $i_o(\infty)$:

- i) -3 ii) -2 iii) -1 **iv) 0** v) 1 vi) 2 vii) 3

f) Find $v_C(\infty)$:

- i) -20 ii) -10 iii) -5 **iv) 0** v) 5 vi) 10 vii) 20

g) Find $i_C(0^-)$:

- i) -3 ii) -2 iii) -1 **iv) 0** v) 1 vi) 2 vii) 3

h) Find $i_C(0^+)$:

- i) -3 ii) -2 **iii) -1** iv) 0 v) 1 vi) 2 vii) 3

i) Find $i_C(\infty)$:


- i) -3 ii) -2 iii) -1 **iv) 0** v) 1 vi) 2 vii) 3

j) Write the expression of $v_C(t)$ for $t \geq 0$. $v_C(t) = 10 e^{-\frac{t}{2}} \text{ V}, t \geq 0$

k) Write the expression of $i_o(t)$ for $t > 0$. $i_o(t) = e^{-\frac{t}{2}} \text{ mA}, t > 0$

l) Write the expression of $i_C(t)$ for $t > 0$. $i_C(t) = -e^{-\frac{t}{2}} \text{ mA}, t > 0$


$$Z = RC = (10 \text{ k}\Omega)(200 \mu\text{F}) \\ Z = 2 \text{ s}$$

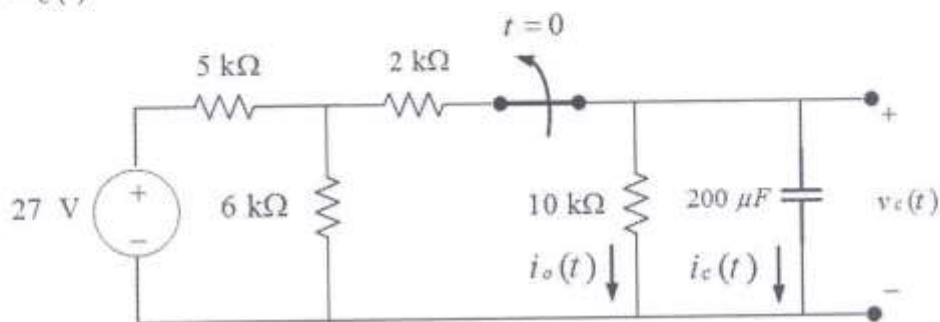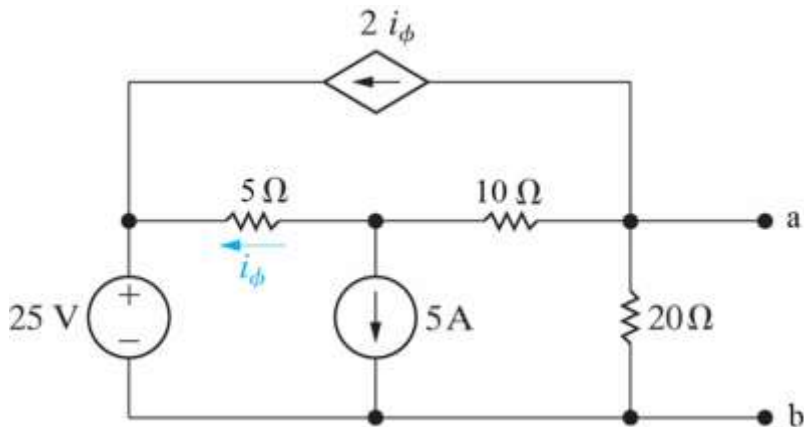


Question 4:

For the circuit below, find the following:

- The open circuit voltage between ab.
- The Thevenin resistor R_{th} .

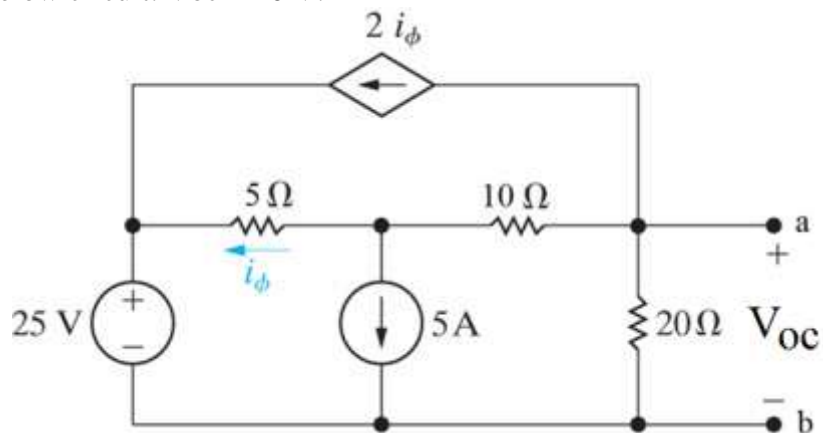**Solution:**

- To find the open circuit voltage:
 - to start with the below circuit. $V_{oc} = 40\text{ V}$.



- b) To find the Thevenin resistor:
- $R_{th} = 4 \Omega$.

