
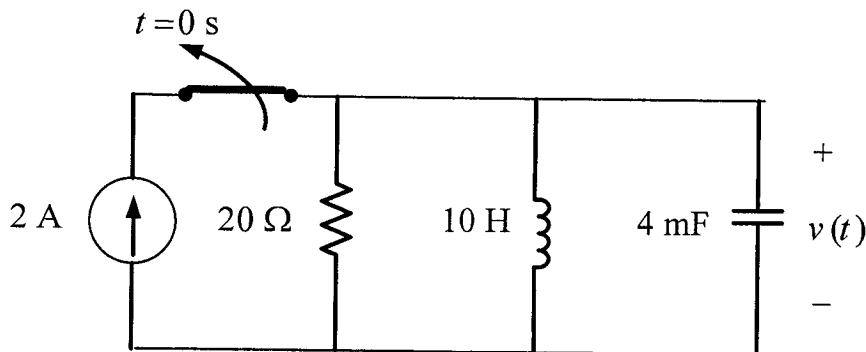


SER	ID	NAME	KEY
-----	----	------	-----

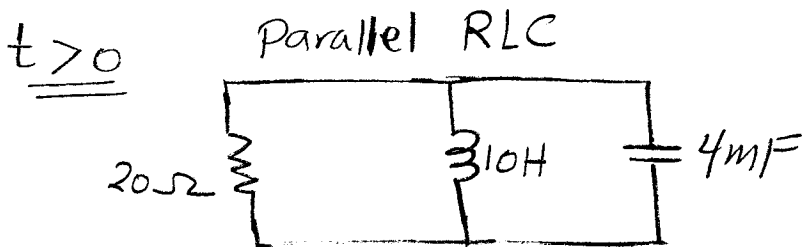

For the circuit shown above, the switch was closed for a long time. At $t=0$ s the switch is opened. Find $v(t)$ for all time?

$t < 0$ Capacitor open $\Rightarrow v(0^-) = 0$
 inductor short $\Rightarrow i_L(0^-) = 2$



$$\alpha = \frac{1}{2RC} = \frac{25}{4} = 6.25 \text{ rad/s}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 5 \text{ rad/s}$$

$\alpha > \omega_0 \Rightarrow$ overdamped $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\frac{25}{4} \pm \frac{15}{4}$$

$$s_1 = -\frac{25}{4} + \frac{15}{4} = -2.5$$

$$s_2 = -\frac{25}{4} - \frac{15}{4} = -10$$


$$\Rightarrow v(t) = A_1 e^{-2.5t} + A_2 e^{-10t}$$

(continue) \Rightarrow

$$v(0^+) = v(0^-) = 0 \Rightarrow A_1 + A_2 = 0 \quad - (1)$$

$$i_c(t) = C \frac{dv(t)}{dt} \Rightarrow \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C}$$

$$t = 0^+$$

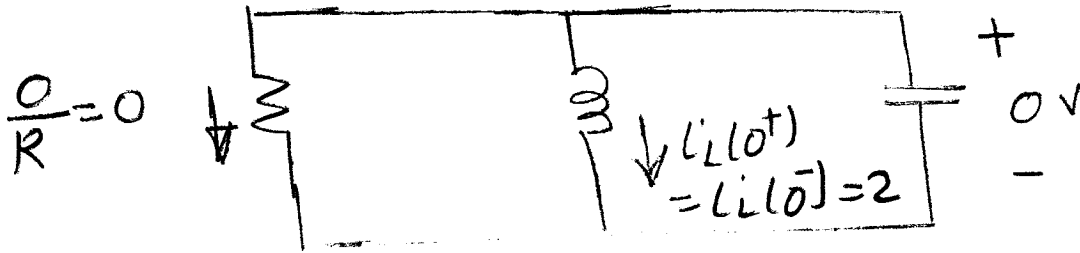

KCL

$$i_R(0^+) + i_L(0^+) + i_c(0^+) = 0$$

$$0 + 2 + i_c(0^+) = 0$$

$$\Rightarrow i_c(0^+) = -2 \text{ A}$$

$$\Rightarrow \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = \frac{-2}{4 \times 10^{-3}} = -500$$


$$\frac{dv(t)}{dt} = -2.5 A_1 e^{-2.5t} - 10 A_2 e^{-10t}$$

$$\frac{dv(0^+)}{dt} = -500 = -2.5 A_1 - 10 A_2 \quad - (2)$$



solving (1) and (2) $\Rightarrow A_1 = -66.67 \quad A_2 = 66.67$

$$\Rightarrow v(t) = 66.67 (e^{-10t} - e^{-2.5t}) \text{ V}$$

SER	ID	NAME	KEY
-----	----	------	-----

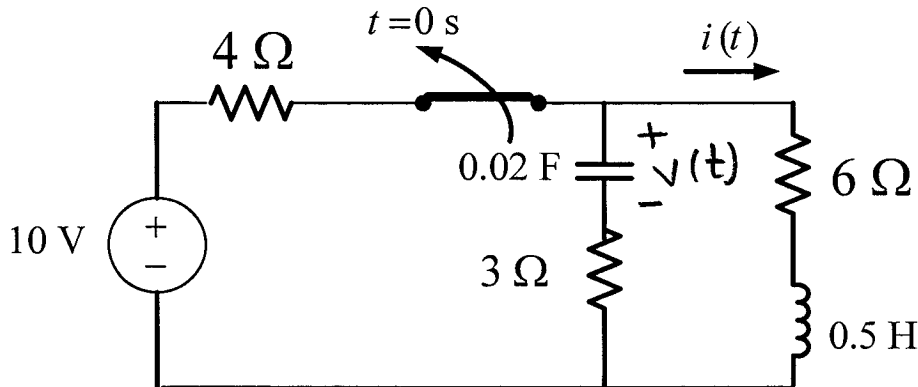

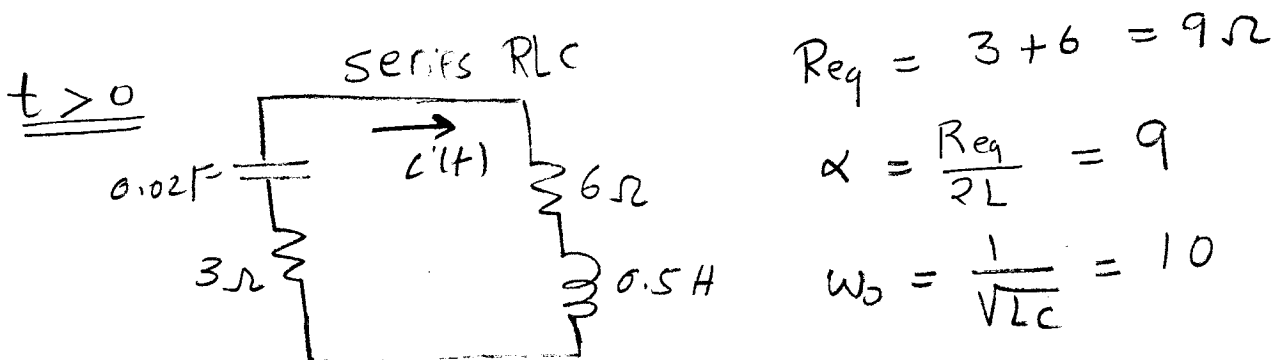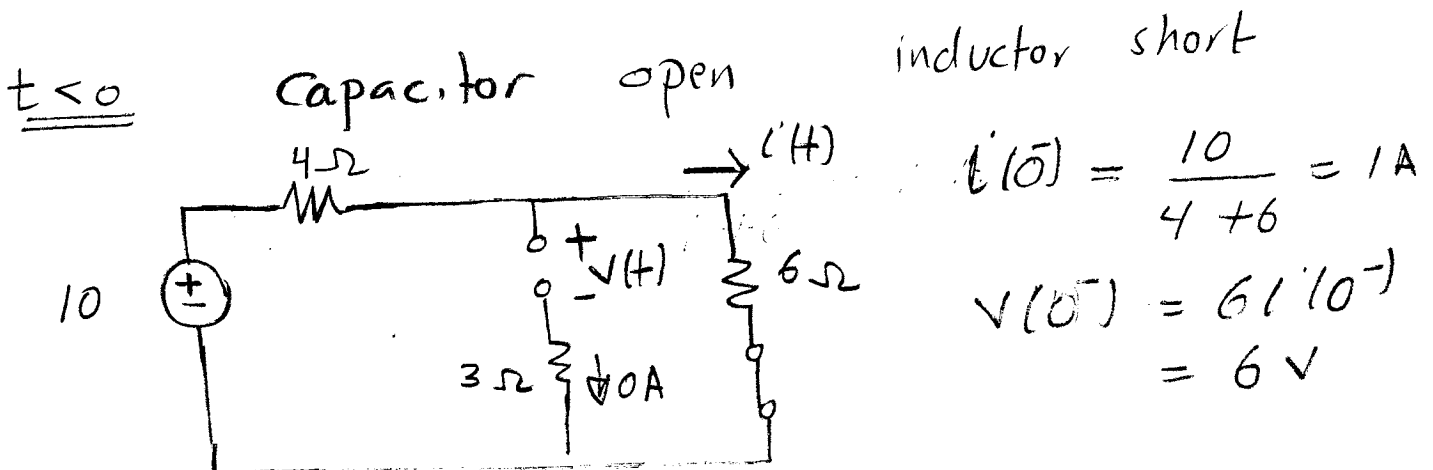For the circuit shown above, the switch was closed for a long time. At $t=0$ s the switch is opened. Find $i(t)$ for all time?



$\alpha < \omega_0 \Rightarrow$ underdamped


$$i'(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 4.359$$

$$\Rightarrow i(t) = e^{-9t} (B_1 \cos 4.359t + B_2 \sin 4.359t)$$

$$i(0^+) = i(0^-) = 1 = B_1 \quad \text{--- ①}$$
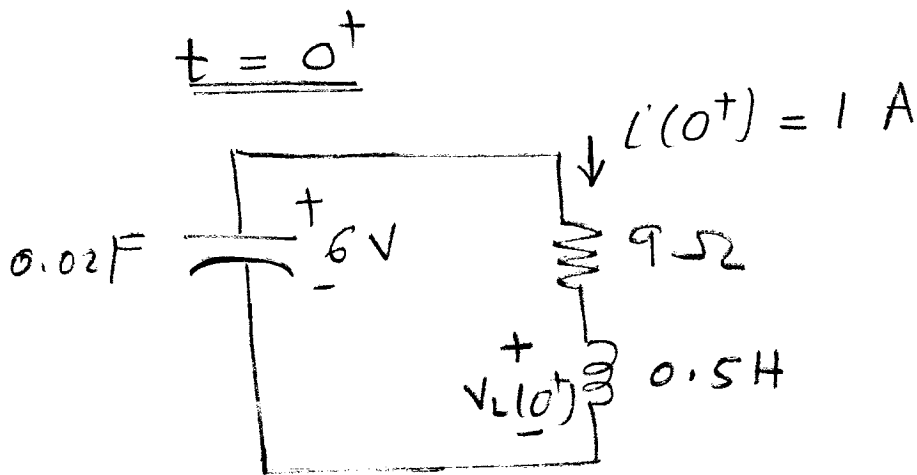
$$v_L(t) = L \frac{di(t)}{dt} \Rightarrow \frac{di(0^+)}{dt} = \frac{v_L(0^+)}{L}$$



$$\text{KVL} \quad -6 + 9i(0^+) + v_L(0^+) = 0$$

$$\Rightarrow v_L(0^+) = 6 - 9(1) = -3$$


$$\Rightarrow \frac{di(0^+)}{dt} = \frac{-3}{0.5} = -6 \text{ A/s}$$

$$\frac{di(t)}{dt} = -9e^{-9t} (B_1 \cos 4.359t + B_2 \sin 4.359t) + e^{-9t} (4.359) (-B_1 \sin 4.359t + B_2 \cos 4.359t)$$


$$\frac{di(0^+)}{dt} = -6 = -9(B_1 + 0) + 4.359(-0 + B_2)$$

$$\Rightarrow B_2 = 0.6882 \Rightarrow i(t) = e^{-9t} (\cos 4.359t + 0.6882 \sin 4.359t)$$

SER	ID	NAME	KEY
-----	----	------	-----

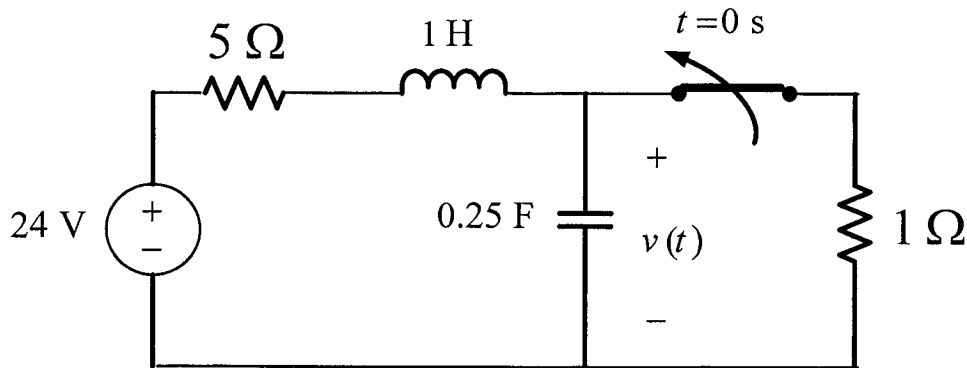

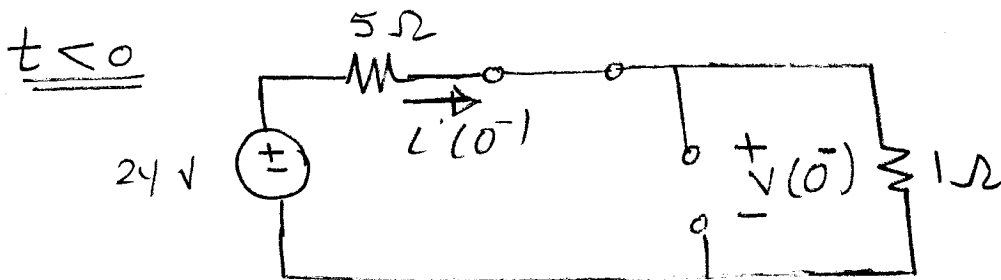For the circuit shown above, the switch was closed for a long time. At $t=0$ s the switch is opened. Find $v(t)$ for all time?




$$v(0^-) = \frac{1}{5+1} 24$$

$$= 4 \text{ V}$$

$$i'(0^-) = \frac{24}{6}$$

$$= 4 \text{ A}$$

$t > 0$ step response series RLC

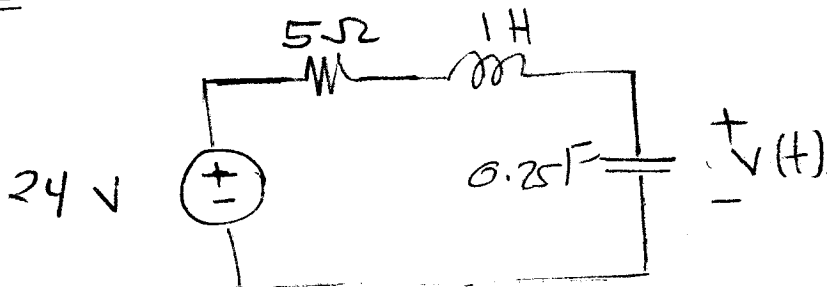

$$\alpha = \frac{R}{2L} = 2.5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2$$

$\alpha > \omega_0 \Rightarrow$ overdamped $v(t) = V_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$$V_f = v(\infty) = 24 \text{ V}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -2.5 \pm 1.5$$

$$s_1 = -1, s_2 = -4$$


$$v(t) = 24 + A_1 e^{-t} + A_2 e^{-4t}$$

\Rightarrow

$$v(0^+) = v(0^-) = 4 = 24 + A_1 + A_2$$

$$\Rightarrow A_1 + A_2 = -20 \quad \text{--- (1)}$$
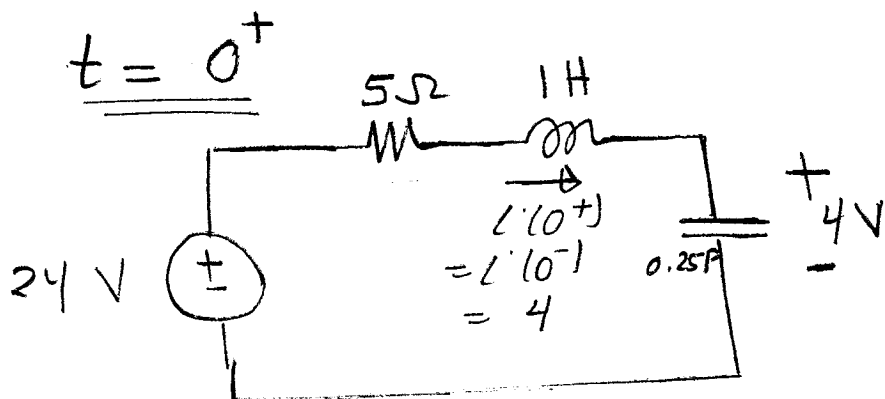
$$i_c(t) = C \frac{dv(t)}{dt} \Rightarrow \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C}$$



$$i_c(0^+) = 4\text{ A}$$

$$\Rightarrow \frac{dv(0^+)}{dt} = \frac{4}{0.25} = 16\text{ V/s}$$

$$\frac{dv(t)}{dt} = -A_1 e^{-t} - 4A_2 e^{-4t}$$

$$\Rightarrow \frac{dv(0^+)}{dt} = 16 = -A_1 - 4A_2 \quad \text{--- (2)}$$

solving (1) and (2)

$$\Rightarrow A_1 = -\frac{64}{3} \quad A_2 = \frac{4}{3}$$

$$\Rightarrow v(t) = 24 + \frac{4}{3} (-16 e^{-t} + e^{-4t}) \text{ V} \quad \underline{t \geq 0}$$