
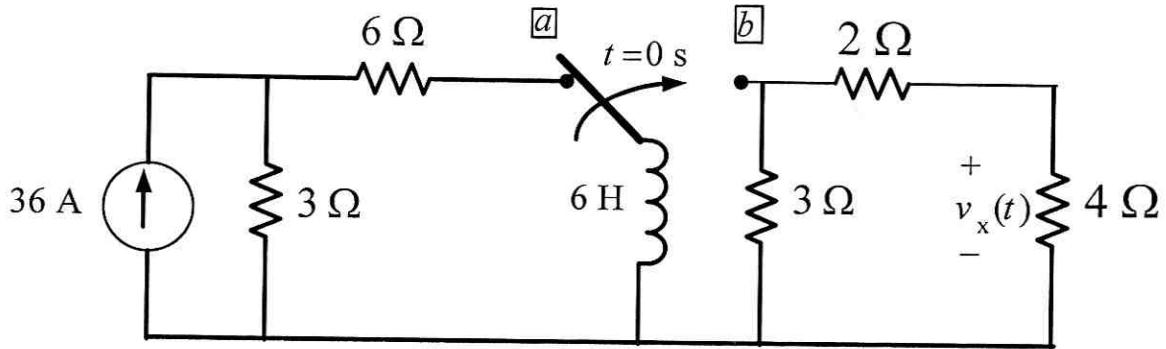



SER	ID	NAME <b>KEY</b>
-----	----	-----------------

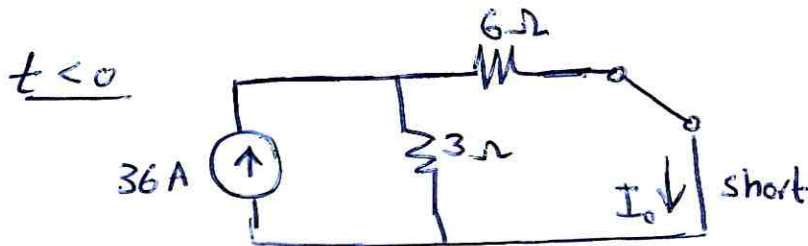

For the circuit shown above, the switch was in position **a** for a long time. At  $t=0$  s the switch is moved to position **b**. Find  $v_x(t)$  for all time?


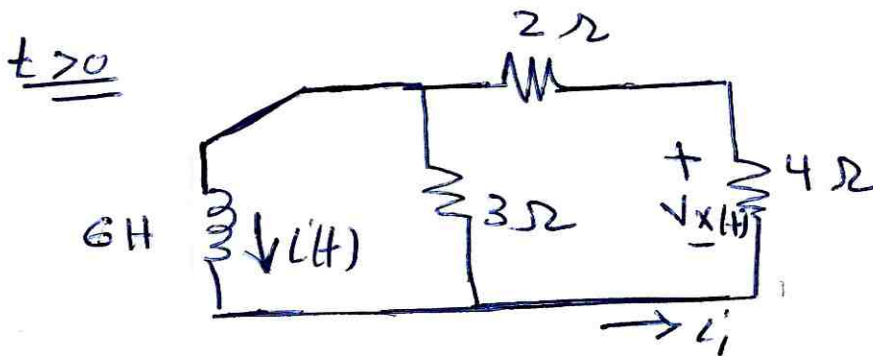
$$I_0 = \frac{3}{3+6} 36 = 12 \text{ A}$$




$$(2+4) \parallel 3 = 2 \Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{6}{2} = 3 \text{ s} \Rightarrow i(t) = 12 e^{-\frac{t}{3}} \text{ A}$$


$$\Rightarrow i_1(t) = \frac{3}{(2+4)+3} i(t) = \frac{3}{9} 12 e^{-\frac{t}{3}} = 4 e^{-\frac{t}{3}} \text{ A}$$

$$v_x(t) = -4 i_1(t) = -16 e^{-\frac{t}{3}} \text{ V}$$


SER	ID	NAME <b>KEY</b>
-----	----	-----------------

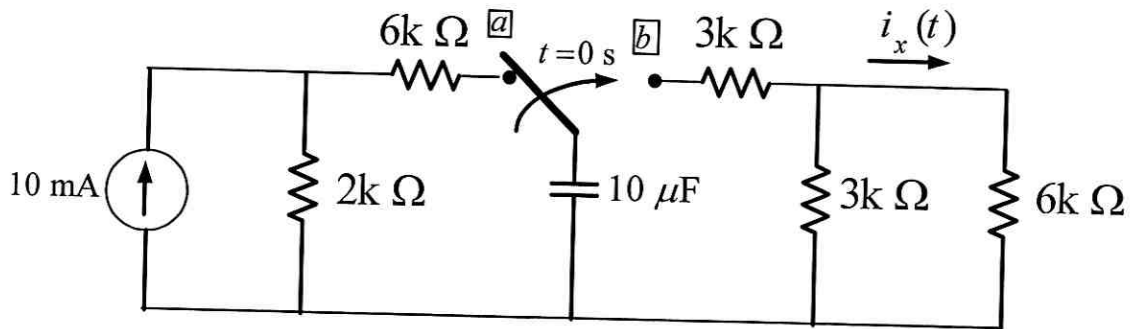

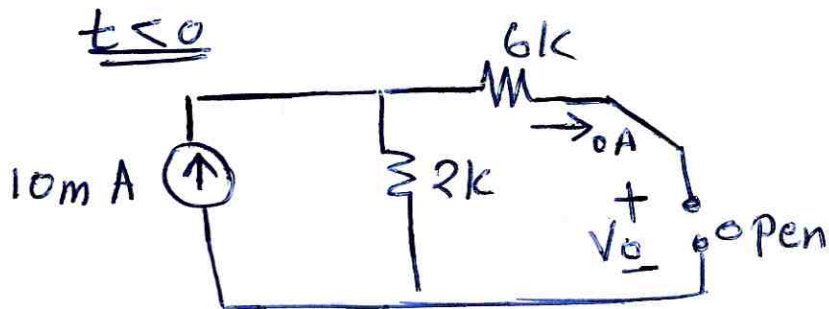For the circuit shown above, the switch was in position **a** for a long time. At  $t=0$  s the switch is moved to position **b**. Find  $i_x(t)$  for all time?



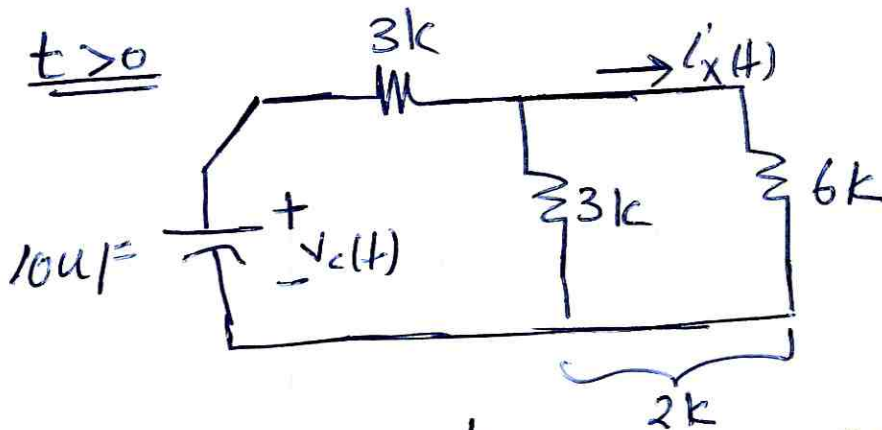
$$V_0 = V_{2k\Omega} = (2k)(10mA) = 20V$$



$$R = RC = (5k)(10\mu F) = 50ms$$
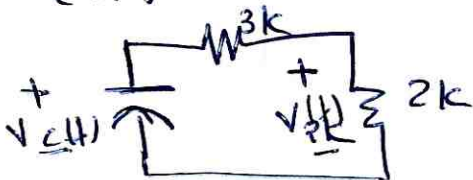
$$V_c(t) = 20 e^{-\frac{t}{50ms}} = 20 e^{-20t} \quad t > 0$$



$$V_{2k}(t) = \frac{2k}{3k+2k} V_c(t) = \frac{2}{5} 20 e^{-20t} = 8 e^{-20t} V$$

$$i'_x(t) = \frac{V_{2k}(t)}{6k} = \frac{8}{6} e^{-20t} = 1.33 e^{-20t} mA$$