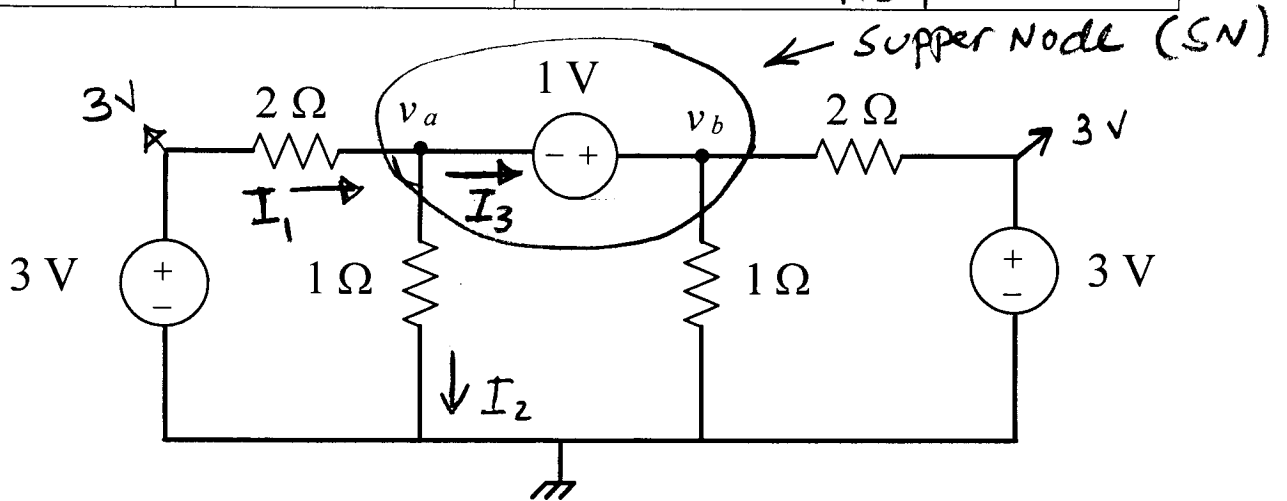


SER	ID	NAME	KEY
-----	----	------	-----



For the circuit shown above :

- (a) Using the node voltage method find the node voltages v_a, v_b ?
- (b) The power deliver by the 1 V independent source ?

(a) Kcl at SN
$$\frac{v_a - 3}{2} + \frac{v_a}{1} + \frac{v_b}{1} + \frac{v_b - 3}{2} = 0$$

$$\Rightarrow 3v_a + 3v_b = 6 \quad \text{--- (1)}$$

Voltage Restriction
$$v_b - v_a = 1$$

or
$$v_a - v_b = -1 \quad \text{--- (2)}$$

solving (1), (2)
$$\Rightarrow v_a = 0.5V \quad v_b = 1.5V$$


(b)
$$P_{1V}^{absorb} = -(1)I_3 \Rightarrow \text{seeking } I_3 ?$$

Kcl at node va
$$I_1 = I_2 + I_3 \Rightarrow I_3 = I_1 - I_2$$

$$I_3 = \frac{3 - 0.5}{2} - \frac{0.5}{1} = 0.75A$$

$$P_{1V}^{absorb} = -(1)(0.75) = -0.75W \Rightarrow P_{1V}^{deliver} = 0.75W$$

SER	ID	NAME	KEY
-----	----	------	-----

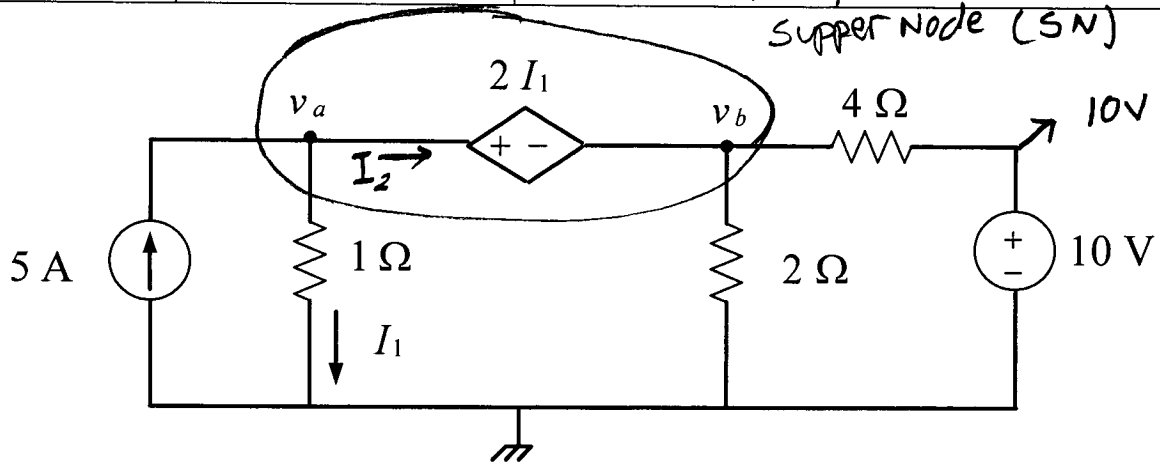

For the circuit shown above :

- (a) Using the node voltage method find the node voltages v_a, v_b ?
- (b) The power deliver by the dependent voltage source ?

(a) KCL at SN $\frac{v_a}{1} - 5 + \frac{v_b}{2} + \frac{v_b - 10}{4} = 0$

$$\Rightarrow 4v_a + 3v_b = 30 \quad \text{--- (1)}$$

Voltage Restriction $v_a - v_b = 2I_1 = 2\frac{v_a}{1}$

$$\Rightarrow v_a + v_b = 0 \quad \text{--- (2)}$$

solving (1), (2) $\Rightarrow v_a = 30V \quad v_b = -30V$

(b) $P_{2I_1}^{absorb} = (2I_1)I_2$ seeking I_1, I_2 ?

$$I_1 = \frac{v_a}{1} = \frac{30}{1} = 30A \quad I_2 = 5 - I_1 = -25A$$

$$P_{2I_1}^{absorb} = (2(30))(-25) = -1500W$$

$$\Rightarrow P_{2I_1}^{deliver} = 1500W$$