

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

EE 202

EXAM II

DATE: Sunday 17 Nov 2013

TIME: 6:00 PM-7:30 PM

SER #	Solution – Ver 2
ID#	
Name	
Section#	

	Maximum Score	Score
Question 1	32	
Question 2	23	
Question 3	22	
Question 4	23	
Total	100	


**** Question 1** is a Multiple Choice . You select one answer only.

**** Question 3** Put your answer in 3 X 3 Matrix form as indicated

Do not solve.

Question 1 [Parts (a) to (h) 28 points]:


Part (a) [5 points]:

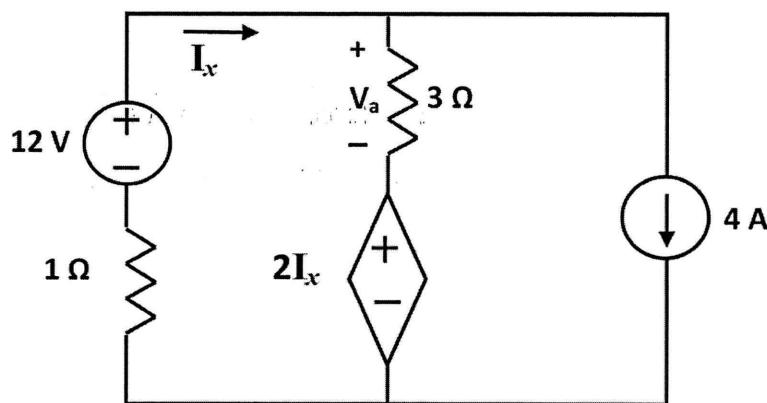

Determine the voltage V_a in the circuit above: (Hint: You may use the superposition principle)

- i) -12 V,
- ii) 12 V,
- iii) 0 V, (circled)
- iv) -6 V,
- v) 6 V,



Part (b) [5 points]:

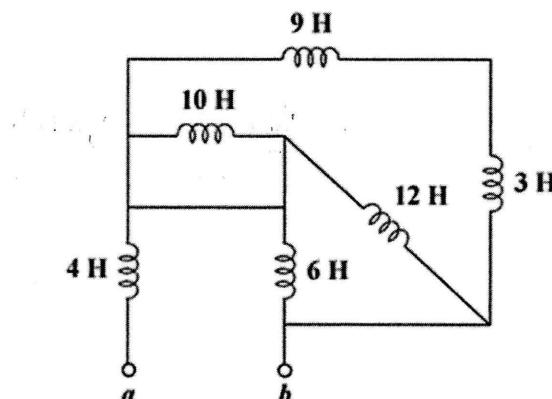

Find the equivalent inductance looking into the terminals a and b of the circuit:

- i) 6.3 H,
- ii) 7 H, (circled)
- iii) 0 H,
- iv) 10.4 H,
- v) 20 H.


Part (c) [5 points]:

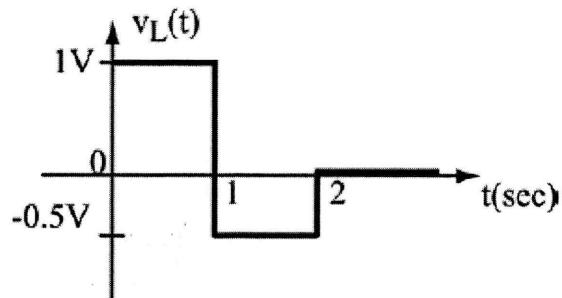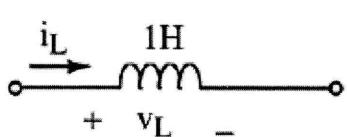

The inductor voltage $V_L(t)$ is as shown in the figure above. It is also known that $i_L(\infty) = 0$. The initial condition $i_L(0^+)$ is :

- i) -2.5, ii) 2.5, **iii) -0.5,** iv) 0.5, v) -1.5, vi) 1.5, vii) none of the previous answers.


Part (d) [5 points]:

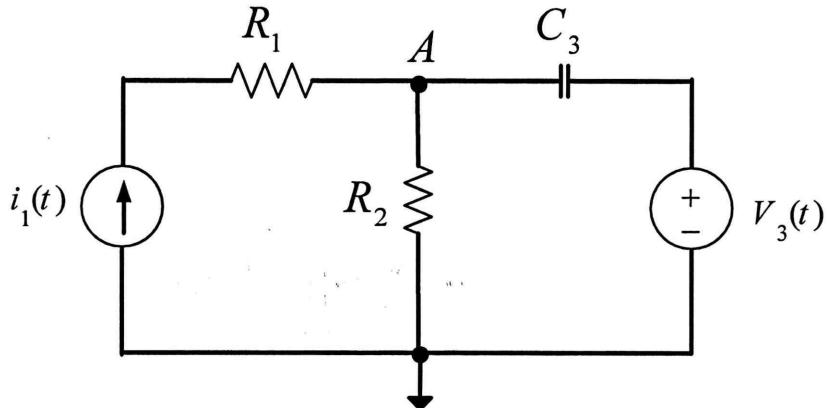

In the circuit above, the Node Voltage Equations is:

- i) $-i_1(t) + \frac{V_A(t)}{R_2} + C_3 \frac{d}{dt}[V_3(t) - V_A(t)] = 0,$ ii) $\frac{V_A(t)}{R_1} + \frac{V_A(t)}{R_2} + C_3 \frac{d}{dt} V_A(t) = 0,$
iii) $-i_1(t) + \frac{V_A(t)}{R_2} + C_3 \frac{d}{dt}[V_A(t) - V_3(t)] = 0,$ iv) $-i_1(t) + \frac{V_A(t)}{R_2} - C_3 \frac{d}{dt} V_A(t) = 0$
 v) $i_1(t) + \frac{V_A(t)}{R_2} + C_3 \frac{d}{dt} V_A(t) = 0,$ vi) $i_1(t) - \frac{V_A(t)}{R_2} - C_3 \frac{d}{dt} V_3(t) = 0,$

Part (e), (f), (g), and (h):

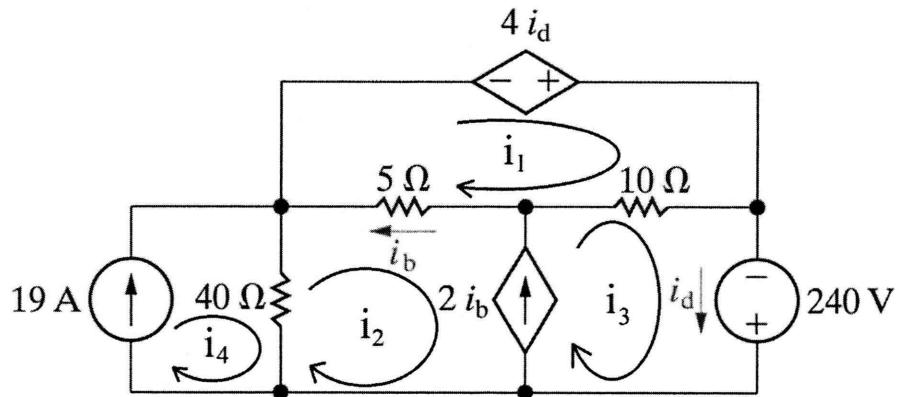

The Mesh-Currents in the above circuit are $i_1 = 18 \text{ A}$, $i_2 = 26 \text{ A}$, and $i_3 = 10 \text{ A}$, find the following:

Part (e) [3 points]: the power generated by dependent voltage source ($4 i_d$) is:

- i) -720 W,
- ii) 720 W,
- iii) -480 W,
- iv) 480 W,
- v) -640 W,
- vi) 640 W,
- vii) -180 W,
- viii) 180.

Part (f) [3 points]: the power generated by dependent current source ($2 i_b$) is:

- i) -256 W,
- ii) 256 W,
- iii) -2560 W,
- iv) 2560 W,
- v) -3600 W,
- vi) 3600 W,
- vii) -5120 W,
- viii) 5120 W,

Part (g) [3 points]: the power generated by independent current source (19 A) is:

- i) -12920 W,
- ii) 12920 W,
- iii) -5320 W,
- iv) 5320 W,
- v) -280 W,
- vi) 280 W,
- vii) -2520 W,
- viii) 2520 W,


Part (h) [3 points]: the power absorbed by all the resistors (5Ω , 10Ω , & 40Ω) is:

- i) -12280 W,
- ii) 12280 W,
- iii) -10120 W,
- iv) 10120 W,
- v) -2920 W,
- vi) 2920 W,
- vii) -81960 W,
- viii) 81960 W,

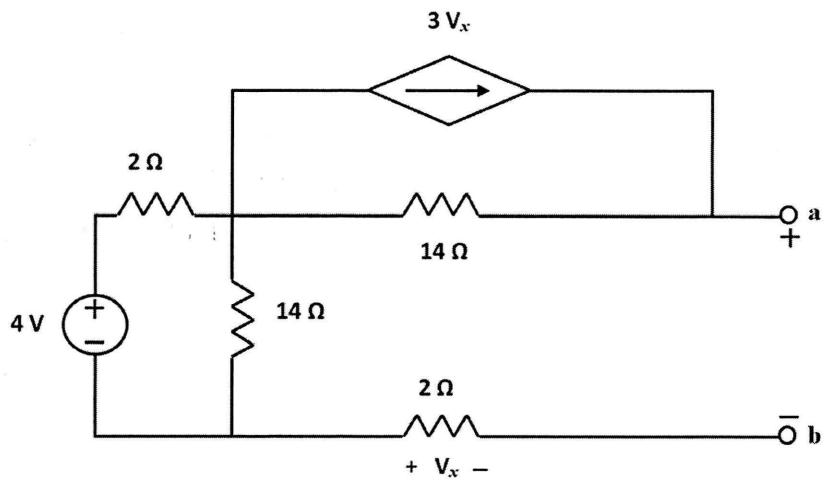
Question 2 [24 points]:

For the circuit shown below:

- Find the open circuit voltage V_{OC} between the terminals **a** and **b** directly?
(Do not use source transformation)
- Find the R_{th} using any method?
- If a load resistor R_L is connected between terminals **a** and **b**, find the maximum power absorbed by this load resistor?



(a)

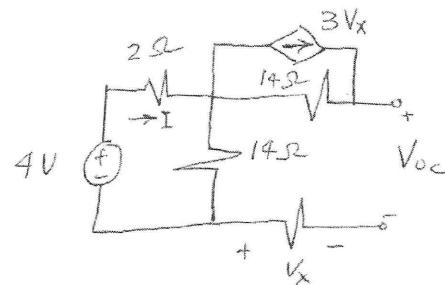

$$V_{oc} = 4 \left(\frac{14}{14+2} \right) = 3.5 \text{ V}$$

OR

KVL in left loop


$$-4 + 16I = 0$$

$$I = 4/16 = 0.25 \text{ A}$$

$$V_{oc} = I(14) = (0.25)(14) \quad \boxed{V_{oc} = 3.5 \text{ V}}$$

(b)

Using I_{sc}

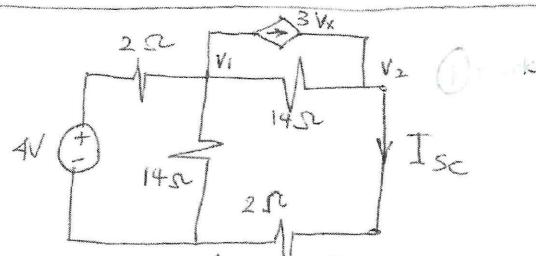

node ①

$$\frac{V_1 - 4}{2} + \frac{V_1}{14} + \frac{V_1 - V_2}{14} + 3V_x = 0 \quad \boxed{I}$$

node ②

$$\frac{V_2 - V_1}{14} + \frac{V_2}{2} - 3V_x = 0 \quad \boxed{II}$$

(i) \rightarrow since $V_2 = -V_x$ [Substitute in (I) and (II)]

(ii) $\rightarrow \boxed{V_2 = 0.069 \text{ V}}$

$$I_{sc} = \frac{V_2}{2} = 34.4 \text{ mA}$$


$$R_{th} = \frac{V_{oc}}{I_{sc}} \Rightarrow \boxed{R_{th} = \frac{3.5}{34.4 \times 10^{-3}} = 101.75 \Omega} \rightarrow (1 \text{ mark})$$

Using Test Source

OR

6

Ans

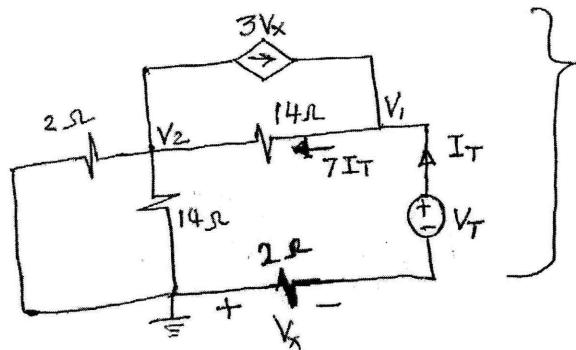

$$V_x = 2 I_T \Rightarrow 3V_x = 6 I_T \rightarrow$$

$$V_1 = V_T - V_x \Rightarrow V_1 = V_T - 2 I_T \rightarrow$$

node V2

$$\frac{V_2 - V_1}{14} + \frac{V_2}{2} + \frac{V_2}{14} + 6 I_T = 0 \quad \text{--- (I)} \rightarrow$$

$$V_1 - 9V_2 = 84 I_T \quad \text{--- (II)}$$

$$\text{also } \frac{V_1 - V_2}{14} = 7 I_T \quad \text{--- (III)} \rightarrow$$

Solving (I) and (II)

$$814 I_T = 8 V_T$$

$$R_{th} = \frac{V_T}{I_T} = \frac{814}{8} \quad \left. \right\} \rightarrow$$

$$R_{th} = 101.75 \Omega \rightarrow$$

Ans


(C)

$$R_L = R_{th} = 101.75 \quad \left. \right\} \rightarrow$$

$$P_{max} = \frac{V_{oc}^2}{4R_L} \quad \left. \right\}$$

$$P_{max} = \frac{(3.5)^2}{4(101.75)} = 30mW$$

Question 3 [22 points]:

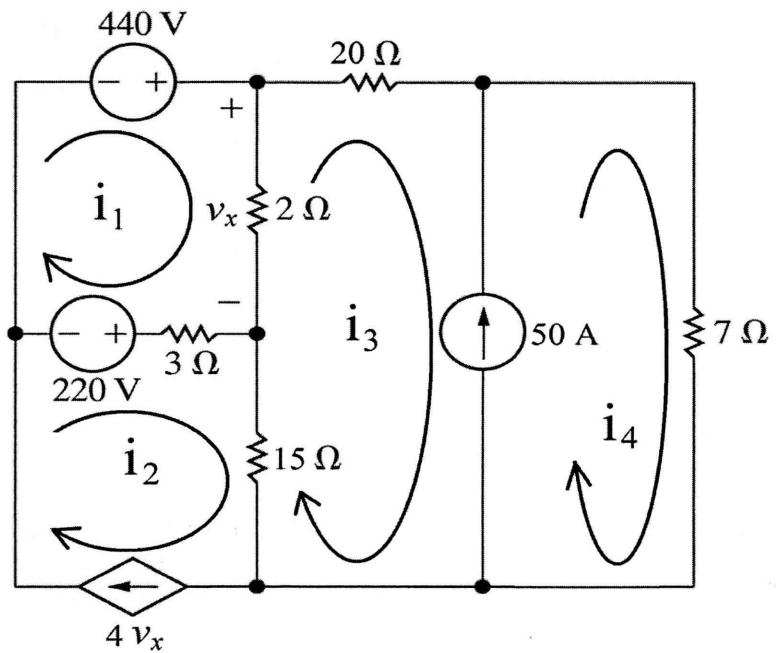

For the circuit shown above find the Mesh-Current equations necessary to solve for the node voltages i_1 , i_2 , i_3 , i_4 , simplify the equations and put them in the matrix form as

$$\left[\begin{array}{c} \\ \\ \\ \end{array} \right] \left[\begin{array}{c} i_1 \\ i_2 \\ i_3 \\ i_4 \end{array} \right] = \left[\begin{array}{c} \\ \\ \\ \end{array} \right]$$

(DO NOT SOLVE THE SYSTEM OF EQUATIONS)

[~~Ans~~] One Negative sign of current direction in Kvl in Mesh#1

$$-440 + 2(i_1 - i_3) + 3(i_1 - i_2) + 220 = 0 \quad \dots \quad (1)$$

[3 Marks, Any additional sign or other, no points] Current Source 50 A:

$$i_4 - i_3 = 50 \quad \dots \quad (2)$$

[~~Ans~~] Any additional sign or other, no points] Current Source 4 v_x :

$$i_2 = 4 v_x \quad \dots \quad (3)$$

[~~Ans~~] Any additional sign or other, no points] Supermesh M3+M4 - kvl:

$$15(i_3 - i_2) + 2(i_3 - i_1) + 20i_3 + 7i_4 = 0 \quad \dots \quad (4)$$

[~~Ans~~] Any additional sign or other, no points] Help Equation for the dependent source:


$$v_x = 2(i_1 - i_3) \quad \dots \quad (H)$$

[~~Ans~~, one mark for the simplification error, and 4, Zero if out row has a simplification error] simplify (1), Substitute (H) in (3), simplify (4) to get

$$\begin{bmatrix} 5 & -3 & -2 & 0 \\ 0 & 0 & -1 & 1 \\ 8 & -1 & -8 & 0 \\ -2 & -15 & 37 & 7 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 220 \\ 50 \\ 0 \\ 0 \end{bmatrix}$$

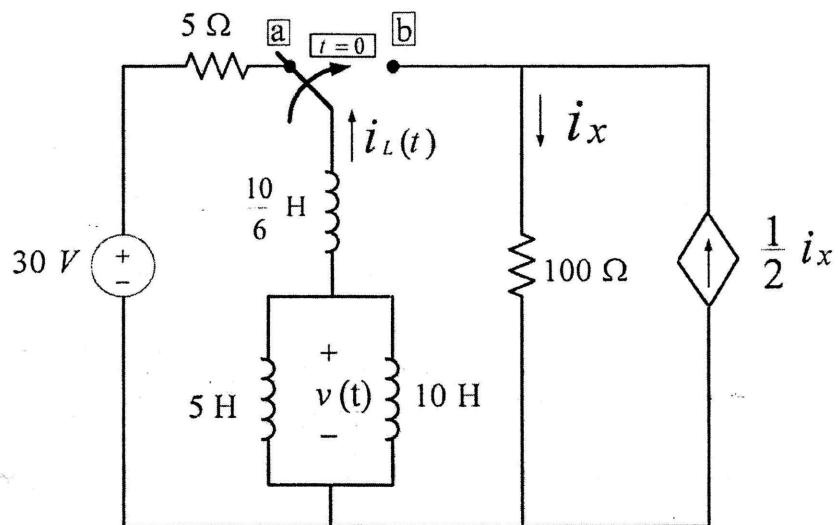Question 4 [24 points]:

In the below circuit, the switch is moved from position "a" to position "b" at time $t = 0$. Solve the following questions and write the final answers in the box.



- a) Find the initial value of i_L

$$i_L(0^+) = -6$$

- b) Find the final value of i_L

$$i_L(\infty) = \text{Zero}$$

- c) Find the time constant τ for $t \geq 0$

$$\tau = 25 \text{ msec}$$


$$\bar{\tau} = \frac{L_{eq}}{R_{eq}}$$

$$L_{eq} = \frac{10}{6} + \frac{(5)(10)}{5+10} = 5 \text{ H}$$

$$I_T = i_x - \frac{1}{2} i_x = \frac{1}{2} i_x$$

$$i_x = \frac{V_T}{100 \Omega}$$
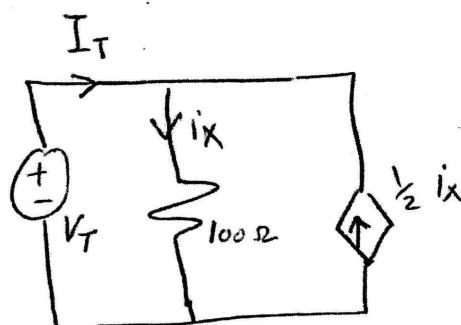
$$I_T = \frac{V_T}{200} \rightarrow R_{eq} = \frac{V_T}{I_T} = 200 \Omega$$



$$\bar{\tau} = \frac{5}{200} = 25 \times 10^{-3} \text{ sec}$$

d) Find the expression of $i_L(t)$ for $t \geq 0$

$$i_L(t) = -6 e^{-t/25*10^{-3}}$$

e) Find the expression of $v(t)$ across the 10 H inductor for $t \geq 0$

$$v(t) = -800 e^{-t/25*10^{-3}}$$

$$\begin{aligned}
 V(+)&= -L_{5/10} \frac{d i_L(t)}{dt} \\
 &= -\frac{50}{15} \frac{d}{dt} \left[-6 e^{-t/25*10^{-3}} \right] \\
 &= \frac{(50)(6)}{15} \left(-\frac{1}{25*10^{-3}} \right) e^{-t/25*10^{-3}} \\
 &= -\frac{20}{25} * 10^3 e^{-t/25*10^{-3}} \\
 &= -800 e^{-t/25*10^{-3}}
 \end{aligned}$$