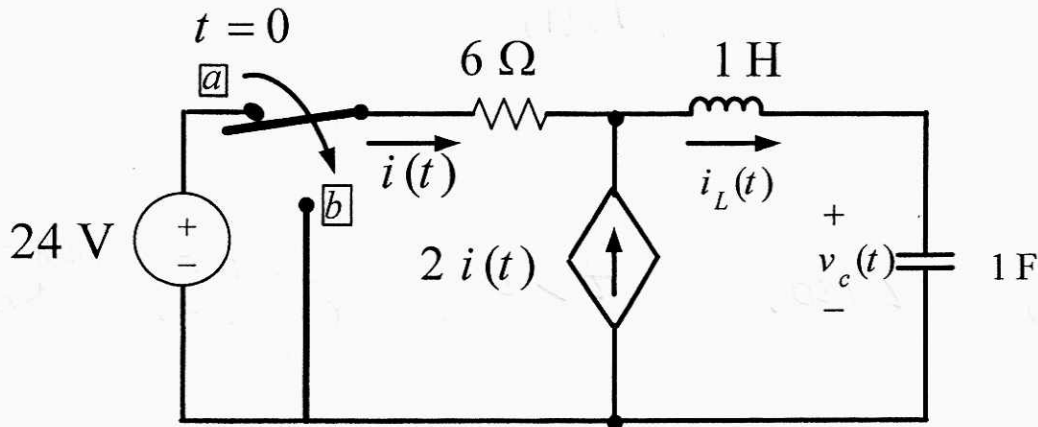


Sec	Ser	ID	Name
-----	-----	----	------





For the circuit shown above, the switch was in position **a** for a long time, then at time $t=0$ the switch move to position **b**. Find the followings :

- (a) α ?
- (b) ω_0 ?
- (c) $i(\infty)$?
- (d) $i_L(0^+)$?
- (e) $v_c(0^+)$?
- (f) $i(0^+)$?
- (g) $\frac{di(0^+)}{dt}$?
- (h) General expersion for $i(t)$?

$$x(t) = X_f + \begin{cases} A_1 e^{s_1 t} + A_2 e^{s_2 t} \\ e^{-\alpha t} \{ B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t) \} \\ D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} \end{cases}$$

(Do not evaluate the costants)

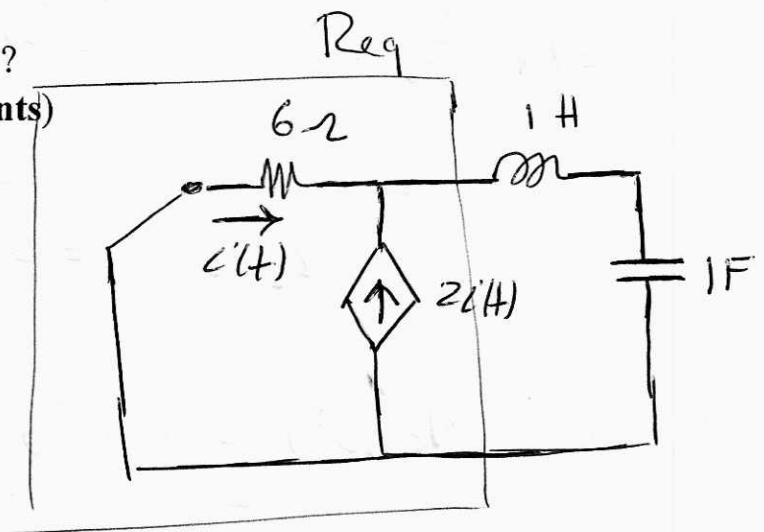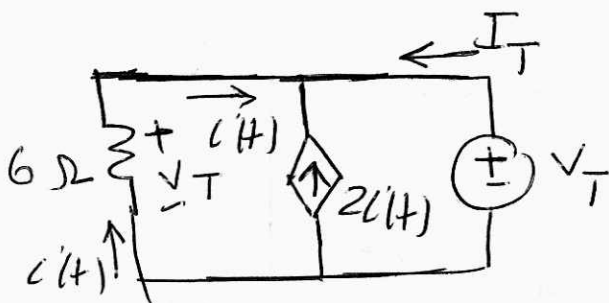(a) $\alpha = \frac{R_{eq}}{2L} \quad t > 0$




$$I_T = -3i(t) = -3 \left(-\frac{V_T}{6} \right) = \frac{V_T}{2} \Rightarrow R_{eq} = \frac{V_T}{I_T} = 2\Omega$$

$$\Rightarrow \alpha = \frac{2}{2(1)} = 1 \text{ rad/s}$$

$$(b) \omega_0 = \frac{1}{\sqrt{LC}} \quad t > 0$$


$$= \frac{1}{\sqrt{(1)(1)}} = 1 \text{ rad/s}$$

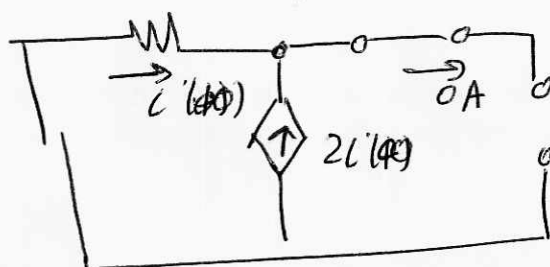(c) $i'(\infty)$ $t > 0$ inductor short
capacitor open




$$3i'(\infty) = 0 \\ \Rightarrow i'(\infty) = 0$$

(d) $i_L(0^+) = i_L(0^-)$ ($t < 0$)

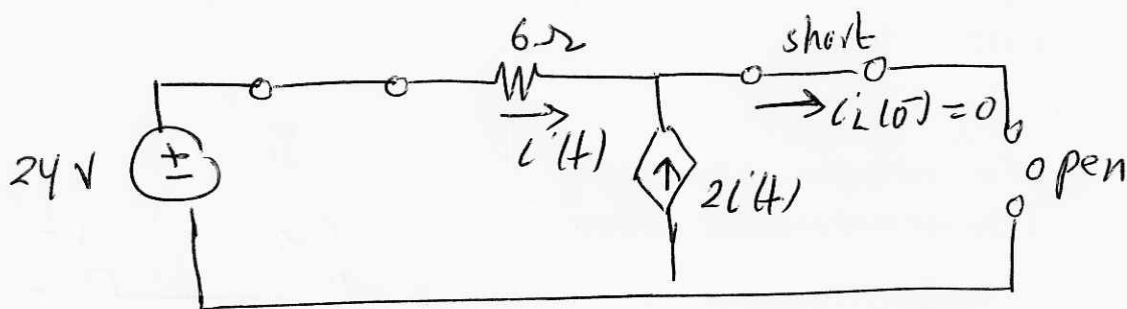

$$i_L(0^-) = 0$$


(e) $V_C(0^+) = V_C(0^-)$ ($t < 0$)

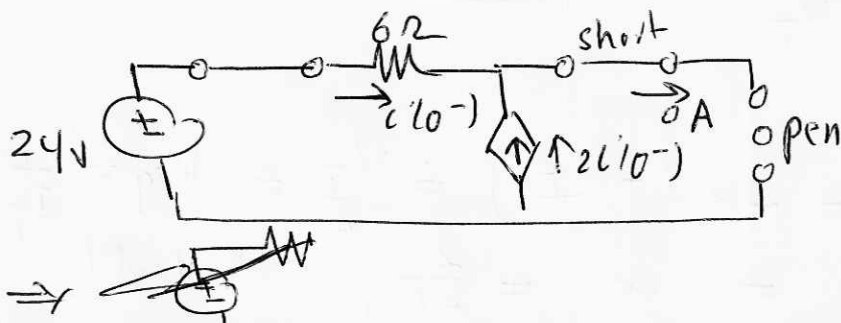

$$3i'(0^-) = 0 \\ \Rightarrow i'(0^-) = 0 \\ \Rightarrow V_C(0^-) = 24 \text{ V} \\ = V_C(0^+)$$


(f) $i'(0^+) \stackrel{?}{=} i'(0^-)$ NO

\Rightarrow look at $t = 0^+$

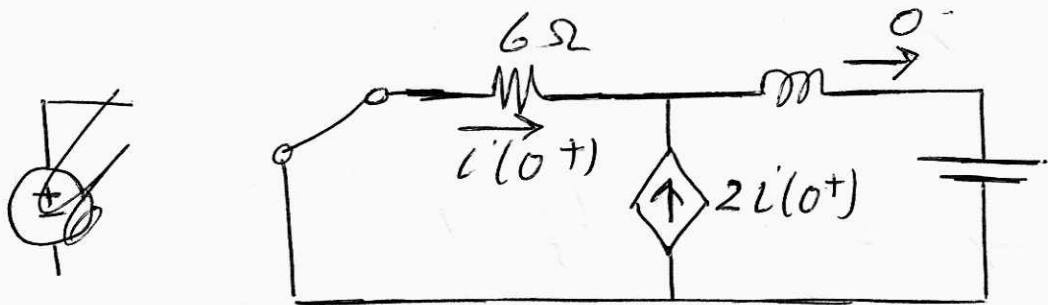

$3i'(0^+) = 0 \Rightarrow i'(0^+) = 0$

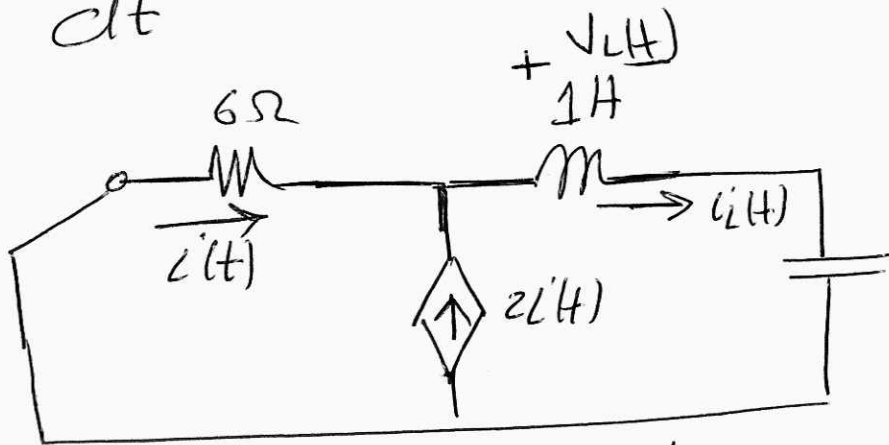
(g) $\frac{di(0^+)}{dt} \stackrel{?}{=} \text{Look at } t \gg 0$



$3i(t) = i_L(t) \Rightarrow 3 \frac{di(t)}{dt} = \frac{di_L(t)}{dt} = \frac{V_L(t)}{L}$

$\Rightarrow \frac{di(t)}{dt} = \frac{1}{3} V_L(t) \Rightarrow \frac{di(0^+)}{dt} = \frac{V_L(0^+)}{3}$

Now Look at $t = 0^+$

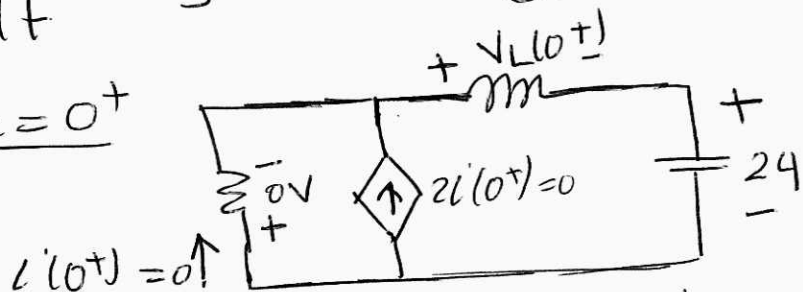

$\Rightarrow V_L(0^+) = -24 \Rightarrow \frac{di(0^+)}{dt} = \frac{-24}{3} = -8 \text{ A/s}$

(h) Since $\alpha = \omega_0 = 1$ rad/s

\Rightarrow Critical damped

$$\Rightarrow i(t) = i_f + D_1 t e^{-\alpha t} + D_2 e^{-\alpha t}$$

$$= 0 + D_1 t e^{-t} + D_2 e^{-t}$$

$$= \cancel{D_1 t e^{-t}}$$

$$= e^{-t} [D_1 t + D_2] \quad A$$