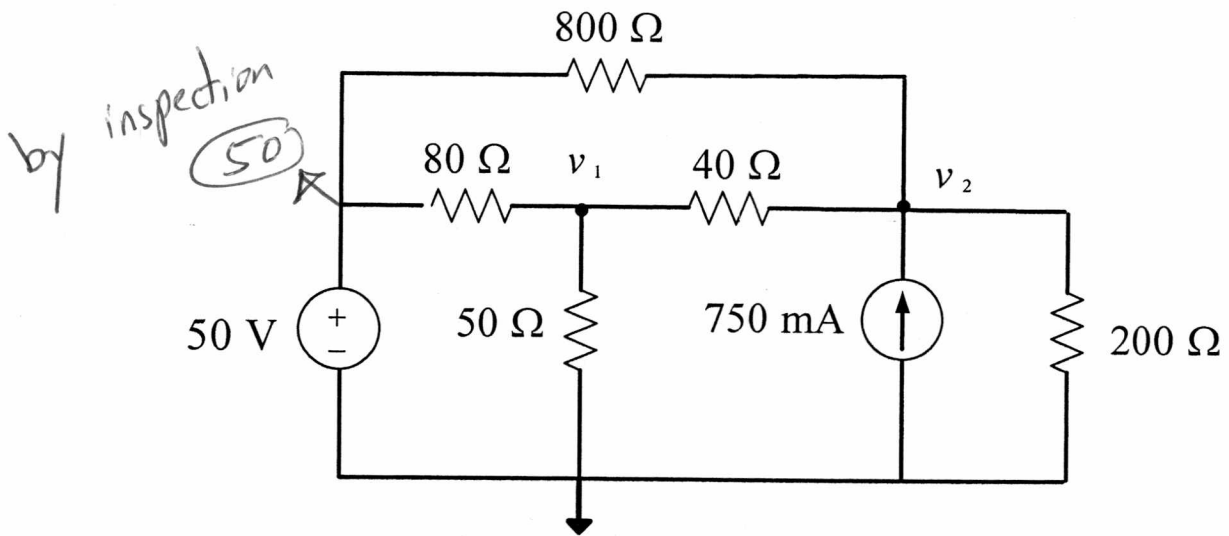


Sec	Ser	ID	Name	KEY
-----	-----	----	------	-----



For the circuit shown above use the node voltage method to find the node voltages  $v_1, v_2$  ?

Kcl on node  $v_1$

$$\frac{v_1 - 50}{80} + \frac{v_1}{50} + \frac{v_1 - v_2}{40} = 0$$

$$\Rightarrow 23v_1 - 10v_2 = 250 \quad \text{--- (1)}$$

Kcl on node  $v_2$

$$\frac{v_2 - v_1}{40} - 0.75 + \frac{v_2}{200} + \frac{v_2 - 50}{800} = 0$$

$$\Rightarrow -20v_1 + 25v_2 = 650 \quad \text{--- (2)}$$


solving (1), (2)

$$v_1 = 34 \text{ V}$$

$$v_2 = 53.2 \text{ V}$$

EE 202-06-Fall 2013(131)  
QZ1

Sec	Ser	ID	Name
			KEY

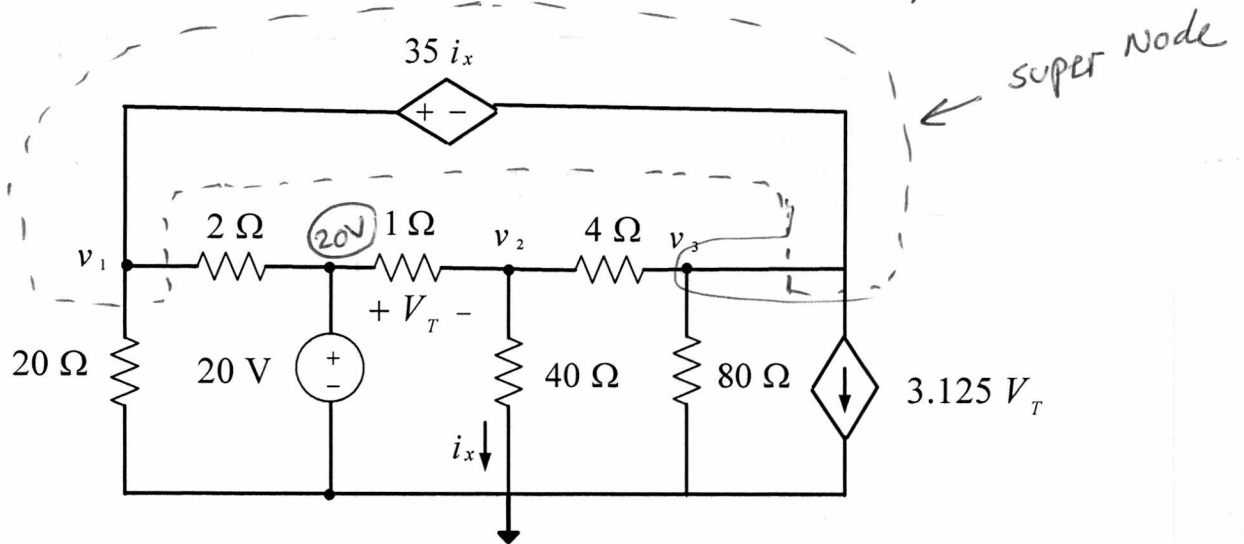

For the circuit shown above find the simplified nodal equations necessary to solve for the node voltages  $v_1, v_2, v_3$ ? Do not solve the equations

Kcl on supernode

$$\frac{v_1}{20} + \frac{v_1 - 20}{2} + \frac{v_3 - v_2}{4} + \frac{v_3}{80} + 3.125 v_T = 0$$

$$v_T = 20 - v_2$$

$$\Rightarrow 44 v_1 - 270 v_2 + 21 v_3 = -4200 \quad \text{--- (1)}$$

Kcl on node v2

$$\frac{v_2 - 20}{1} + \frac{v_2 - v_3}{4} + \frac{v_2}{40} = 0$$

$$\Rightarrow 51 v_2 - 10 v_3 = 800 \quad \text{--- (2)}$$

~~Kcl on no~~

voltage source restriction

$$v_1 - v_3 = 35 i_x = 35 \frac{v_2}{40}$$

$$\Rightarrow 8 v_1 - 7 v_2 - 8 v_3 = 0 \quad \text{--- (3)}$$

$$\begin{bmatrix} 44 & -270 & 21 \\ 51 & 0 & -10 \\ 8 & -7 & 8 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} -4200 \\ 800 \\ 0 \end{bmatrix}$$